

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO  
5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 0

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① When there is an electric current passing through a wire, the particles moving are:

- ☐ A electrons.  
☐ B protons.  
☐ C atoms.  
☐ D ions.

CP5201400010

- ② The unit of current is:

- ☐ A ampere.  
☐ B watt.  
☐ C volt.  
☐ D coulomb.

CP5201400020

- ③ A positive charge released from rest:

- ☐ A moves towards the regions of lower potential.  
☐ B moves towards the regions of higher potential.  
☐ C moves towards the regions of equal potential.  
☐ D does not move.

CP5201400030

- ④ The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- ☐ A Current.  
☐ B Voltage.  
☐ C Power.  
☐ D Resistance.

CP5201400040

- ⑤ Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.

- ☐ A To the right.  
☐ B To the left.  
☐ C Downward.  
☐ D Upward.

CP5201400050

- ⑥ A battery is used to:

- ☐ A maintain a potential difference.  
☐ B measure electric current.  
☐ C measure electric potential.  
☐ D safeguard against short-circuit.

CP5201400060

- ⑦ The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- ☐ A potential difference.  
☐ B current.  
☐ C resistance.  
☐ D power.

CP5201400070

- ⑧ Joule/coulomb is same as:

- ☐ A volt.  
☐ B watt.  
☐ C ampere.  
☐ D ohm.

CP5201400080

- ⑨ Complete the following statement: “The electromotive force is:

- ☐ A the maximum potential difference between the terminals of a battery”.

- ☐ B the force that accelerates electrons through a wire when a battery is connected to it".
- ☐ C the force that accelerates protons through a wire when a battery is connected to it".
- ☐ D the maximum electric potential energy stored within a battery".

CP5201400090

- (10) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

- ☐ A  $2.2 \times 10^{20}$ .
- ☐ B 36.
- ☐ C  $4.8 \times 10^{15}$ .
- ☐ D  $6.4 \times 10^{18}$ .

CP5201400100

- (11) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- ☐ A 600 C.
- ☐ B 200 C.
- ☐ C 500 C.
- ☐ D 400 C.

CP5201400110

- (12) Ohm's law relates potential difference with:

- ☐ A current.
- ☐ B power.
- ☐ C energy.
- ☐ D time.

CP5202400010

- (13) The current in a wire:

- ☐ A depends on both resistance and potential difference.
- ☐ B depends only on the potential difference applied.
- ☐ C depends only on the resistance of the wire.
- ☐ D does not depend on resistance and potential difference.

CP5202400020

- (14) Determine which of the following statements does not represent Ohm's law.

- ☐ A current = resistance  $\times$  potential difference.
- ☐ B current / potential difference = constant.
- ☐ C potential difference / current = constant.
- ☐ D potential difference = current  $\times$  resistance.

CP5202400030

- (15) The potential difference required to pass a current 0.2 A in a wire of resistance 20  $\Omega$  is:

- ☐ A 4 V.
- ☐ B 100 V.

- ☐ C 1 V.
- ☐ D 40 V.

CP5202400040

- (16) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- ☐ A 5 W.
- ☐ B 0.5 W.
- ☐ C 0.2 W.
- ☐ D 2 W.

CP5202400050

- (17) Determine which of the graphs in Figure 2 at the end of the text represents Ohm's law for a solid conductor.

- ☐ A (c).
- ☐ B (a).
- ☐ C (b).
- ☐ D (d).

CP5202400060

- (18) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the resistance of the wire.

- ☐ A 1.7  $\Omega$ .
- ☐ B 1  $\Omega$ .
- ☐ C 0.8  $\Omega$ .
- ☐ D 0.4  $\Omega$ .

CP5202400070

- (19) The unit of resistivity is:

- ☐ A ohm·m.
- ☐ B ohm.
- ☐ C ohm/m.
- ☐ D ohm/m<sup>2</sup>.

CP5203400010

- (20) The resistivity of a wire depends on:

- ☐ A material.
- ☐ B length.
- ☐ C area of cross-section.
- ☐ D length, material and area of cross-section.

CP5203400020

- (21) A wire of length  $L$  and cross-sectional area  $A$  has a resistivity  $\rho$ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- ☐ A  $R = \frac{\rho L}{A}$ .
- ☐ B  $R = \frac{\rho A}{L}$ .
- ☐ C  $R = \frac{L}{\rho A}$ .
- ☐ D  $R = \frac{A}{\rho L}$ .

CP5203400030

- (22) All of the wires in Figure 4 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- ☐ (b).  
☐ (a).  
☐ (c).  
☐ (d).

CP5203400040

- (23) Two copper wires have the same cross-sectional area but have different lengths. Wire  $X$  has a length  $L$  and wire  $Y$  has a length  $2L$ . The ratio between the resistance of wire  $Y$  and wire  $X$  is:

- ☐  $\frac{R_Y}{R_X} = \frac{2}{1}$ .  
☐  $\frac{R_Y}{R_X} = \frac{1}{1}$ .  
☐  $\frac{R_Y}{R_X} = \frac{1}{2}$ .  
☐  $\frac{R_Y}{R_X} = \frac{1}{4}$ .

CP5203400050

- (24) Two aluminum wires have the same length and different cross-sectional area. Wire  $B$  has twice the radius of that of wire  $A$ . Determine how the resistance of wire  $B$  compares to the resistance of wire  $A$ .

- ☐  $\frac{R_B}{R_A} = \frac{1}{4}$ .  
☐  $\frac{R_B}{R_A} = \frac{1}{1}$ .  
☐  $\frac{R_B}{R_A} = \frac{1}{2}$ .  
☐  $\frac{R_B}{R_A} = \frac{2}{1}$ .

CP5203400060

- (25) The unit of electric power is:

- ☐ watt.  
☐ ampere.  
☐ volt.  
☐ joule.

CP5204400010

- (26) If  $D$  is the intensity of current circulating in a conductor and  $P$  is the voltage across the conductor, the power dissipated is described by the formula:

- ☐  $D \cdot P$ .  
☐  $D^2 \cdot P$ .  
☐  $D \cdot P^2$ .  
☐  $D^2 / P$ .

CP5204400020

- (27) If  $D$  is the intensity of current circulating in a resistor with resistance  $F$ , the power dissipated by the resistor is described by the formula:

- ☐  $D^2 \cdot F$ .  
☐  $D \cdot F$ .  
☐  $D \cdot F^2$ .  
☐  $D^2 / F$ .

CP5204400030

- (28) When a current  $I$  flows through a resistance  $R$  for time  $t$  the electrical energy spent is given by:

- ☐  $I^2 R t$ .  
☐  $I R t$ .  
☐  $I R^2 t$ .  
☐  $I^2 R / t$ .

CP5204400040

- (29) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- ☐ 30 J.  
☐ 60 J.  
☐ 15 J.  
☐ 120 J.

CP5204400050

- (30) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- ☐ 15 W.  
☐ 5 W.  
☐ 10 W.  
☐ 20 W.

CP5204400060

- (31) Determine which one of the following statements concerning resistors in series is *true*.

- ☐ The current through each resistor is the same.  
☐ The voltage across each resistor is the same.  
☐ The power dissipated by each resistor is the same.  
☐ The total current through the resistors is the sum of the current through each resistor.

CP5205400010

- (32) Determine which one of the following statements concerning resistors in parallel is *true*.

- ☐ The voltage across each resistor is the same.  
☐ The current through each resistor is the same.  
☐ The power dissipated by each resistor is the same.  
☐ The total voltage across the resistors is the sum of the voltage across each resistor.

CP5205400020

- (33) Two resistances of  $100 \Omega$  and zero ohm are connected in parallel. The overall resistance will be:

- ☐ A 0  $\Omega$ .
- ☐ B 100  $\Omega$ .
- ☐ C 50  $\Omega$ .
- ☐ D 25  $\Omega$ .

CP5205400030

- (34) Two resistances of 100  $\Omega$  and zero ohm are connected in series. The overall resistance will be:
- ☐ A 100  $\Omega$ .
  - ☐ B 50  $\Omega$ .
  - ☐ C 25  $\Omega$ .
  - ☐ D 0  $\Omega$ .

CP5205400040

- (35) Three resistors 2  $\Omega$ , 3  $\Omega$  and 4  $\Omega$  are connected so that the equivalent resistance is 9  $\Omega$ . The resistors are connected:
- ☐ A all in series.
  - ☐ B all in parallel.
  - ☐ C 2  $\Omega$  and 3  $\Omega$  in parallel and the combination in series with 4  $\Omega$ .
  - ☐ D 2  $\Omega$  and 3  $\Omega$  in series and the combination in parallel to 4  $\Omega$ .

CP5205400050

- (36) In Figure 5 at the end of the text,
- ☐ A 3  $\Omega$ , 6  $\Omega$  are in parallel and 9  $\Omega$  is in series.
  - ☐ B 6  $\Omega$ , 3  $\Omega$  and 9  $\Omega$  are in series.
  - ☐ C 9  $\Omega$  and 6  $\Omega$  are in parallel and the combination is in series with 3  $\Omega$ .
  - ☐ D 3  $\Omega$ , 6  $\Omega$  and  $\Omega$  are in parallel.

CP5205400060

- (37) In Figure 6 at the end of the text, the resistance across AB is:
- ☐ A 1  $\Omega$ .
  - ☐ B 4  $\Omega$ .
  - ☐ C 2  $\Omega$ .
  - ☐ D 0.5  $\Omega$ .

CP5205400070

- (38) Three equal resistances when combined in series are equivalent to 90  $\Omega$ . Their equivalent resistance when combined in parallel will be:
- ☐ A 10  $\Omega$ .
  - ☐ B 270  $\Omega$ .
  - ☐ C 30  $\Omega$ .
  - ☐ D 810  $\Omega$ .

CP5205400080

- (39) Two resistors  $R_1 = 3 \Omega$  and  $R_2 = 6 \Omega$  are connected in parallel. Compute the net resistance in the circuit.
- ☐ A 2  $\Omega$ .

- ☐ B 1  $\Omega$ .
- ☐ C 3  $\Omega$ .
- ☐ D 6  $\Omega$ .

CP5205400090

- (40) Two resistors  $R_1 = 6 \Omega$  and  $R_2 = 12 \Omega$  are connected in parallel to each other and in series to  $R_2 = 2 \Omega$ . Compute the net resistance in the circuit.
- ☐ A 6  $\Omega$ .
  - ☐ B 1  $\Omega$ .
  - ☐ C 3  $\Omega$ .
  - ☐ D 2  $\Omega$ .

CP5205400100

- (41) Text 1. State which of the following best defines a closed circuit.
- ☐ A Does not allow the electricity or electrons to flow through the wires, a switch is off.
  - ☐ B Does not allow the electricity or electrons to flow through the wires, a switch is on.
  - ☐ C Does allow the electricity or electrons to flow through the wires, a switch is on.
  - ☐ D Does allow the electricity or electrons to flow through the wires, a switch is off.

CP5209400010

- (42) Text 1. State which of the following circuits have different amounts of electricity flowing through them.
- ☐ A Parallel circuits.
  - ☐ B Closed circuits.
  - ☐ C Open circuits.
  - ☐ D Series circuits.

CP5209400020

- (43) Text 1. State which of the following is the system connecting power plants across the country.
- ☐ A Transformer.
  - ☐ B Power grid.
  - ☐ C Meter.
  - ☐ D Transmission line.

CP5209400030

- (44) Text 1. State which of the following is used to measure electricity used by a home or business.
- ☐ A Voltage.
  - ☐ B Meter.
  - ☐ C Battery.
  - ☐ D Conductor.

CP5209400040

- (45) Text 1. All of the following are examples of conductors except:
- ☐ A Water.
  - ☐ B Glass.

☐ C Aluminum.

☐ D Copper.

☐ B Porcelain.

☐ C Plastic.

☐ D Trees.

CP5209400050

46 Text 1. All of the following are examples of insulators except:

☐ A Rubber.

CP5209400060

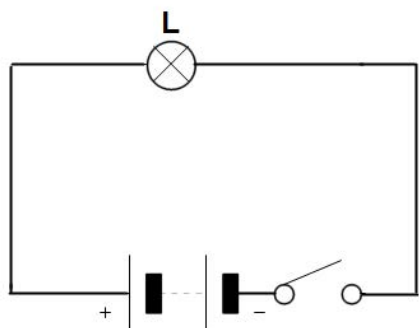


Figura 1

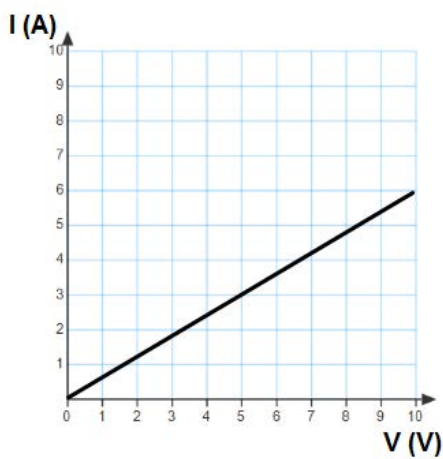


Figura 3

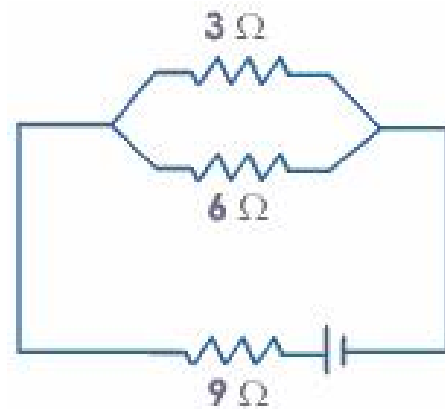


Figura 5

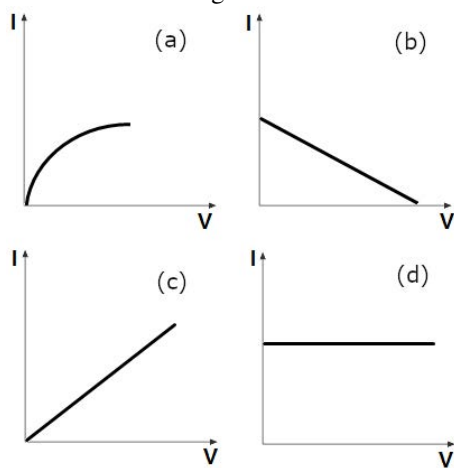


Figura 2

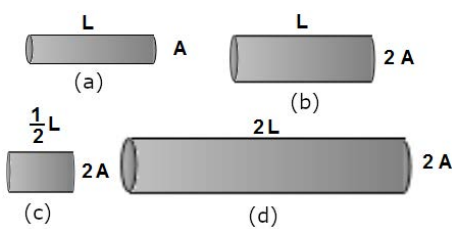


Figura 4

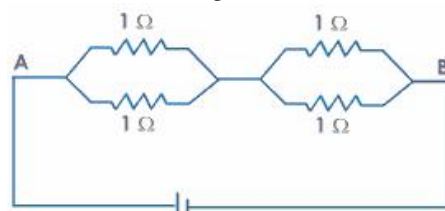


Figura 6