

LICEO STATALE “NICCOLÒ MACHIAVELLI” DI ROMA
5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

VERSIONE ♡0

DATA CLASSE

ALUNNO

IL PUNTEGGIO PER OGNI RISPOSTA CORRETTA È DI 4 PUNTI, PER OGNI RISPOSTA OMESSA 1 PUNTO, PER OGNI RISPOSTA SBAGLIATA 0 PUNTI. LA DURATA DELLA VERIFICA È DI UN’ORA. SI SUGGERISCE DI RICOPIARE LE RISPOSTE NELLA TABELLA A SEGUIRE O IN CASO DI DIFFICOLTÀ NELLA COPIA SE NE SEGNALI L’ASSENZA.

TABELLA DELLE RISPOSTE									
1	2	3	4	5	6	7	8	9	10
11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40

① WHEN THERE IS AN ELECTRIC CURRENT PASSING THROUGH A WIRE, THE PARTICLES MOVING ARE:

☐ A ELECTRONS.

☐ B PROTONS.

☐ C ATOMS.

☐ D IONS.

② THE UNIT OF CURRENT IS:

- ☐ A AMPERE.
- ☐ B WATT.
- ☐ C VOLT.
- ☐ D COULOMB.

③ A POSITIVE CHARGE RELEASED FROM REST:

- ☐ A MOVES TOWARDS THE REGIONS OF LOWER POTENTIAL.
- ☐ B MOVES TOWARDS THE REGIONS OF HIGHER POTENTIAL.
- ☐ C MOVES TOWARDS THE REGIONS OF EQUAL POTENTIAL.
- ☐ D DOES NOT MOVE.

④ THE AMOUNT OF CHARGE FLOWING THROUGH A CROSS-SECTIONAL AREA OF A WIRE PER UNIT OF TIME IS CALLED:

- ☐ A CURRENT.
- ☐ B VOLTAGE.
- ☐ C POWER.
- ☐ D RESISTANCE.

⑤ DETERMINE THE DIRECTION OF THE CONVENTIONAL CURRENT THROUGH THE LIGHT BULB IN THE CIRCUIT PRESENTED IN FIGURE 1 AT THE END OF THE TEXT.

- ☐ A TO THE RIGHT.
- ☐ B TO THE LEFT.
- ☐ C DOWNWARD.
- ☐ D UPWARD.

⑥ A BATTERY IS USED TO:

- ☐ A MAINTAIN A POTENTIAL DIFFERENCE.
- ☐ B MEASURE ELECTRIC CURRENT.
- ☐ C MEASURE ELECTRIC POTENTIAL.
- ☐ D SAFEGUARD AGAINST SHORT-CIRCUIT.

7 THE WORK DONE IN MOVING A UNIT POSITIVE CHARGE ACROSS TWO POINTS IN AN ELECTRIC CIRCUIT IS A MEASURE OF:

- ☐ A POTENTIAL DIFFERENCE.
- ☐ B CURRENT.
- ☐ C RESISTANCE.
- ☐ D POWER.

8 JOULE/COULOMB IS SAME AS:

- ☐ A VOLT.
- ☐ B WATT.
- ☐ C AMPERE.
- ☐ D OHM.

9 COMPLETE THE FOLLOWING STATEMENT: "THE ELECTROMOTIVE FORCE IS:

- ☐ A THE MAXIMUM POTENTIAL DIFFERENCE BETWEEN THE TERMINALS OF A BATTERY".
- ☐ B THE FORCE THAT ACCELERATES ELECTRONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
- ☐ C THE FORCE THAT ACCELERATES PROTONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
- ☐ D THE MAXIMUM ELECTRIC POTENTIAL ENERGY STORED WITHIN A BATTERY".

10 COMPUTE THE NUMBER OF ELECTRONS FLOWING THROUGH A BATTERY THAT DELIVERS A CURRENT OF 3.0 A FOR 12 S.

- ☐ A 2.2×10^{20} .
- ☐ B 36.
- ☐ C 4.8×10^{15} .
- ☐ D 6.4×10^{18} .

11 A 10 A CURRENT IS MAINTAINED IN A SIMPLE CIRCUIT. COMPUTE THE NET CHARGE THAT PASSES THROUGH ANY POINT IN THE CIRCUIT DURING A 1 MINUTE INTERVAL.

- ☐ A 600 C.
- ☐ B 200 C.
- ☐ C 500 C.
- ☐ D 400 C.

- ⑫ OHM'S LAW RELATES POTENTIAL DIFFERENCE WITH:
- ☐ A CURRENT.
 - ☐ B POWER.
 - ☐ C ENERGY.
 - ☐ D TIME.
- ⑬ THE CURRENT IN A WIRE:
- ☐ A DEPENDS ON BOTH RESISTANCE AND POTENTIAL DIFFERENCE.
 - ☐ B DEPENDS ONLY ON THE POTENTIAL DIFFERENCE APPLIED.
 - ☐ C DEPENDS ONLY ON THE RESISTANCE OF THE WIRE.
 - ☐ D DOES NOT DEPEND ON RESISTANCE AND POTENTIAL DIFFERENCE.
- ⑭ DETERMINE WHICH OF THE FOLLOWING STATEMENTS DOES NOT REPRESENT OHM'S LAW.
- ☐ A $\text{CURRENT} = \text{RESISTANCE} \times \text{POTENTIAL DIFFERENCE}$.
 - ☐ B $\text{CURRENT} / \text{POTENTIAL DIFFERENCE} = \text{CONSTANT}$.
 - ☐ C $\text{POTENTIAL DIFFERENCE} / \text{CURRENT} = \text{CONSTANT}$.
 - ☐ D $\text{POTENTIAL DIFFERENCE} = \text{CURRENT} \times \text{RESISTANCE}$.
- ⑮ THE POTENTIAL DIFFERENCE REQUIRED TO PASS A CURRENT 0.2 A IN A WIRE OF RESISTANCE $20\ \Omega$ IS:
- ☐ A 4 V.
 - ☐ B 100 V.
 - ☐ C 1 V.
 - ☐ D 40 V.
- ⑯ THE RESISTANCE OF AN ELECTRIC BULB DRAWING 1.2 A CURRENT AT 6.0 V IS:
- ☐ A 5 W.
 - ☐ B 0.5 W.
 - ☐ C 0.2 W.
 - ☐ D 2 W.

- 17) DETERMINE WHICH OF THE GRAPHS IN FIGURE 2 AT THE END OF THE TEXT REPRESENTS OHM'S LAW FOR A SOLID CONDUCTOR.
- ☐ A (C).
 - ☐ B (A).
 - ☐ C (B).
 - ☐ D (D).
- 18) THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 3. COMPUTE THE RESISTANCE OF THE WIRE.
- ☐ A $1.7 \, \Omega$.
 - ☐ B $1 \, \Omega$.
 - ☐ C $0.8 \, \Omega$.
 - ☐ D $0.4 \, \Omega$.
- 19) THE UNIT OF RESISTIVITY IS:
- ☐ A $\text{OHM} \cdot \text{M}$.
 - ☐ B OHM .
 - ☐ C OHM/M .
 - ☐ D OHM/M^2 .
- 20) THE RESISTIVITY OF A WIRE DEPENDS ON:
- ☐ A MATERIAL.
 - ☐ B LENGTH.
 - ☐ C AREA OF CROSS-SECTION.
 - ☐ D LENGTH, MATERIAL AND AREA OF CROSS-SECTION.
- 21) A WIRE OF LENGTH L AND CROSS-SECTIONAL AREA A HAS A RESISTIVITY ρ . DETERMINE WHICH OF THE FOLLOWING FORMULAS CAN BE USED TO CALCULATE THE RESISTANCE OF THE WIRE.
- ☐ A $R = \frac{\rho L}{A}$.
 - ☐ B $R = \frac{\rho A}{L}$.
 - ☐ C $R = \frac{L}{\rho A}$.
 - ☐ D $R = \frac{A}{\rho L}$.

- 22) ALL OF THE WIRES IN FIGURE 4 AT THE END OF THE TEXT ARE MADE OF THE SAME MATERIAL BUT ARE DIFFERENT SIZES. IDENTIFY THE WIRE WITH THE LOWEST RESISTANCE.

☐ A (B).
☐ B (A).
☐ C (C).
☐ D (D).

- 23) TWO COPPER WIRES HAVE THE SAME CROSS-SECTIONAL AREA BUT HAVE DIFFERENT LENGTHS. WIRE X HAS A LENGTH L AND WIRE Y HAS A LENGTH $2L$. THE RATIO BETWEEN THE RESISTANCE OF WIRE Y AND WIRE X IS:

☐ A $\frac{R_Y}{R_X} = \frac{2}{1}$.
☐ B $\frac{R_Y}{R_X} = \frac{1}{1}$.
☐ C $\frac{R_Y}{R_X} = \frac{1}{2}$.
☐ D $\frac{R_Y}{R_X} = \frac{1}{4}$.

- 24) TWO ALUMINUM WIRES HAVE THE SAME LENGTH AND DIFFERENT CROSS-SECTIONAL AREA. WIRE B HAS TWICE THE RADIUS OF THAT OF WIRE A . DETERMINE HOW THE RESISTANCE OF WIRE B COMPARES TO THE RESISTANCE OF WIRE A .

☐ A $\frac{R_B}{R_A} = \frac{1}{4}$.
☐ B $\frac{R_B}{R_A} = \frac{1}{1}$.
☐ C $\frac{R_B}{R_A} = \frac{1}{2}$.
☐ D $\frac{R_B}{R_A} = \frac{2}{1}$.

- 25) THE UNIT OF ELECTRIC POWER IS:

☐ A WATT.
☐ B AMPERE.
☐ C VOLT.
☐ D JOULE.

- 26) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

☐ A $D \cdot P$.
☐ B $D^2 \cdot P$.
☐ C $D \cdot P^2$.
☐ D D^2/P .

- 27) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

☐ A $D^2 \cdot F$.
☐ B $D \cdot F$.
☐ C $D \cdot F^2$.
☐ D D^2/F .

- 28) When a current I flows through a resistance R for time t the electrical energy spent is given by:

☐ A $I^2 R t$.
☐ B $I R t$.
☐ C $I R^2 t$.
☐ D $I^2 R/t$.

- 29) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

☐ A 30 J.
☐ B 60 J.
☐ C 15 J.
☐ D 120 J.

- 30) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the power dissipated in the resistor when the applied voltage is 5 V.

☐ A 15 W.
☐ B 5 W.
☐ C 10 W.
☐ D 20 W.

- 31) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN SERIES IS *true*.
- ☐ A THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
 - ☐ B THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ C THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ D THE TOTAL CURRENT THROUGH THE RESISTORS IS THE SUM OF THE CURRENT THROUGH EACH RESISTOR.
- 32) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN PARALLEL IS *true*.
- ☐ A THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ B THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
 - ☐ C THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ D THE TOTAL VOLTAGE ACROSS THE RESISTORS IS THE SUM OF THE VOLTAGE ACROSS EACH RESISTOR.
- 33) TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN PARALLEL. THE OVERALL RESISTANCE WILL BE:
- ☐ A $0\ \Omega$.
 - ☐ B $100\ \Omega$.
 - ☐ C $50\ \Omega$.
 - ☐ D $25\ \Omega$.
- 34) TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN SERIES. THE OVERALL RESISTANCE WILL BE:
- ☐ A $100\ \Omega$.
 - ☐ B $50\ \Omega$.
 - ☐ C $25\ \Omega$.
 - ☐ D $0\ \Omega$.
- 35) THREE RESISTORS $2\ \Omega$, $3\ \Omega$ AND $4\ \Omega$ ARE CONNECTED SO THAT THE EQUIVALENT RESISTANCE IS $9\ \Omega$. THE RESISTORS ARE CONNECTED:
- ☐ A ALL IN SERIES.
 - ☐ B ALL IN PARALLEL.
 - ☐ C $2\ \Omega$ AND $3\ \Omega$ IN PARALLEL AND THE COMBINATION IN SERIES WITH $4\ \Omega$.
 - ☐ D $2\ \Omega$ AND $3\ \Omega$ IN SERIES AND THE COMBINATION IN PARALLEL TO $4\ \Omega$.

- 36) IN FIGURE 5 AT THE END OF THE TEXT,
- A $3\ \Omega$, $6\ \Omega$ ARE IN PARALLEL AND $9\ \Omega$ IS IN SERIES.
 - B $6\ \Omega$, $3\ \Omega$ AND $9\ \Omega$ ARE IN SERIES.
 - C $9\ \Omega$ AND $6\ \Omega$ ARE IN PARALLEL AND THE COMBINATION IS IN SERIES WITH $3\ \Omega$.
 - D $3\ \Omega$, $6\ \Omega$ AND $9\ \Omega$ ARE IN PARALLEL.
- 37) IN FIGURE 6 AT THE END OF THE TEXT, THE RESISTANCE ACROSS AB IS:
- A $1\ \Omega$.
 - B $4\ \Omega$.
 - C $2\ \Omega$.
 - D $0.5\ \Omega$.
- 38) THREE EQUAL RESISTANCES WHEN COMBINED IN SERIES ARE EQUIVALENT TO $90\ \Omega$. THEIR EQUIVALENT RESISTANCE WHEN COMBINED IN PARALLEL WILL BE:
- A $10\ \Omega$.
 - B $270\ \Omega$.
 - C $30\ \Omega$.
 - D $810\ \Omega$.
- 39) TWO RESISTORS $R_1 = 3\ \Omega$ AND $R_2 = 6\ \Omega$ ARE CONNECTED IN PARALLEL. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- A $2\ \Omega$.
 - B $1\ \Omega$.
 - C $3\ \Omega$.
 - D $6\ \Omega$.
- 40) TWO RESISTORS $R_1 = 6\ \Omega$ AND $R_2 = 12\ \Omega$ ARE CONNECTED IN PARALLEL TO EACH OTHER AND IN SERIES TO $R_3 = 2\ \Omega$. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- A $6\ \Omega$.
 - B $1\ \Omega$.
 - C $3\ \Omega$.
 - D $2\ \Omega$.

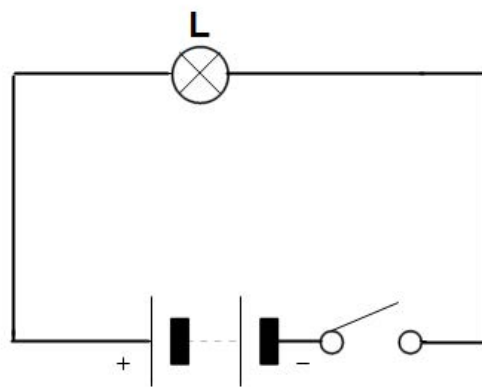


FIGURA 1

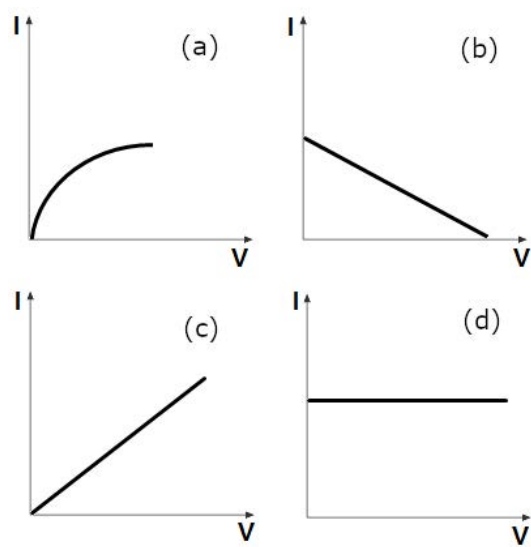


FIGURA 2

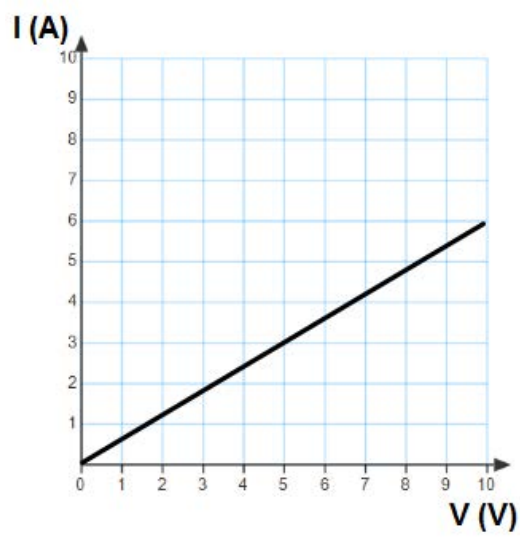


FIGURA 3

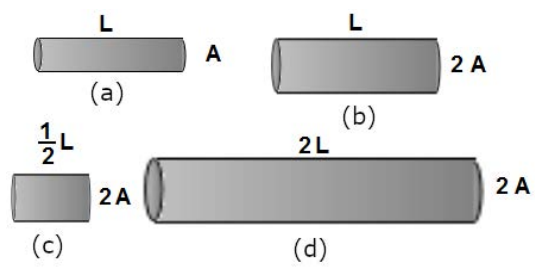


FIGURA 4

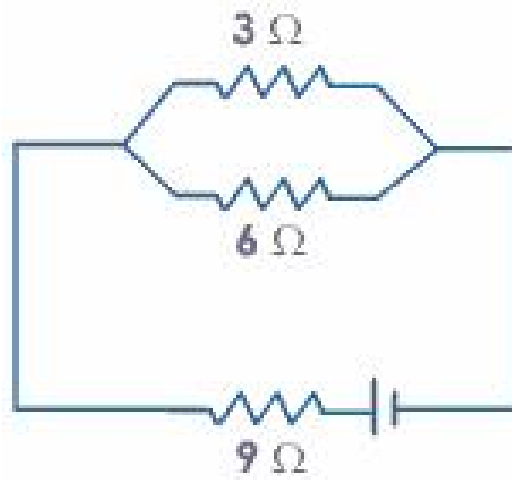


FIGURA 5

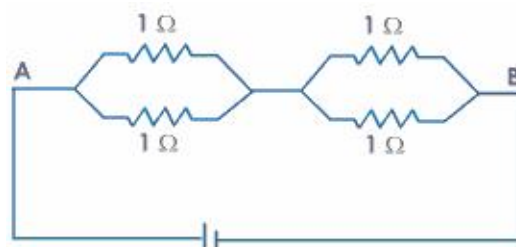


FIGURA 6

LICEO STATALE “NICCOLÒ MACHIAVELLI” DI ROMA
5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

VERSIONE ♡1

DATA CLASSE

ALUNNO

IL PUNTEGGIO PER OGNI RISPOSTA CORRETTA È DI 4 PUNTI, PER OGNI RISPOSTA OMESSA 1 PUNTO, PER OGNI RISPOSTA SBAGLIATA 0 PUNTI. LA DURATA DELLA VERIFICA È DI UN’ORA. SI SUGGERISCE DI RICOPIARE LE RISPOSTE NELLA TABELLA A SEGUIRE O IN CASO DI DIFFICOLTÀ NELLA COPIA SE NE SEGNALI L’ASSENZA.

TABELLA DELLE RISPOSTE									
1	2	3	4	5	6	7	8	9	10
11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40

- ① TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN PARALLEL. THE OVERALL RESISTANCE WILL BE:
- ☐ A $100\ \Omega$.
 - ☐ B $0\ \Omega$.
 - ☐ C $25\ \Omega$.
 - ☐ D $50\ \Omega$.

- ② THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 1. COMPUTE THE POWER DISSIPATED IN THE RESISTOR WHEN THE APPLIED VOLTAGE IS 5 V.

☐ A 5 W.
☐ B 10 W.
☐ C 20 W.
☐ D 15 W.

- ③ THE RESISTANCE OF AN ELECTRIC BULB DRAWING 1.2 A CURRENT AT 6.0 V IS:

☐ A 5 W.
☐ B 2 W.
☐ C 0.5 W.
☐ D 0.2 W.

- ④ THE UNIT OF CURRENT IS:

☐ A COULOMB.
☐ B AMPERE.
☐ C WATT.
☐ D VOLT.

- ⑤ IN FIGURE 2 AT THE END OF THE TEXT,

☐ A $6\ \Omega$, $3\ \Omega$ AND $9\ \Omega$ ARE IN SERIES.
☐ B $3\ \Omega$, $6\ \Omega$ AND Ω ARE IN PARALLEL.
☐ C $3\ \Omega$, $6\ \Omega$ ARE IN PARALLEL AND $9\ \Omega$ IS IN SERIES.
☐ D $9\ \Omega$ AND $6\ \Omega$ ARE IN PARALLEL AND THE COMBINATION IS IN SERIES WITH $3\ \Omega$.

- ⑥ TWO ALUMINUM WIRES HAVE THE SAME LENGTH AND DIFFERENT CROSS-SECTIONAL AREA. WIRE *B* HAS TWICE THE RADIUS OF THAT OF WIRE *A*. DETERMINE HOW THE RESISTANCE OF WIRE *B* COMPARES TO THE RESISTANCE OF WIRE *A*.

☐ A $\frac{R_B}{R_A} = \frac{1}{2}$.
☐ B $\frac{R_B}{R_A} = \frac{2}{1}$.
☐ C $\frac{R_B}{R_A} = \frac{1}{1}$.
☐ D $\frac{R_B}{R_A} = \frac{1}{4}$.

- 7) THREE RESISTORS $2\ \Omega$, $3\ \Omega$ AND $4\ \Omega$ ARE CONNECTED SO THAT THE EQUIVALENT RESISTANCE IS $9\ \Omega$. THE RESISTORS ARE CONNECTED:
- ☐ A $2\ \Omega$ AND $3\ \Omega$ IN SERIES AND THE COMBINATION IN PARALLEL TO $4\ \Omega$.
 - ☐ B ALL IN PARALLEL.
 - ☐ C ALL IN SERIES.
 - ☐ D $2\ \Omega$ AND $3\ \Omega$ IN PARALLEL AND THE COMBINATION IN SERIES WITH $4\ \Omega$.
- 8) THE UNIT OF RESISTIVITY IS:
- ☐ A OHM·M.
 - ☐ B OHM.
 - ☐ C OHM/M.
 - ☐ D OHM/M².
- 9) HEAT PRODUCED IN A CURRENT CARRYING WIRE IN 5s IS 60 J. THE SAME CURRENT IS PASSED THROUGH ANOTHER WIRE OF HALF THE RESISTANCE. THE HEAT PRODUCED IN 5 s WILL BE:
- ☐ A 60 J.
 - ☐ B 120 J.
 - ☐ C 30 J.
 - ☐ D 15 J.
- 10) TWO RESISTORS $R_1 = 6\ \Omega$ AND $R_2 = 12\ \Omega$ ARE CONNECTED IN PARALLEL TO EACH OTHER AND IN SERIES TO $R_2 = 2\ \Omega$. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- ☐ A $1\ \Omega$.
 - ☐ B $2\ \Omega$.
 - ☐ C $6\ \Omega$.
 - ☐ D $3\ \Omega$.
- 11) DETERMINE THE DIRECTION OF THE CONVENTIONAL CURRENT THROUGH THE LIGHT BULB IN THE CIRCUIT PRESENTED IN FIGURE 3 AT THE END OF THE TEXT.
- ☐ A TO THE RIGHT.
 - ☐ B DOWNWARD.
 - ☐ C TO THE LEFT.
 - ☐ D UPWARD.

- ⑫ THE WORK DONE IN MOVING A UNIT POSITIVE CHARGE ACROSS TWO POINTS IN AN ELECTRIC CIRCUIT IS A MEASURE OF:
- ☐ A CURRENT.
 - ☐ B POWER.
 - ☐ C RESISTANCE.
 - ☐ D POTENTIAL DIFFERENCE.
- ⑬ A 10 A CURRENT IS MAINTAINED IN A SIMPLE CIRCUIT. COMPUTE THE NET CHARGE THAT PASSES THROUGH ANY POINT IN THE CIRCUIT DURING A 1 MINUTE INTERVAL.
- ☐ A 400 C.
 - ☐ B 600 C.
 - ☐ C 500 C.
 - ☐ D 200 C.
- ⑭ TWO RESISTANCES OF 100 Ω AND ZERO OHM ARE CONNECTED IN SERIES. THE OVERALL RESISTANCE WILL BE:
- ☐ A 25 Ω .
 - ☐ B 100 Ω .
 - ☐ C 50 Ω .
 - ☐ D 0 Ω .
- ⑮ THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 1. COMPUTE THE RESISTANCE OF THE WIRE.
- ☐ A 0.4 Ω .
 - ☐ B 1.7 Ω .
 - ☐ C 1 Ω .
 - ☐ D 0.8 Ω .
- ⑯ DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN SERIES IS *true*.
- ☐ A THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ B THE TOTAL CURRENT THROUGH THE RESISTORS IS THE SUM OF THE CURRENT THROUGH EACH RESISTOR.
 - ☐ C THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ D THE CURRENT THROUGH EACH RESISTOR IS THE SAME.

- 17) IN FIGURE 4 AT THE END OF THE TEXT, THE RESISTANCE ACROSS AB IS:
- ☐ A $4\ \Omega$.
 - ☐ B $2\ \Omega$.
 - ☐ C $0.5\ \Omega$.
 - ☐ D $1\ \Omega$.
- 18) TWO COPPER WIRES HAVE THE SAME CROSS-SECTIONAL AREA BUT HAVE DIFFERENT LENGTHS. WIRE X HAS A LENGTH L AND WIRE Y HAS A LENGTH $2L$. THE RATIO BETWEEN THE RESISTANCE OF WIRE Y AND WIRE X IS:
- ☐ A $\frac{R_Y}{R_X} = \frac{1}{2}$.
 - ☐ B $\frac{R_Y}{R_X} = \frac{1}{1}$.
 - ☐ C $\frac{R_Y}{R_X} = \frac{1}{4}$.
 - ☐ D $\frac{R_Y}{R_X} = \frac{2}{1}$.
- 19) A POSITIVE CHARGE RELEASED FROM REST:
- ☐ A MOVES TOWARDS THE REGIONS OF HIGHER POTENTIAL.
 - ☐ B MOVES TOWARDS THE REGIONS OF EQUAL POTENTIAL.
 - ☐ C DOES NOT MOVE.
 - ☐ D MOVES TOWARDS THE REGIONS OF LOWER POTENTIAL.
- 20) THE AMOUNT OF CHARGE FLOWING THROUGH A CROSS-SECTIONAL AREA OF A WIRE PER UNIT OF TIME IS CALLED:
- ☐ A VOLTAGE.
 - ☐ B RESISTANCE.
 - ☐ C CURRENT.
 - ☐ D POWER.
- 21) ALL OF THE WIRES IN FIGURE 5 AT THE END OF THE TEXT ARE MADE OF THE SAME MATERIAL BUT ARE DIFFERENT SIZES. IDENTIFY THE WIRE WITH THE LOWEST RESISTANCE.
- ☐ A (A).
 - ☐ B (B).
 - ☐ C (D).
 - ☐ D (C).

- 22) WHEN THERE IS AN ELECTRIC CURRENT PASSING THROUGH A WIRE, THE PARTICLES MOVING ARE:
- ☐ A IONS.
 - ☐ B ATOMS.
 - ☐ C PROTONS.
 - ☐ D ELECTRONS.
- 23) COMPLETE THE FOLLOWING STATEMENT: "THE ELECTROMOTIVE FORCE IS:
- ☐ A THE MAXIMUM ELECTRIC POTENTIAL ENERGY STORED WITHIN A BATTERY".
 - ☐ B THE MAXIMUM POTENTIAL DIFFERENCE BETWEEN THE TERMINALS OF A BATTERY".
 - ☐ C THE FORCE THAT ACCELERATES ELECTRONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
 - ☐ D THE FORCE THAT ACCELERATES PROTONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
- 24) JOULE/COULOMB IS SAME AS:
- ☐ A OHM.
 - ☐ B AMPERE.
 - ☐ C VOLT.
 - ☐ D WATT.
- 25) IF D IS THE INTENSITY OF CURRENT CIRCULATING IN A RESISTOR WITH RESISTANCE F , THE POWER DISSIPATED BY THE RESISTOR IS DESCRIBED BY THE FORMULA:
- ☐ A $D \cdot F^2$.
 - ☐ B $D \cdot F$.
 - ☐ C D^2/F .
 - ☐ D $D^2 \cdot F$.
- 26) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN PARALLEL IS *true*.
- ☐ A THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
 - ☐ B THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ C THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ D THE TOTAL VOLTAGE ACROSS THE RESISTORS IS THE SUM OF THE VOLTAGE ACROSS EACH RESISTOR.

- 27) DETERMINE WHICH OF THE FOLLOWING STATEMENTS DOES NOT REPRESENT OHM'S LAW.
- ☐ A CURRENT = RESISTANCE \times POTENTIAL DIFFERENCE.
 - ☐ B CURRENT / POTENTIAL DIFFERENCE = CONSTANT.
 - ☐ C POTENTIAL DIFFERENCE / CURRENT = CONSTANT.
 - ☐ D POTENTIAL DIFFERENCE = CURRENT \times RESISTANCE.
- 28) THE POTENTIAL DIFFERENCE REQUIRED TO PASS A CURRENT 0.2 A IN A WIRE OF RESISTANCE 20 Ω IS:
- ☐ A 100 V.
 - ☐ B 40 V.
 - ☐ C 1 V.
 - ☐ D 4 V.
- 29) THE UNIT OF ELECTRIC POWER IS:
- ☐ A AMPERE.
 - ☐ B VOLT.
 - ☐ C WATT.
 - ☐ D JOULE.
- 30) COMPUTE THE NUMBER OF ELECTRONS FLOWING THROUGH A BATTERY THAT DELIVERS A CURRENT OF 3.0 A FOR 12 S.
- ☐ A 36.
 - ☐ B 6.4×10^{18} .
 - ☐ C 4.8×10^{15} .
 - ☐ D 2.2×10^{20} .
- 31) OHM'S LAW RELATES POTENTIAL DIFFERENCE WITH:
- ☐ A ENERGY.
 - ☐ B TIME.
 - ☐ C POWER.
 - ☐ D CURRENT.

- 32) A BATTERY IS USED TO:
- ☐ A MEASURE ELECTRIC POTENTIAL.
 - ☐ B SAFEGUARD AGAINST SHORT-CIRCUIT.
 - ☐ C MEASURE ELECTRIC CURRENT.
 - ☐ D MAINTAIN A POTENTIAL DIFFERENCE.
- 33) THE CURRENT IN A WIRE:
- ☐ A DEPENDS ONLY ON THE POTENTIAL DIFFERENCE APPLIED.
 - ☐ B DOES NOT DEPEND ON RESISTANCE AND POTENTIAL DIFFERENCE.
 - ☐ C DEPENDS ON BOTH RESISTANCE AND POTENTIAL DIFFERENCE.
 - ☐ D DEPENDS ONLY ON THE RESISTANCE OF THE WIRE.
- 34) DETERMINE WHICH OF THE GRAPHS IN FIGURE 6 AT THE END OF THE TEXT REPRESENTS OHM'S LAW FOR A SOLID CONDUCTOR.
- ☐ A (B).
 - ☐ B (A).
 - ☐ C (C).
 - ☐ D (D).
- 35) TWO RESISTORS $R_1 = 3\ \Omega$ AND $R_2 = 6\ \Omega$ ARE CONNECTED IN PARALLEL. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- ☐ A $1\ \Omega$.
 - ☐ B $3\ \Omega$.
 - ☐ C $2\ \Omega$.
 - ☐ D $6\ \Omega$.
- 36) THE RESISTIVITY OF A WIRE DEPENDS ON:
- ☐ A LENGTH.
 - ☐ B AREA OF CROSS-SECTION.
 - ☐ C LENGTH, MATERIAL AND AREA OF CROSS-SECTION.
 - ☐ D MATERIAL.

- 37) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

☐ A D^2/P .

☐ B $D^2 \cdot P$.

☐ C $D \cdot P^2$.

☐ D $D \cdot P$.

- 38) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

☐ A $R = \frac{A}{\rho L}$.

☐ B $R = \frac{\rho L}{A}$.

☐ C $R = \frac{\rho A}{L}$.

☐ D $R = \frac{L}{\rho A}$.

- 39) When a current I flows through a resistance R for time t the electrical energy spent is given by:

☐ A IRt .

☐ B IR^2t .

☐ C I^2R/t .

☐ D I^2Rt .

- 40) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:

☐ A 30Ω .

☐ B 270Ω .

☐ C 810Ω .

☐ D 10Ω .

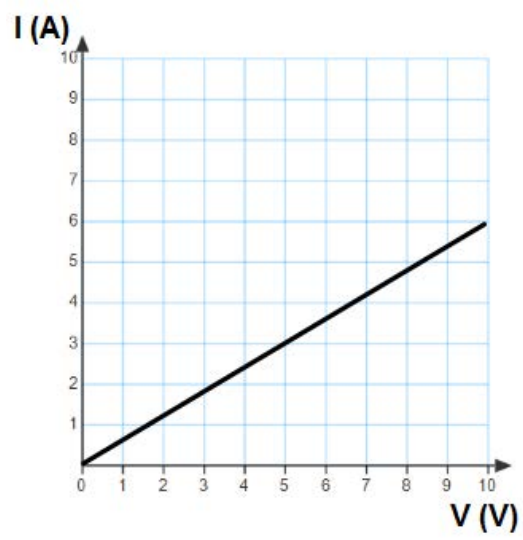


FIGURA 1

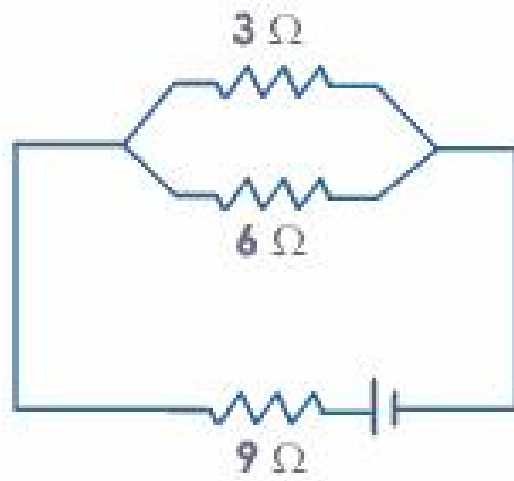


FIGURA 2

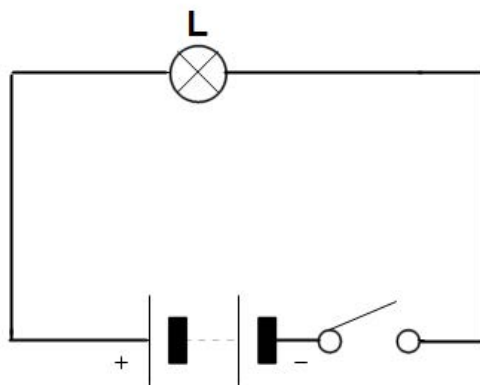


FIGURA 3

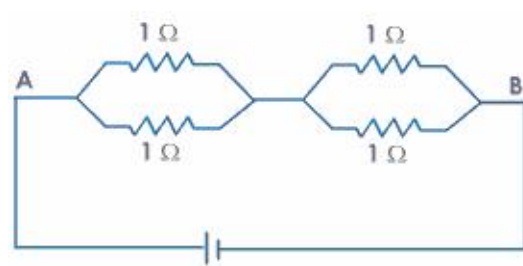


FIGURA 4

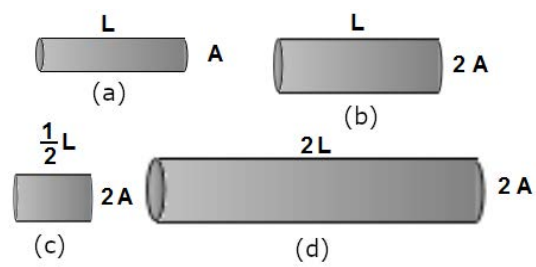


FIGURA 5

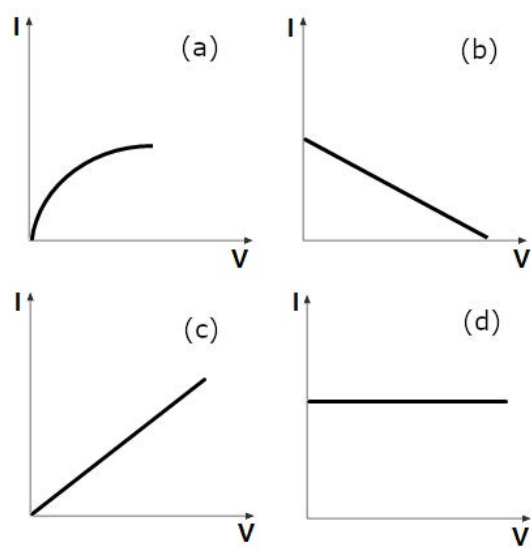


FIGURA 6

LICEO STATALE “NICCOLÒ MACHIAVELLI” DI ROMA
5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

VERSIONE ♡2

DATA CLASSE

ALUNNO

IL PUNTEGGIO PER OGNI RISPOSTA CORRETTA È DI 4 PUNTI, PER OGNI RISPOSTA OMESSA 1 PUNTO, PER OGNI RISPOSTA SBAGLIATA 0 PUNTI. LA DURATA DELLA VERIFICA È DI UN’ORA. SI SUGGERISCE DI RICOPIARE LE RISPOSTE NELLA TABELLA A SEGUIRE O IN CASO DI DIFFICOLTÀ NELLA COPIA SE NE SEGNALI L’ASSENZA.

TABELLA DELLE RISPOSTE									
1	2	3	4	5	6	7	8	9	10
11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40

- ① A WIRE OF LENGTH L AND CROSS-SECTIONAL AREA A HAS A RESISTIVITY ρ . DETERMINE WHICH OF THE FOLLOWING FORMULAS CAN BE USED TO CALCULATE THE RESISTANCE OF THE WIRE.

☐ A $R = \frac{\rho L}{A}$.

☐ B $R = \frac{\rho A}{L}$.

☐ C $R = \frac{L}{\rho A}$.

☐ D $R = \frac{A}{\rho L}$.

② DETERMINE THE DIRECTION OF THE CONVENTIONAL CURRENT THROUGH THE LIGHT BULB IN THE CIRCUIT PRESENTED IN FIGURE 1 AT THE END OF THE TEXT.

- ☐ A TO THE LEFT.
- ☐ B TO THE RIGHT.
- ☐ C DOWNWARD.
- ☐ D UPWARD.

③ IF D IS THE INTENSITY OF CURRENT CIRCULATING IN A CONDUCTOR AND P IS THE VOLTAGE ACROSS THE CONDUCTOR, THE POWER DISSIPATED IS DESCRIBED BY THE FORMULA:

- ☐ A $D \cdot P^2$.
- ☐ B $D \cdot P$.
- ☐ C D^2/P .
- ☐ D $D^2 \cdot P$.

④ IN FIGURE 2 AT THE END OF THE TEXT,

- ☐ A $9\ \Omega$ AND $6\ \Omega$ ARE IN PARALLEL AND THE COMBINATION IS IN SERIES WITH $3\ \Omega$.
- ☐ B $6\ \Omega$, $3\ \Omega$ AND $9\ \Omega$ ARE IN SERIES.
- ☐ C $3\ \Omega$, $6\ \Omega$ AND $9\ \Omega$ ARE IN PARALLEL.
- ☐ D $3\ \Omega$, $6\ \Omega$ ARE IN PARALLEL AND $9\ \Omega$ IS IN SERIES.

⑤ A BATTERY IS USED TO:

- ☐ A MEASURE ELECTRIC POTENTIAL.
- ☐ B SAFEGUARD AGAINST SHORT-CIRCUIT.
- ☐ C MAINTAIN A POTENTIAL DIFFERENCE.
- ☐ D MEASURE ELECTRIC CURRENT.

⑥ THE UNIT OF CURRENT IS:

- ☐ A COULOMB.
- ☐ B AMPERE.
- ☐ C VOLT.
- ☐ D WATT.

- ⑦ A POSITIVE CHARGE RELEASED FROM REST:
- ☐ A MOVES TOWARDS THE REGIONS OF HIGHER POTENTIAL.
 - ☐ B MOVES TOWARDS THE REGIONS OF EQUAL POTENTIAL.
 - ☐ C DOES NOT MOVE.
 - ☐ D MOVES TOWARDS THE REGIONS OF LOWER POTENTIAL.
- ⑧ THREE EQUAL RESISTANCES WHEN COMBINED IN SERIES ARE EQUIVALENT TO $90\ \Omega$. THEIR EQUIVALENT RESISTANCE WHEN COMBINED IN PARALLEL WILL BE:
- ☐ A $270\ \Omega$.
 - ☐ B $810\ \Omega$.
 - ☐ C $10\ \Omega$.
 - ☐ D $30\ \Omega$.
- ⑨ IF D IS THE INTENSITY OF CURRENT CIRCULATING IN A RESISTOR WITH RESISTANCE F , THE POWER DISSIPATED BY THE RESISTOR IS DESCRIBED BY THE FORMULA:
- ☐ A $D^2 \cdot F$.
 - ☐ B $D \cdot F^2$.
 - ☐ C D^2/F .
 - ☐ D $D \cdot F$.
- ⑩ THE RESISTANCE OF AN ELECTRIC BULB DRAWING $1.2\ \text{A}$ CURRENT AT $6.0\ \text{V}$ IS:
- ☐ A $2\ \text{W}$.
 - ☐ B $0.5\ \text{W}$.
 - ☐ C $0.2\ \text{W}$.
 - ☐ D $5\ \text{W}$.
- ⑪ THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 3. COMPUTE THE RESISTANCE OF THE WIRE.
- ☐ A $0.8\ \Omega$.
 - ☐ B $0.4\ \Omega$.
 - ☐ C $1.7\ \Omega$.
 - ☐ D $1\ \Omega$.

- 12) DETERMINE WHICH OF THE GRAPHS IN FIGURE 4 AT THE END OF THE TEXT REPRESENTS OHM'S LAW FOR A SOLID CONDUCTOR.
- ☐ A (C).
 - ☐ B (D).
 - ☐ C (A).
 - ☐ D (B).
- 13) WHEN A CURRENT I FLOWS THROUGH A RESISTANCE R FOR TIME t THE ELECTRICAL ENERGY SPENT IS GIVEN BY:
- ☐ A I^2Rt .
 - ☐ B IRt .
 - ☐ C IR^2t .
 - ☐ D I^2R/t .
- 14) TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN PARALLEL. THE OVERALL RESISTANCE WILL BE:
- ☐ A $50\ \Omega$.
 - ☐ B $0\ \Omega$.
 - ☐ C $25\ \Omega$.
 - ☐ D $100\ \Omega$.
- 15) THE AMOUNT OF CHARGE FLOWING THROUGH A CROSS-SECTIONAL AREA OF A WIRE PER UNIT OF TIME IS CALLED:
- ☐ A VOLTAGE.
 - ☐ B POWER.
 - ☐ C RESISTANCE.
 - ☐ D CURRENT.
- 16) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN SERIES IS *true*.
- ☐ A THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ B THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
 - ☐ C THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ D THE TOTAL CURRENT THROUGH THE RESISTORS IS THE SUM OF THE CURRENT THROUGH EACH RESISTOR.

- 17) IN FIGURE 5 AT THE END OF THE TEXT, THE RESISTANCE ACROSS AB IS:
- ☐ A $4\ \Omega$.
 - ☐ B $2\ \Omega$.
 - ☐ C $1\ \Omega$.
 - ☐ D $0.5\ \Omega$.
- 18) THREE RESISTORS $2\ \Omega$, $3\ \Omega$ AND $4\ \Omega$ ARE CONNECTED SO THAT THE EQUIVALENT RESISTANCE IS $9\ \Omega$. THE RESISTORS ARE CONNECTED:
- ☐ A $2\ \Omega$ AND $3\ \Omega$ IN SERIES AND THE COMBINATION IN PARALLEL TO $4\ \Omega$.
 - ☐ B ALL IN PARALLEL.
 - ☐ C $2\ \Omega$ AND $3\ \Omega$ IN PARALLEL AND THE COMBINATION IN SERIES WITH $4\ \Omega$.
 - ☐ D ALL IN SERIES.
- 19) HEAT PRODUCED IN A CURRENT CARRYING WIRE IN 5S IS 60 J. THE SAME CURRENT IS PASSED THROUGH ANOTHER WIRE OF HALF THE RESISTANCE. THE HEAT PRODUCED IN 5 S WILL BE:
- ☐ A 120 J.
 - ☐ B 15 J.
 - ☐ C 30 J.
 - ☐ D 60 J.
- 20) THE POTENTIAL DIFFERENCE REQUIRED TO PASS A CURRENT 0.2 A IN A WIRE OF RESISTANCE $20\ \Omega$ IS:
- ☐ A 40 V.
 - ☐ B 1 V.
 - ☐ C 100 V.
 - ☐ D 4 V.
- 21) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN PARALLEL IS *true*.
- ☐ A THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ B THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ C THE TOTAL VOLTAGE ACROSS THE RESISTORS IS THE SUM OF THE VOLTAGE ACROSS EACH RESISTOR.
 - ☐ D THE CURRENT THROUGH EACH RESISTOR IS THE SAME.

22) OHM'S LAW RELATES POTENTIAL DIFFERENCE WITH:

- ☐ A POWER.
- ☐ B CURRENT.
- ☐ C ENERGY.
- ☐ D TIME.

23) THE UNIT OF RESISTIVITY IS:

- ☐ A OHM.
- ☐ B OHM/M².
- ☐ C OHM·M.
- ☐ D OHM/M.

24) TWO COPPER WIRES HAVE THE SAME CROSS-SECTIONAL AREA BUT HAVE DIFFERENT LENGTHS. WIRE *X* HAS A LENGTH *L* AND WIRE *Y* HAS A LENGTH *2L*. THE RATIO BETWEEN THE RESISTANCE OF WIRE *Y* AND WIRE *X* IS:

- ☐ A $\frac{R_Y}{R_X} = \frac{1}{2}$.
- ☐ B $\frac{R_Y}{R_X} = \frac{2}{1}$.
- ☐ C $\frac{R_Y}{R_X} = \frac{1}{4}$.
- ☐ D $\frac{R_Y}{R_X} = \frac{1}{1}$.

25) JOULE/COULOMB IS SAME AS:

- ☐ A WATT.
- ☐ B AMPERE.
- ☐ C OHM.
- ☐ D VOLT.

26) A 10 A CURRENT IS MAINTAINED IN A SIMPLE CIRCUIT. COMPUTE THE NET CHARGE THAT PASSES THROUGH ANY POINT IN THE CIRCUIT DURING A 1 MINUTE INTERVAL.

- ☐ A 200 C.
- ☐ B 600 C.
- ☐ C 400 C.
- ☐ D 500 C.

- 27) COMPLETE THE FOLLOWING STATEMENT: "THE ELECTROMOTIVE FORCE IS:
- A THE MAXIMUM POTENTIAL DIFFERENCE BETWEEN THE TERMINALS OF A BATTERY".
 - B THE FORCE THAT ACCELERATES PROTONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
 - C THE MAXIMUM ELECTRIC POTENTIAL ENERGY STORED WITHIN A BATTERY".
 - D THE FORCE THAT ACCELERATES ELECTRONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
- 28) THE WORK DONE IN MOVING A UNIT POSITIVE CHARGE ACROSS TWO POINTS IN AN ELECTRIC CIRCUIT IS A MEASURE OF:
- A CURRENT.
 - B RESISTANCE.
 - C POTENTIAL DIFFERENCE.
 - D POWER.
- 29) TWO RESISTORS $R_1 = 3\ \Omega$ AND $R_2 = 6\ \Omega$ ARE CONNECTED IN PARALLEL. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- A $3\ \Omega$.
 - B $6\ \Omega$.
 - C $1\ \Omega$.
 - D $2\ \Omega$.
- 30) TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN SERIES. THE OVERALL RESISTANCE WILL BE:
- A $100\ \Omega$.
 - B $0\ \Omega$.
 - C $50\ \Omega$.
 - D $25\ \Omega$.
- 31) WHEN THERE IS AN ELECTRIC CURRENT PASSING THROUGH A WIRE, THE PARTICLES MOVING ARE:
- A IONS.
 - B ATOMS.
 - C ELECTRONS.
 - D PROTONS.

- 32) COMPUTE THE NUMBER OF ELECTRONS FLOWING THROUGH A BATTERY THAT DELIVERS A CURRENT OF 3.0 A FOR 12 S.
- A 4.8×10^{15} .
 - B 2.2×10^{20} .
 - C 36.
 - D 6.4×10^{18} .
- 33) THE CURRENT IN A WIRE:
- A DEPENDS ONLY ON THE POTENTIAL DIFFERENCE APPLIED.
 - B DOES NOT DEPEND ON RESISTANCE AND POTENTIAL DIFFERENCE.
 - C DEPENDS ON BOTH RESISTANCE AND POTENTIAL DIFFERENCE.
 - D DEPENDS ONLY ON THE RESISTANCE OF THE WIRE.
- 34) ALL OF THE WIRES IN FIGURE 6 AT THE END OF THE TEXT ARE MADE OF THE SAME MATERIAL BUT ARE DIFFERENT SIZES. IDENTIFY THE WIRE WITH THE LOWEST RESISTANCE.
- A (A).
 - B (D).
 - C (B).
 - D (C).
- 35) DETERMINE WHICH OF THE FOLLOWING STATEMENTS DOES NOT REPRESENT OHM'S LAW.
- A CURRENT / POTENTIAL DIFFERENCE = CONSTANT.
 - B CURRENT = RESISTANCE \times POTENTIAL DIFFERENCE.
 - C POTENTIAL DIFFERENCE = CURRENT \times RESISTANCE.
 - D POTENTIAL DIFFERENCE / CURRENT = CONSTANT.
- 36) THE UNIT OF ELECTRIC POWER IS:
- A WATT.
 - B VOLT.
 - C AMPERE.
 - D JOULE.

- 37) TWO RESISTORS $R_1 = 6\ \Omega$ AND $R_2 = 12\ \Omega$ ARE CONNECTED IN PARALLEL TO EACH OTHER AND IN SERIES TO $R_3 = 2\ \Omega$. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.

☐ A $3\ \Omega$.
☐ B $6\ \Omega$.
☐ C $2\ \Omega$.
☐ D $1\ \Omega$.

- 38) TWO ALUMINUM WIRES HAVE THE SAME LENGTH AND DIFFERENT CROSS-SECTIONAL AREA. WIRE B HAS TWICE THE RADIUS OF THAT OF WIRE A . DETERMINE HOW THE RESISTANCE OF WIRE B COMPARES TO THE RESISTANCE OF WIRE A .

☐ A $\frac{R_B}{R_A} = \frac{1}{1}$.
☐ B $\frac{R_B}{R_A} = \frac{1}{2}$.
☐ C $\frac{R_B}{R_A} = \frac{2}{1}$.
☐ D $\frac{R_B}{R_A} = \frac{1}{4}$.

- 39) THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 3. COMPUTE THE POWER DISSIPATED IN THE RESISTOR WHEN THE APPLIED VOLTAGE IS $5\ \text{V}$.

☐ A $20\ \text{W}$.
☐ B $5\ \text{W}$.
☐ C $10\ \text{W}$.
☐ D $15\ \text{W}$.

- 40) THE RESISTIVITY OF A WIRE DEPENDS ON:

☐ A AREA OF CROSS-SECTION.
☐ B LENGTH.
☐ C LENGTH, MATERIAL AND AREA OF CROSS-SECTION.
☐ D MATERIAL.

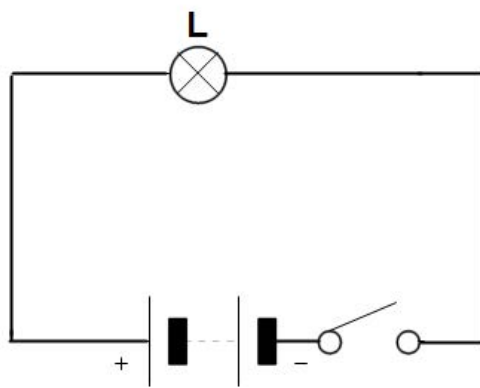


FIGURA 1

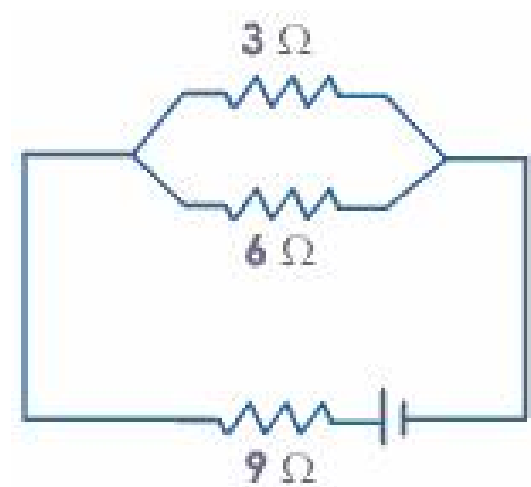


FIGURA 2

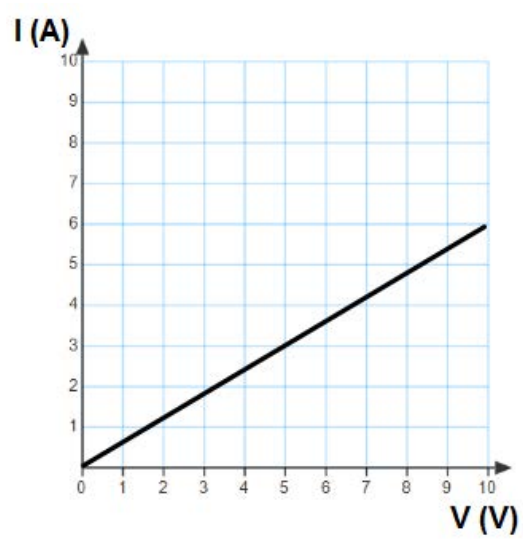


FIGURA 3

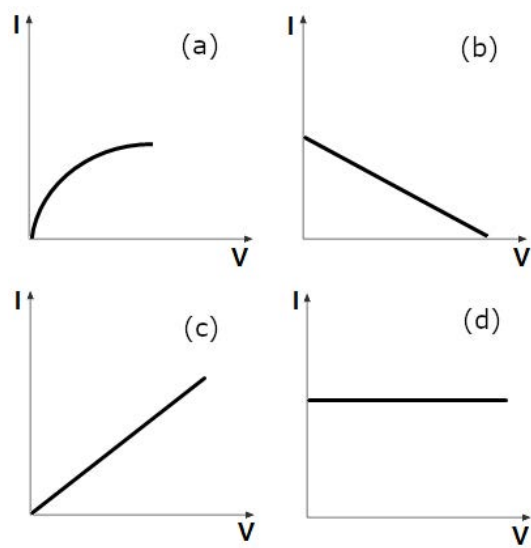


FIGURA 4

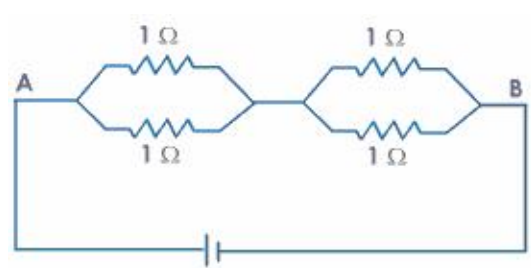


FIGURA 5

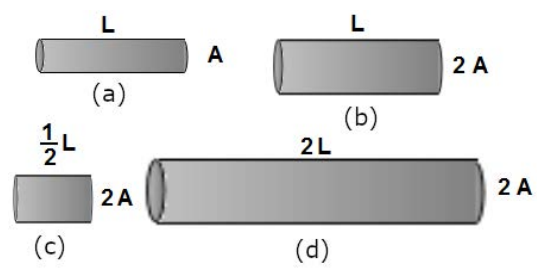


FIGURA 6

LICEO STATALE “NICCOLÒ MACHIAVELLI” DI ROMA
5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

VERSIONE ♡3

DATA CLASSE

ALUNNO

IL PUNTEGGIO PER OGNI RISPOSTA CORRETTA È DI 4 PUNTI, PER OGNI RISPOSTA OMESSA 1 PUNTO, PER OGNI RISPOSTA SBAGLIATA 0 PUNTI. LA DURATA DELLA VERIFICA È DI UN’ORA. SI SUGGERISCE DI RICOPIARE LE RISPOSTE NELLA TABELLA A SEGUIRE O IN CASO DI DIFFICOLTÀ NELLA COPIA SE NE SEGNALI L’ASSENZA.

TABELLA DELLE RISPOSTE									
1	2	3	4	5	6	7	8	9	10
11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40

- ① TWO RESISTORS $R_1 = 3 \, \Omega$ AND $R_2 = 6 \, \Omega$ ARE CONNECTED IN PARALLEL. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- ☐ A 6 Ω .
- ☐ B 2 Ω .
- ☐ C 3 Ω .
- ☐ D 1 Ω .

② THE RESISTANCE OF AN ELECTRIC BULB DRAWING 1.2 A CURRENT AT 6.0 V IS:

☐ A 0.5 W.

☐ B 5 W.

☐ C 0.2 W.

☐ D 2 W.

③ THE AMOUNT OF CHARGE FLOWING THROUGH A CROSS-SECTIONAL AREA OF A WIRE PER UNIT OF TIME IS CALLED:

☐ A VOLTAGE.

☐ B CURRENT.

☐ C POWER.

☐ D RESISTANCE.

④ IN FIGURE 1 AT THE END OF THE TEXT, THE RESISTANCE ACROSS AB IS:

☐ A 1 Ω .

☐ B 4 Ω .

☐ C 0.5 Ω .

☐ D 2 Ω .

⑤ THREE EQUAL RESISTANCES WHEN COMBINED IN SERIES ARE EQUIVALENT TO 90 Ω . THEIR EQUIVALENT RESISTANCE WHEN COMBINED IN PARALLEL WILL BE:

☐ A 10 Ω .

☐ B 270 Ω .

☐ C 810 Ω .

☐ D 30 Ω .

⑥ OHM'S LAW RELATES POTENTIAL DIFFERENCE WITH:

☐ A CURRENT.

☐ B ENERGY.

☐ C TIME.

☐ D POWER.

- 7 DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN SERIES IS *true*.
- ☐ A THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ B THE TOTAL CURRENT THROUGH THE RESISTORS IS THE SUM OF THE CURRENT THROUGH EACH RESISTOR.
 - ☐ C THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ D THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
- 8 THE POTENTIAL DIFFERENCE REQUIRED TO PASS A CURRENT 0.2 A IN A WIRE OF RESISTANCE 20 Ω IS:
- ☐ A 40 V.
 - ☐ B 100 V.
 - ☐ C 4 V.
 - ☐ D 1 V.
- 9 A WIRE OF LENGTH L AND CROSS-SECTIONAL AREA A HAS A RESISTIVITY ρ . DETERMINE WHICH OF THE FOLLOWING FORMULAS CAN BE USED TO CALCULATE THE RESISTANCE OF THE WIRE.
- ☐ A $R = \frac{A}{\rho L}$.
 - ☐ B $R = \frac{\rho L}{A}$.
 - ☐ C $R = \frac{L}{\rho A}$.
 - ☐ D $R = \frac{\rho A}{L}$.
- 10 THREE RESISTORS 2 Ω , 3 Ω AND 4 Ω ARE CONNECTED SO THAT THE EQUIVALENT RESISTANCE IS 9 Ω . THE RESISTORS ARE CONNECTED:
- ☐ A ALL IN PARALLEL.
 - ☐ B 2 Ω AND 3 Ω IN SERIES AND THE COMBINATION IN PARALLEL TO 4 Ω .
 - ☐ C 2 Ω AND 3 Ω IN PARALLEL AND THE COMBINATION IN SERIES WITH 4 Ω .
 - ☐ D ALL IN SERIES.
- 11 THE UNIT OF CURRENT IS:
- ☐ A AMPERE.
 - ☐ B COULOMB.
 - ☐ C VOLT.
 - ☐ D WATT.

- ⑫ DETERMINE WHICH OF THE GRAPHS IN FIGURE 2 AT THE END OF THE TEXT REPRESENTS OHM'S LAW FOR A SOLID CONDUCTOR.
- ☐ A (A).
 - ☐ B (C).
 - ☐ C (D).
 - ☐ D (B).
- ⑬ THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 3. COMPUTE THE POWER DISSIPATED IN THE RESISTOR WHEN THE APPLIED VOLTAGE IS 5 V.
- ☐ A 10 W.
 - ☐ B 5 W.
 - ☐ C 20 W.
 - ☐ D 15 W.
- ⑭ DETERMINE WHICH OF THE FOLLOWING STATEMENTS DOES NOT REPRESENT OHM'S LAW.
- ☐ A POTENTIAL DIFFERENCE / CURRENT = CONSTANT.
 - ☐ B CURRENT / POTENTIAL DIFFERENCE = CONSTANT.
 - ☐ C POTENTIAL DIFFERENCE = CURRENT \times RESISTANCE.
 - ☐ D CURRENT = RESISTANCE \times POTENTIAL DIFFERENCE.
- ⑮ A POSITIVE CHARGE RELEASED FROM REST:
- ☐ A MOVES TOWARDS THE REGIONS OF EQUAL POTENTIAL.
 - ☐ B MOVES TOWARDS THE REGIONS OF LOWER POTENTIAL.
 - ☐ C MOVES TOWARDS THE REGIONS OF HIGHER POTENTIAL.
 - ☐ D DOES NOT MOVE.
- ⑯ IF D IS THE INTENSITY OF CURRENT CIRCULATING IN A CONDUCTOR AND P IS THE VOLTAGE ACROSS THE CONDUCTOR, THE POWER DISSIPATED IS DESCRIBED BY THE FORMULA:
- ☐ A $D^2 \cdot P$.
 - ☐ B $D \cdot P^2$.
 - ☐ C D^2/P .
 - ☐ D $D \cdot P$.

- ①⑦ WHEN A CURRENT I FLOWS THROUGH A RESISTANCE R FOR TIME t THE ELECTRICAL ENERGY SPENT IS GIVEN BY:
- ☐ A IR^2t .
 - ☐ B I^2R/t .
 - ☐ C IRt .
 - ☐ D I^2Rt .
- ①⑧ WHEN THERE IS AN ELECTRIC CURRENT PASSING THROUGH A WIRE, THE PARTICLES MOVING ARE:
- ☐ A ATOMS.
 - ☐ B ELECTRONS.
 - ☐ C IONS.
 - ☐ D PROTONS.
- ①⑨ A BATTERY IS USED TO:
- ☐ A SAFEGUARD AGAINST SHORT-CIRCUIT.
 - ☐ B MEASURE ELECTRIC CURRENT.
 - ☐ C MEASURE ELECTRIC POTENTIAL.
 - ☐ D MAINTAIN A POTENTIAL DIFFERENCE.
- ②① DETERMINE THE DIRECTION OF THE CONVENTIONAL CURRENT THROUGH THE LIGHT BULB IN THE CIRCUIT PRESENTED IN FIGURE 4 AT THE END OF THE TEXT.
- ☐ A UPWARD.
 - ☐ B TO THE RIGHT.
 - ☐ C DOWNWARD.
 - ☐ D TO THE LEFT.
- ②① IN FIGURE 5 AT THE END OF THE TEXT,
- ☐ A $6\ \Omega$, $3\ \Omega$ AND $9\ \Omega$ ARE IN SERIES.
 - ☐ B $3\ \Omega$, $6\ \Omega$ AND Ω ARE IN PARALLEL.
 - ☐ C $9\ \Omega$ AND $6\ \Omega$ ARE IN PARALLEL AND THE COMBINATION IS IN SERIES WITH $3\ \Omega$.
 - ☐ D $3\ \Omega$, $6\ \Omega$ ARE IN PARALLEL AND $9\ \Omega$ IS IN SERIES.

- ②② COMPUTE THE NUMBER OF ELECTRONS FLOWING THROUGH A BATTERY THAT DELIVERS A CURRENT OF 3.0 A FOR 12 S.
- ☐ A 2.2×10^{20} .
 - ☐ B 4.8×10^{15} .
 - ☐ C 36.
 - ☐ D 6.4×10^{18} .
- ②③ IF D IS THE INTENSITY OF CURRENT CIRCULATING IN A RESISTOR WITH RESISTANCE F , THE POWER DISSIPATED BY THE RESISTOR IS DESCRIBED BY THE FORMULA:
- ☐ A $D \cdot F^2$.
 - ☐ B D^2/F .
 - ☐ C $D^2 \cdot F$.
 - ☐ D $D \cdot F$.
- ②④ A 10 A CURRENT IS MAINTAINED IN A SIMPLE CIRCUIT. COMPUTE THE NET CHARGE THAT PASSES THROUGH ANY POINT IN THE CIRCUIT DURING A 1 MINUTE INTERVAL.
- ☐ A 500 C.
 - ☐ B 600 C.
 - ☐ C 200 C.
 - ☐ D 400 C.
- ②⑤ THE CURRENT IN A WIRE:
- ☐ A DEPENDS ONLY ON THE POTENTIAL DIFFERENCE APPLIED.
 - ☐ B DEPENDS ON BOTH RESISTANCE AND POTENTIAL DIFFERENCE.
 - ☐ C DOES NOT DEPEND ON RESISTANCE AND POTENTIAL DIFFERENCE.
 - ☐ D DEPENDS ONLY ON THE RESISTANCE OF THE WIRE.
- ②⑥ HEAT PRODUCED IN A CURRENT CARRYING WIRE IN 5S IS 60 J. THE SAME CURRENT IS PASSED THROUGH ANOTHER WIRE OF HALF THE RESISTANCE. THE HEAT PRODUCED IN 5 S WILL BE:
- ☐ A 15 J.
 - ☐ B 120 J.
 - ☐ C 60 J.
 - ☐ D 30 J.

- 27) THE UNIT OF ELECTRIC POWER IS:
- ☐ A WATT.
 - ☐ B JOULE.
 - ☐ C VOLT.
 - ☐ D AMPERE.
- 28) THE WORK DONE IN MOVING A UNIT POSITIVE CHARGE ACROSS TWO POINTS IN AN ELECTRIC CIRCUIT IS A MEASURE OF:
- ☐ A RESISTANCE.
 - ☐ B POWER.
 - ☐ C CURRENT.
 - ☐ D POTENTIAL DIFFERENCE.
- 29) TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN PARALLEL. THE OVERALL RESISTANCE WILL BE:
- ☐ A $50\ \Omega$.
 - ☐ B $25\ \Omega$.
 - ☐ C $100\ \Omega$.
 - ☐ D $0\ \Omega$.
- 30) ALL OF THE WIRES IN FIGURE 6 AT THE END OF THE TEXT ARE MADE OF THE SAME MATERIAL BUT ARE DIFFERENT SIZES. IDENTIFY THE WIRE WITH THE LOWEST RESISTANCE.
- ☐ A (B).
 - ☐ B (C).
 - ☐ C (A).
 - ☐ D (D).
- 31) TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN SERIES. THE OVERALL RESISTANCE WILL BE:
- ☐ A $0\ \Omega$.
 - ☐ B $100\ \Omega$.
 - ☐ C $25\ \Omega$.
 - ☐ D $50\ \Omega$.

- 32) THE RESISTIVITY OF A WIRE DEPENDS ON:
- ☐ A MATERIAL.
 - ☐ B AREA OF CROSS-SECTION.
 - ☐ C LENGTH.
 - ☐ D LENGTH, MATERIAL AND AREA OF CROSS-SECTION.
- 33) THE UNIT OF RESISTIVITY IS:
- ☐ A OHM/M².
 - ☐ B OHM.
 - ☐ C OHM·M.
 - ☐ D OHM/M.
- 34) TWO ALUMINUM WIRES HAVE THE SAME LENGTH AND DIFFERENT CROSS-SECTIONAL AREA. WIRE *B* HAS TWICE THE RADIUS OF THAT OF WIRE *A*. DETERMINE HOW THE RESISTANCE OF WIRE *B* COMPARES TO THE RESISTANCE OF WIRE *A*.
- ☐ A $\frac{R_B}{R_A} = \frac{1}{2}$.
 - ☐ B $\frac{R_B}{R_A} = \frac{1}{1}$.
 - ☐ C $\frac{R_B}{R_A} = \frac{2}{1}$.
 - ☐ D $\frac{R_B}{R_A} = \frac{1}{4}$.
- 35) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN PARALLEL IS *true*.
- ☐ A THE TOTAL VOLTAGE ACROSS THE RESISTORS IS THE SUM OF THE VOLTAGE ACROSS EACH RESISTOR.
 - ☐ B THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
 - ☐ C THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ D THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
- 36) TWO RESISTORS $R_1 = 6\ \Omega$ AND $R_2 = 12\ \Omega$ ARE CONNECTED IN PARALLEL TO EACH OTHER AND IN SERIES TO $R_2 = 2\ \Omega$. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- ☐ A $6\ \Omega$.
 - ☐ B $1\ \Omega$.
 - ☐ C $3\ \Omega$.
 - ☐ D $2\ \Omega$.

37) JOULE/COULOMB IS SAME AS:

- ☐ A OHM.
- ☐ B VOLT.
- ☐ C WATT.
- ☐ D AMPERE.

38) THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 3. COMPUTE THE RESISTANCE OF THE WIRE.

- ☐ A $1\ \Omega$.
- ☐ B $0.8\ \Omega$.
- ☐ C $0.4\ \Omega$.
- ☐ D $1.7\ \Omega$.

39) TWO COPPER WIRES HAVE THE SAME CROSS-SECTIONAL AREA BUT HAVE DIFFERENT LENGTHS. WIRE X HAS A LENGTH L AND WIRE Y HAS A LENGTH $2L$. THE RATIO BETWEEN THE RESISTANCE OF WIRE Y AND WIRE X IS:

- ☐ A $\frac{R_Y}{R_X} = \frac{2}{1}$.
- ☐ B $\frac{R_Y}{R_X} = \frac{1}{1}$.
- ☐ C $\frac{R_Y}{R_X} = \frac{1}{4}$.
- ☐ D $\frac{R_Y}{R_X} = \frac{1}{2}$.

40) COMPLETE THE FOLLOWING STATEMENT: "THE ELECTROMOTIVE FORCE IS:

- ☐ A THE MAXIMUM POTENTIAL DIFFERENCE BETWEEN THE TERMINALS OF A BATTERY".
- ☐ B THE MAXIMUM ELECTRIC POTENTIAL ENERGY STORED WITHIN A BATTERY".
- ☐ C THE FORCE THAT ACCELERATES PROTONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
- ☐ D THE FORCE THAT ACCELERATES ELECTRONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".

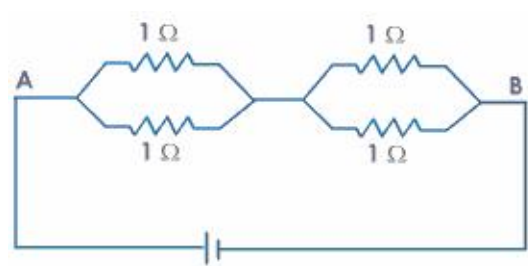


FIGURA 1

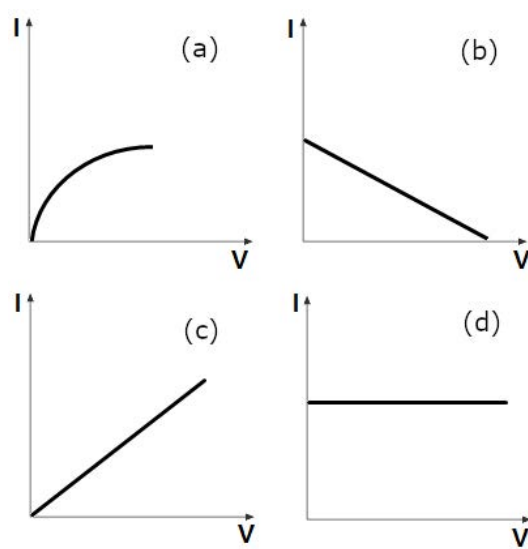


FIGURA 2

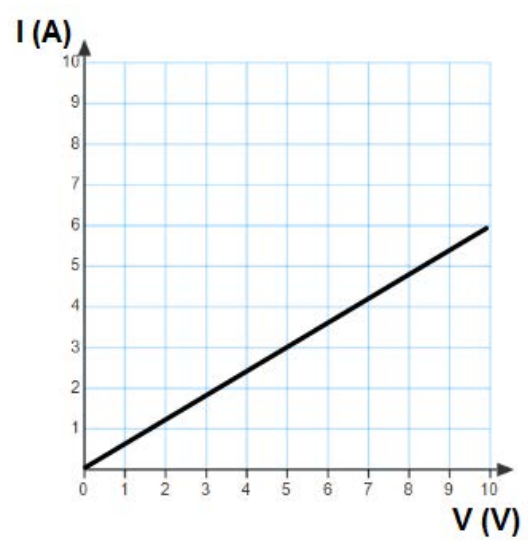


FIGURA 3

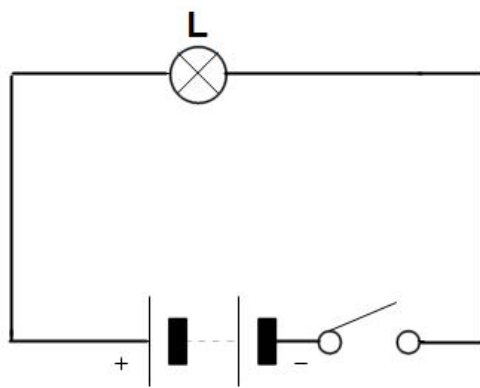


FIGURA 4

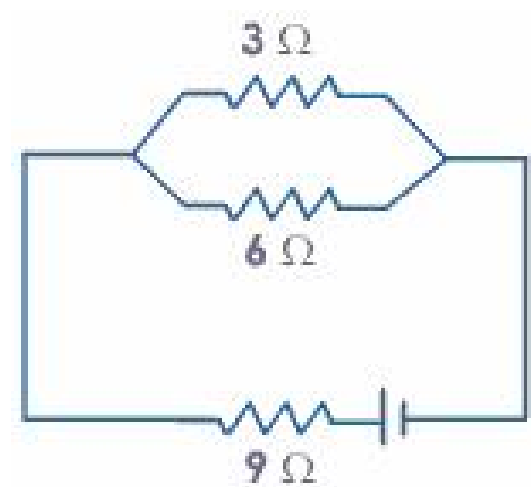


FIGURA 5

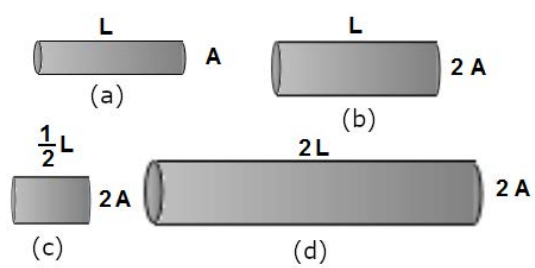


FIGURA 6

LICEO STATALE “NICCOLÒ MACHIAVELLI” DI ROMA
5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

VERSIONE ♡4

DATA CLASSE

ALUNNO

IL PUNTEGGIO PER OGNI RISPOSTA CORRETTA È DI 4 PUNTI, PER OGNI RISPOSTA OMESSA 1 PUNTO, PER OGNI RISPOSTA SBAGLIATA 0 PUNTI. LA DURATA DELLA VERIFICA È DI UN’ORA. SI SUGGERISCE DI RICOPIARE LE RISPOSTE NELLA TABELLA A SEGUIRE O IN CASO DI DIFFICOLTÀ NELLA COPIA SE NE SEGNALI L’ASSENZA.

TABELLA DELLE RISPOSTE									
1	2	3	4	5	6	7	8	9	10
11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40

① THE UNIT OF ELECTRIC POWER IS:

- ☐ A JOULE.
- ☐ B VOLT.
- ☐ C WATT.
- ☐ D AMPERE.

- ② TWO RESISTORS $R_1 = 3\ \Omega$ AND $R_2 = 6\ \Omega$ ARE CONNECTED IN PARALLEL. COMPUTE THE NET RESISTANCE IN THE CIRCUIT.
- ☐ A $1\ \Omega$.
 - ☐ B $3\ \Omega$.
 - ☐ C $2\ \Omega$.
 - ☐ D $6\ \Omega$.
- ③ TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN SERIES. THE OVERALL RESISTANCE WILL BE:
- ☐ A $50\ \Omega$.
 - ☐ B $0\ \Omega$.
 - ☐ C $25\ \Omega$.
 - ☐ D $100\ \Omega$.
- ④ DETERMINE WHICH OF THE GRAPHS IN FIGURE 1 AT THE END OF THE TEXT REPRESENTS OHM'S LAW FOR A SOLID CONDUCTOR.
- ☐ A (D).
 - ☐ B (A).
 - ☐ C (B).
 - ☐ D (C).
- ⑤ THE CURRENT IN A WIRE:
- ☐ A DEPENDS ON BOTH RESISTANCE AND POTENTIAL DIFFERENCE.
 - ☐ B DEPENDS ONLY ON THE RESISTANCE OF THE WIRE.
 - ☐ C DEPENDS ONLY ON THE POTENTIAL DIFFERENCE APPLIED.
 - ☐ D DOES NOT DEPEND ON RESISTANCE AND POTENTIAL DIFFERENCE.
- ⑥ THE RESISTIVITY OF A WIRE DEPENDS ON:
- ☐ A MATERIAL.
 - ☐ B AREA OF CROSS-SECTION.
 - ☐ C LENGTH, MATERIAL AND AREA OF CROSS-SECTION.
 - ☐ D LENGTH.

- ⑦ THE AMOUNT OF CHARGE FLOWING THROUGH A CROSS-SECTIONAL AREA OF A WIRE PER UNIT OF TIME IS CALLED:
- ☐ A POWER.
 - ☐ B CURRENT.
 - ☐ C VOLTAGE.
 - ☐ D RESISTANCE.
- ⑧ JOULE/COULOMB IS SAME AS:
- ☐ A OHM.
 - ☐ B VOLT.
 - ☐ C WATT.
 - ☐ D AMPERE.
- ⑨ IN FIGURE 2 AT THE END OF THE TEXT,
- ☐ A $6\ \Omega$, $3\ \Omega$ AND $9\ \Omega$ ARE IN SERIES.
 - ☐ B $9\ \Omega$ AND $6\ \Omega$ ARE IN PARALLEL AND THE COMBINATION IS IN SERIES WITH $3\ \Omega$.
 - ☐ C $3\ \Omega$, $6\ \Omega$ ARE IN PARALLEL AND $9\ \Omega$ IS IN SERIES.
 - ☐ D $3\ \Omega$, $6\ \Omega$ AND $9\ \Omega$ ARE IN PARALLEL.
- ⑩ THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 3. COMPUTE THE POWER DISSIPATED IN THE RESISTOR WHEN THE APPLIED VOLTAGE IS 5 V .
- ☐ A 20 W .
 - ☐ B 15 W .
 - ☐ C 10 W .
 - ☐ D 5 W .
- ⑪ WHEN A CURRENT I FLOWS THROUGH A RESISTANCE R FOR TIME t THE ELECTRICAL ENERGY SPENT IS GIVEN BY:
- ☐ A IR^2t .
 - ☐ B I^2Rt .
 - ☐ C IRt .
 - ☐ D I^2R/t .

- ⑫ THREE EQUAL RESISTANCES WHEN COMBINED IN SERIES ARE EQUIVALENT TO $90\ \Omega$. THEIR EQUIVALENT RESISTANCE WHEN COMBINED IN PARALLEL WILL BE:
- ☐ A $270\ \Omega$.
 - ☐ B $810\ \Omega$.
 - ☐ C $30\ \Omega$.
 - ☐ D $10\ \Omega$.
- ⑬ A BATTERY IS USED TO:
- ☐ A MEASURE ELECTRIC POTENTIAL.
 - ☐ B MEASURE ELECTRIC CURRENT.
 - ☐ C MAINTAIN A POTENTIAL DIFFERENCE.
 - ☐ D SAFEGUARD AGAINST SHORT-CIRCUIT.
- ⑭ THE RESISTANCE OF AN ELECTRIC BULB DRAWING $1.2\ \text{A}$ CURRENT AT $6.0\ \text{V}$ IS:
- ☐ A $0.2\ \text{W}$.
 - ☐ B $0.5\ \text{W}$.
 - ☐ C $2\ \text{W}$.
 - ☐ D $5\ \text{W}$.
- ⑮ ALL OF THE WIRES IN FIGURE 4 AT THE END OF THE TEXT ARE MADE OF THE SAME MATERIAL BUT ARE DIFFERENT SIZES. IDENTIFY THE WIRE WITH THE LOWEST RESISTANCE.
- ☐ A (A).
 - ☐ B (C).
 - ☐ C (B).
 - ☐ D (D).
- ⑯ THE WORK DONE IN MOVING A UNIT POSITIVE CHARGE ACROSS TWO POINTS IN AN ELECTRIC CIRCUIT IS A MEASURE OF:
- ☐ A CURRENT.
 - ☐ B POTENTIAL DIFFERENCE.
 - ☐ C POWER.
 - ☐ D RESISTANCE.

- 17) COMPLETE THE FOLLOWING STATEMENT: "THE ELECTROMOTIVE FORCE IS:
- A THE MAXIMUM ELECTRIC POTENTIAL ENERGY STORED WITHIN A BATTERY".
 - B THE FORCE THAT ACCELERATES PROTONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
 - C THE FORCE THAT ACCELERATES ELECTRONS THROUGH A WIRE WHEN A BATTERY IS CONNECTED TO IT".
 - D THE MAXIMUM POTENTIAL DIFFERENCE BETWEEN THE TERMINALS OF A BATTERY".
- 18) TWO ALUMINUM WIRES HAVE THE SAME LENGTH AND DIFFERENT CROSS-SECTIONAL AREA. WIRE *B* HAS TWICE THE RADIUS OF THAT OF WIRE *A*. DETERMINE HOW THE RESISTANCE OF WIRE *B* COMPARES TO THE RESISTANCE OF WIRE *A*.
- A $\frac{R_B}{R_A} = \frac{2}{1}$.
 - B $\frac{R_B}{R_A} = \frac{1}{4}$.
 - C $\frac{R_B}{R_A} = \frac{1}{2}$.
 - D $\frac{R_B}{R_A} = \frac{1}{1}$.
- 19) THREE RESISTORS $2\ \Omega$, $3\ \Omega$ AND $4\ \Omega$ ARE CONNECTED SO THAT THE EQUIVALENT RESISTANCE IS $9\ \Omega$. THE RESISTORS ARE CONNECTED:
- A ALL IN SERIES.
 - B $2\ \Omega$ AND $3\ \Omega$ IN PARALLEL AND THE COMBINATION IN SERIES WITH $4\ \Omega$.
 - C ALL IN PARALLEL.
 - D $2\ \Omega$ AND $3\ \Omega$ IN SERIES AND THE COMBINATION IN PARALLEL TO $4\ \Omega$.
- 20) A 10 A CURRENT IS MAINTAINED IN A SIMPLE CIRCUIT. COMPUTE THE NET CHARGE THAT PASSES THROUGH ANY POINT IN THE CIRCUIT DURING A 1 MINUTE INTERVAL.
- A 500 C.
 - B 400 C.
 - C 200 C.
 - D 600 C.

- 21) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_3 = 2\ \Omega$. Compute the net resistance in the circuit.
- ☐ A $1\ \Omega$.
 - ☐ B $2\ \Omega$.
 - ☐ C $3\ \Omega$.
 - ☐ D $6\ \Omega$.
- 22) A positive charge released from rest:
- ☐ A moves towards the regions of lower potential.
 - ☐ B does not move.
 - ☐ C moves towards the regions of higher potential.
 - ☐ D moves towards the regions of equal potential.
- 23) Ohm's law relates potential difference with:
- ☐ A time.
 - ☐ B energy.
 - ☐ C current.
 - ☐ D power.
- 24) Compute the number of electrons flowing through a battery that delivers a current of $3.0\ \text{A}$ for $12\ \text{s}$.
- ☐ A 2.2×10^{20} .
 - ☐ B 36.
 - ☐ C 4.8×10^{15} .
 - ☐ D 6.4×10^{18} .
- 25) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- ☐ A $D^2 \cdot P$.
 - ☐ B D^2/P .
 - ☐ C $D \cdot P^2$.
 - ☐ D $D \cdot P$.

- 26) DETERMINE WHICH OF THE FOLLOWING STATEMENTS DOES NOT REPRESENT OHM'S LAW.
- ☐ A POTENTIAL DIFFERENCE / CURRENT = CONSTANT.
 - ☐ B CURRENT / POTENTIAL DIFFERENCE = CONSTANT.
 - ☐ C POTENTIAL DIFFERENCE = CURRENT \times RESISTANCE.
 - ☐ D CURRENT = RESISTANCE \times POTENTIAL DIFFERENCE.
- 27) THE UNIT OF RESISTIVITY IS:
- ☐ A OHM.
 - ☐ B OHM/M.
 - ☐ C OHM·M.
 - ☐ D OHM/M².
- 28) IN FIGURE 5 AT THE END OF THE TEXT, THE RESISTANCE ACROSS AB IS:
- ☐ A 2 Ω .
 - ☐ B 1 Ω .
 - ☐ C 0.5 Ω .
 - ☐ D 4 Ω .
- 29) HEAT PRODUCED IN A CURRENT CARRYING WIRE IN 5s IS 60 J. THE SAME CURRENT IS PASSED THROUGH ANOTHER WIRE OF HALF THE RESISTANCE. THE HEAT PRODUCED IN 5 s WILL BE:
- ☐ A 15 J.
 - ☐ B 30 J.
 - ☐ C 120 J.
 - ☐ D 60 J.
- 30) IF D IS THE INTENSITY OF CURRENT CIRCULATING IN A RESISTOR WITH RESISTANCE F , THE POWER DISSIPATED BY THE RESISTOR IS DESCRIBED BY THE FORMULA:
- ☐ A $D \cdot F$.
 - ☐ B D^2/F .
 - ☐ C $D^2 \cdot F$.
 - ☐ D $D \cdot F^2$.

- 31) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN PARALLEL IS *true*.
- ☐ A THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ B THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
 - ☐ C THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
 - ☐ D THE TOTAL VOLTAGE ACROSS THE RESISTORS IS THE SUM OF THE VOLTAGE ACROSS EACH RESISTOR.
- 32) WHEN THERE IS AN ELECTRIC CURRENT PASSING THROUGH A WIRE, THE PARTICLES MOVING ARE:
- ☐ A PROTONS.
 - ☐ B ATOMS.
 - ☐ C IONS.
 - ☐ D ELECTRONS.
- 33) THE POTENTIAL DIFFERENCE REQUIRED TO PASS A CURRENT 0.2 A IN A WIRE OF RESISTANCE 20 Ω IS:
- ☐ A 40 V.
 - ☐ B 100 V.
 - ☐ C 1 V.
 - ☐ D 4 V.
- 34) A WIRE OF LENGTH L AND CROSS-SECTIONAL AREA A HAS A RESISTIVITY ρ . DETERMINE WHICH OF THE FOLLOWING FORMULAS CAN BE USED TO CALCULATE THE RESISTANCE OF THE WIRE.
- ☐ A $R = \frac{\rho L}{A}$.
 - ☐ B $R = \frac{A}{\rho L}$.
 - ☐ C $R = \frac{L}{\rho A}$.
 - ☐ D $R = \frac{\rho A}{L}$.
- 35) DETERMINE THE DIRECTION OF THE CONVENTIONAL CURRENT THROUGH THE LIGHT BULB IN THE CIRCUIT PRESENTED IN FIGURE 6 AT THE END OF THE TEXT.
- ☐ A TO THE RIGHT.
 - ☐ B UPWARD.
 - ☐ C TO THE LEFT.
 - ☐ D DOWNWARD.

- 36) DETERMINE WHICH ONE OF THE FOLLOWING STATEMENTS CONCERNING RESISTORS IN SERIES IS *true*.
- ☐ A THE POWER DISSIPATED BY EACH RESISTOR IS THE SAME.
 - ☐ B THE TOTAL CURRENT THROUGH THE RESISTORS IS THE SUM OF THE CURRENT THROUGH EACH RESISTOR.
 - ☐ C THE CURRENT THROUGH EACH RESISTOR IS THE SAME.
 - ☐ D THE VOLTAGE ACROSS EACH RESISTOR IS THE SAME.
- 37) TWO RESISTANCES OF $100\ \Omega$ AND ZERO OHM ARE CONNECTED IN PARALLEL. THE OVERALL RESISTANCE WILL BE:
- ☐ A $0\ \Omega$.
 - ☐ B $50\ \Omega$.
 - ☐ C $25\ \Omega$.
 - ☐ D $100\ \Omega$.
- 38) TWO COPPER WIRES HAVE THE SAME CROSS-SECTIONAL AREA BUT HAVE DIFFERENT LENGTHS. WIRE X HAS A LENGTH L AND WIRE Y HAS A LENGTH $2L$. THE RATIO BETWEEN THE RESISTANCE OF WIRE Y AND WIRE X IS:
- ☐ A $\frac{R_Y}{R_X} = \frac{2}{1}$.
 - ☐ B $\frac{R_Y}{R_X} = \frac{1}{1}$.
 - ☐ C $\frac{R_Y}{R_X} = \frac{1}{4}$.
 - ☐ D $\frac{R_Y}{R_X} = \frac{1}{2}$.
- 39) THE ELECTRIC CURRENT AS A FUNCTION OF VOLTAGE OF A WIRE IS PRESENTED BY THE GRAPH IN FIGURE 3. COMPUTE THE RESISTANCE OF THE WIRE.
- ☐ A $1.7\ \Omega$.
 - ☐ B $0.8\ \Omega$.
 - ☐ C $1\ \Omega$.
 - ☐ D $0.4\ \Omega$.
- 40) THE UNIT OF CURRENT IS:
- ☐ A WATT.
 - ☐ B VOLT.
 - ☐ C COULOMB.
 - ☐ D AMPERE.

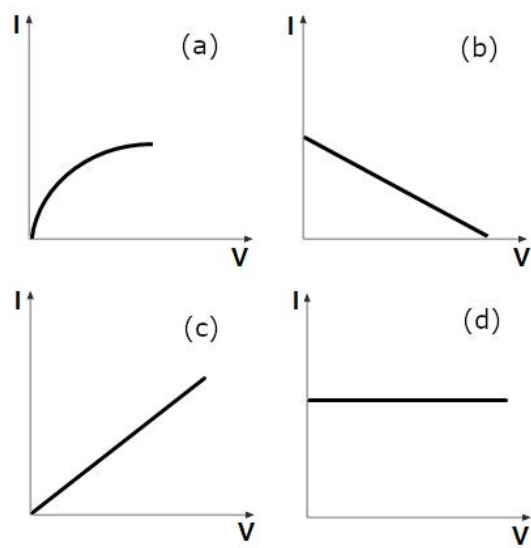


FIGURA 1

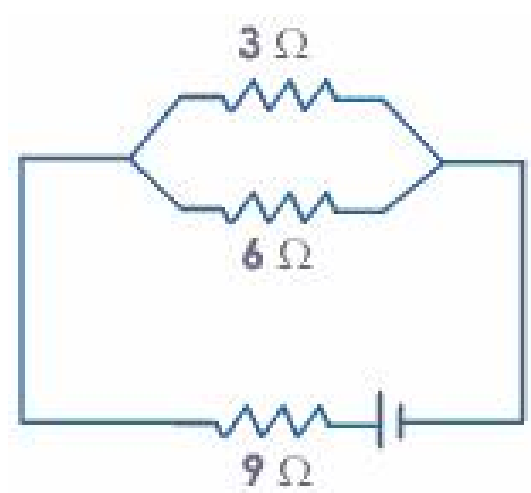


FIGURA 2

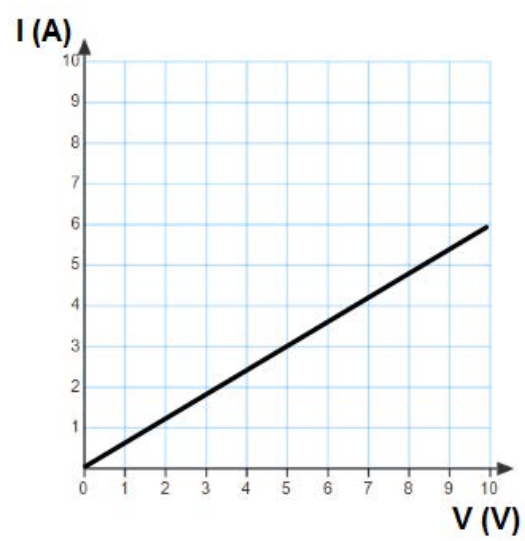


FIGURA 3

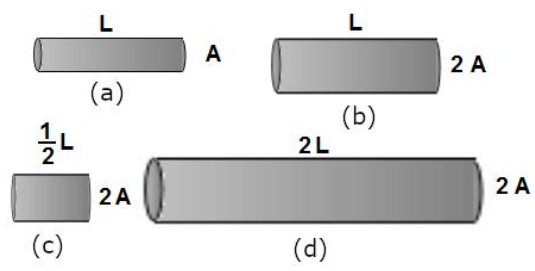


FIGURA 4

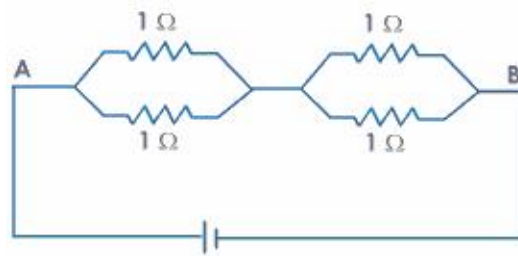


FIGURA 5

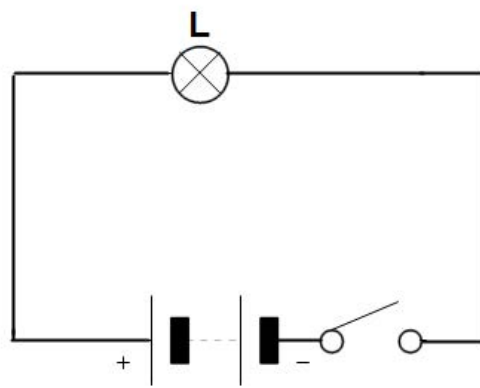


FIGURA 6