

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 0

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																				
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	

- 1 When there is an electric current passing through a wire, the particles moving are:
- A electrons.
B protons.
C atoms.
D ions.
- 2 The unit of current is:
- A ampere.
B watt.
C volt.
D coulomb.
- 3 A positive charge released from rest:
- A moves towards the regions of lower potential.
B moves towards the regions of higher potential.
C moves towards the regions of equal potential.
D does not move.
- 4 The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- A Current.
B Voltage.
C Power.
D Resistance.
- 5 Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.
- A To the right.
B To the left.
C Downward.
- 6 A battery is used to:
- A maintain a potential difference.
B measure electric current.
C measure electric potential.
D safeguard against short-circuit.
- 7 The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A potential difference.
B current.
C resistance.
D power.
- 8 Joule/coulomb is same as:
- A volt.
B watt.
C ampere.
D ohm.
- 9 Complete the following statement: “The electromotive force is:
- A the maximum potential difference between the terminals of a battery”.
B the force that accelerates electrons through a wire when a battery is connected to it”.
C the force that accelerates protons through a wire when a battery is connected to it”.
D the maximum electric potential energy stored within a battery”.
- 10 Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- A 2.2×10^{20} .

B 36.

C 4.8×10^{15} .

D 6.4×10^{18} .

- (11) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

A 600 C.

B 200 C.

C 500 C.

D 400 C.

- (12) Ohm's law relates potential difference with:

A current.

B power.

C energy.

D time.

- (13) The current in a wire:

A depends on both resistance and potential difference.

B depends only on the potential difference applied.

C depends only on the resistance of the wire.

D does not depend on resistance and potential difference.

- (14) Determine which of the following statements does not represent Ohm's law.

A current = resistance \times potential difference.

B current / potential difference = constant.

C potential difference / current = constant.

D potential difference = current \times resistance.

- (15) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

A 4 V.

B 100 V.

C 1 V.

D 40 V.

- (16) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

A 5 W.

B 0.5 W.

C 0.2 W.

D 2 W.

- (17) Determine which of the graphs in Figure 2 at the end of the text represents Ohm's law for a solid conductor.

A (c).

B (a).

C (b).

D (d).

- (18) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the resistance of the wire.

A 1.7Ω .

B 1Ω .

C 0.8Ω .

D 0.4Ω .

- (19) The unit of resistivity is:

A ohm \cdot m.

B ohm.

C ohm/m.

D ohm/m 2 .

- (20) The resistivity of a wire depends on:

A material.

B length.

C area of cross-section.

D length, material and area of cross-section.

- (21) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{\rho L}{A}$.

B $R = \frac{\rho A}{L}$.

C $R = \frac{L}{\rho A}$.

D $R = \frac{A}{\rho L}$.

- (22) All of the wires in Figure 4 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (b).

B (a).

C (c).

D (d).

- (23) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{2}{1}$.

B $\frac{R_Y}{R_X} = \frac{1}{1}$.

C $\frac{R_Y}{R_X} = \frac{1}{2}$.

D $\frac{R_Y}{R_X} = \frac{1}{4}$.

- (24) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

- (A) $\frac{R_B}{R_A} = \frac{1}{4}$.
- (B) $\frac{R_B}{R_A} = \frac{1}{1}$.
- (C) $\frac{R_B}{R_A} = \frac{1}{2}$.
- (D) $\frac{R_B}{R_A} = \frac{2}{1}$.

(25) The unit of electric power is:

- (A) watt.
- (B) ampere.
- (C) volt.
- (D) joule.

(26) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- (A) $D \cdot P$.
- (B) $D^2 \cdot P$.
- (C) $D \cdot P^2$.
- (D) D^2/P .

(27) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- (A) $D^2 \cdot F$.
- (B) $D \cdot F$.
- (C) $D \cdot F^2$.
- (D) D^2/F .

(28) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- (A) $I^2 R t$.
- (B) IRt .
- (C) $IR^2 t$.
- (D) $I^2 R/t$.

(29) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- (A) 30 J.
- (B) 60 J.
- (C) 15 J.
- (D) 120 J.

(30) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- (A) 15 W.
- (B) 5 W.
- (C) 10 W.
- (D) 20 W.

(31) Determine which one of the following statements concerning resistors in series is *true*.

- (A) The current through each resistor is the same.
- (B) The voltage across each resistor is the same.
- (C) The power dissipated by each resistor is the same.
- (D) The total current through the resistors is the sum of the current through each resistor.

(32) Determine which one of the following statements concerning resistors in parallel is *true*.

- (A) The voltage across each resistor is the same.
- (B) The current through each resistor is the same.
- (C) The power dissipated by each resistor is the same.
- (D) The total voltage across the resistors is the sum of the voltage across each resistor.

(33) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

- (A) $0\ \Omega$.
- (B) $100\ \Omega$.
- (C) $50\ \Omega$.
- (D) $25\ \Omega$.

(34) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

- (A) $100\ \Omega$.
- (B) $50\ \Omega$.
- (C) $25\ \Omega$.
- (D) $0\ \Omega$.

(35) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:

- (A) all in series.
- (B) all in parallel.
- (C) $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
- (D) $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.

(36) In Figure 5 at the end of the text,

- (A) $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
- (B) $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
- (C) $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
- (D) $3\ \Omega$, $6\ \Omega$ and $9\ \Omega$ are in parallel.

(37) In Figure 6 at the end of the text, the resistance across AB is:

- (A) $1\ \Omega$.
- (B) $4\ \Omega$.
- (C) $2\ \Omega$.
- (D) $0.5\ \Omega$.

- (38) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:

- A $10\ \Omega$.
 B $270\ \Omega$.
 C $30\ \Omega$.
 D $810\ \Omega$.

- (39) Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A $2\ \Omega$.

- (40) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.

- A $6\ \Omega$.
 B $1\ \Omega$.
 C $3\ \Omega$.
 D $2\ \Omega$.

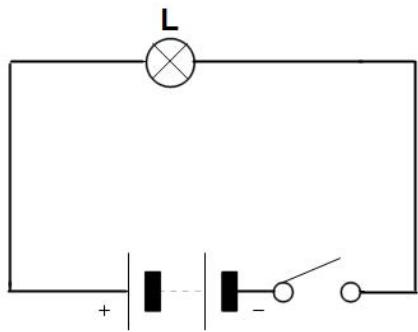


Figura 1

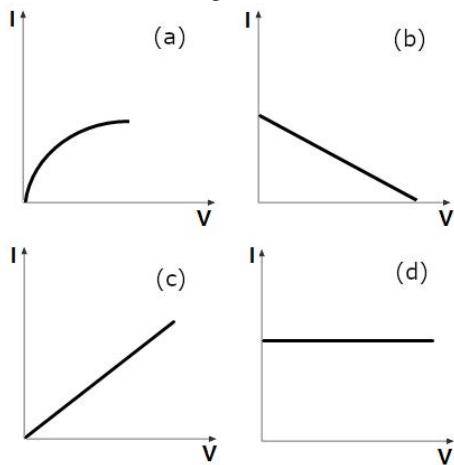


Figura 2

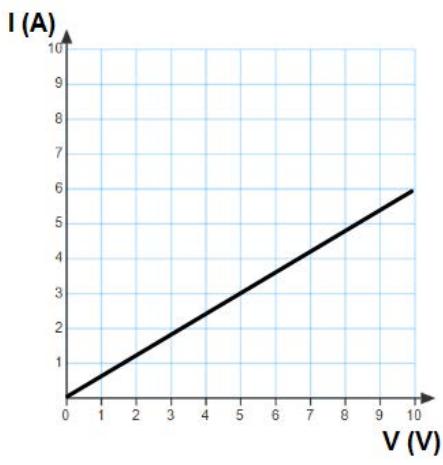


Figura 3

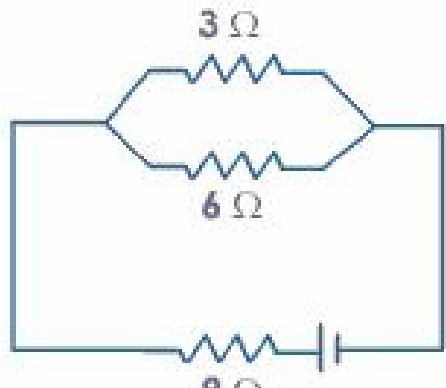


Figura 5

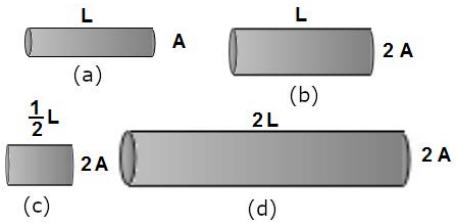


Figura 4

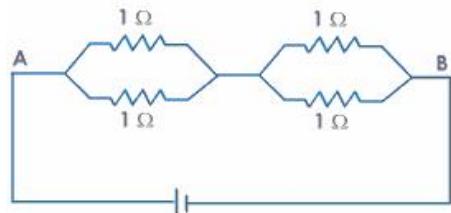


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 1

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

① The unit of current is:

- A ampere.
- B watt.
- C volt.
- D coulomb.

D Voltage.

② The current in a wire:

- A depends only on the potential difference applied.
- B depends on both resistance and potential difference.
- C depends only on the resistance of the wire.
- D does not depend on resistance and potential difference.

⑥ Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

- A 1Ω .
- B 3Ω .
- C 6Ω .
- D 2Ω .

③ In Figure 1 at the end of the text,

- A 6Ω , 3Ω and 9Ω are in series.
- B 3Ω , 6Ω and Ω are in parallel.
- C 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
- D 3Ω , 6Ω are in parallel and 9Ω is in series.

⑦ The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- A 2 W.
- B 0.2 W.
- C 5 W.
- D 0.5 W.

④ If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D \cdot F$.
- B D^2/F .
- C $D \cdot F^2$.
- D $D^2 \cdot F$.

⑧ Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A 6Ω .
- B 3Ω .
- C 1Ω .
- D 2Ω .

⑤ The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Power.
- B Resistance.
- C Current.

⑨ Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.

- A To the left.
- B To the right.
- C Upward.
- D Downward.

⑩ If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A $D \cdot P$.

B $D \cdot P^2$.

C D^2/P .

D $D^2 \cdot P$.

- (11) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

A 500 C.

B 600 C.

C 400 C.

D 200 C.

- (12) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{1}{4}$.

B $\frac{R_Y}{R_X} = \frac{1}{1}$.

C $\frac{R_Y}{R_X} = \frac{1}{2}$.

D $\frac{R_Y}{R_X} = \frac{2}{1}$.

- (13) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

A 4.8×10^{15} .

B 36.

C 6.4×10^{18} .

D 2.2×10^{20} .

- (14) When there is an electric current passing through a wire, the particles moving are:

A atoms.

B protons.

C ions.

D electrons.

- (15) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

A potential difference.

B power.

C current.

D resistance.

- (16) Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:

A 100Ω .

B 0Ω .

C 25Ω .

D 50Ω .

- (17) Determine which of the following statements does not represent Ohm's law.

A current = resistance \times potential difference.

B potential difference / current = constant.

C potential difference = current \times resistance.

D current / potential difference = constant.

- (18) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the resistance of the wire.

A 1.7Ω .

B 1Ω .

C 0.8Ω .

D 0.4Ω .

- (19) All of the wires in Figure 4 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (a).

B (d).

C (b).

D (c).

- (20) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:

A 30Ω .

B 10Ω .

C 270Ω .

D 810Ω .

- (21) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

A 4 V.

B 100 V.

C 1 V.

D 40 V.

- (22) Ohm's law relates potential difference with:

A time.

B current.

C power.

D energy.

- (23) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{1}{4}$.

B $\frac{R_B}{R_A} = \frac{2}{1}$.

C $\frac{R_B}{R_A} = \frac{1}{2}$.

D $\frac{R_B}{R_A} = \frac{1}{1}$.

- (24) Complete the following statement: "The electromotive force is:
 A the force that accelerates protons through a wire when a battery is connected to it".
 B the maximum electric potential energy stored within a battery".
 C the maximum potential difference between the terminals of a battery".
 D the force that accelerates electrons through a wire when a battery is connected to it".
- (25) Determine which of the graphs in Figure 5 at the end of the text represents Ohm's law for a solid conductor.
 A (d).
 B (c).
 C (b).
 D (a).
- (26) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the power dissipated in the resistor when the applied voltage is 5 V.
 A 20 W.
 B 15 W.
 C 10 W.
 D 5 W.
- (27) In Figure 6 at the end of the text, the resistance across AB is:
 A 2 Ω .
 B 0.5 Ω .
 C 1 Ω .
 D 4 Ω .
- (28) Determine which one of the following statements concerning resistors in parallel is *true*.
 A The power dissipated by each resistor is the same.
 B The current through each resistor is the same.
 C The voltage across each resistor is the same.
 D The total voltage across the resistors is the sum of the voltage across each resistor.
- (29) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
 A 30 J.
 B 15 J.
 C 60 J.
 D 120 J.
- (30) Determine which one of the following statements concerning resistors in series is *true*.
 A The voltage across each resistor is the same.
 B The current through each resistor is the same.
- (31) The total current through the resistors is the sum of the current through each resistor.
 D The power dissipated by each resistor is the same.
- (32) A battery is used to:
 A safeguard against short-circuit.
 B maintain a potential difference.
 C measure electric current.
 D measure electric potential.
- (33) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:
 A all in series.
 B 2Ω and 3Ω in series and the combination in parallel to 4Ω .
 C 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 D all in parallel.
- (34) When a current I flows through a resistance R for time t the electrical energy spent is given by:
 A IRt .
 B IR^2t .
 C I^2Rt .
 D I^2R/t .
- (35) The resistivity of a wire depends on:
 A area of cross-section.
 B length.
 C length, material and area of cross-section.
 D material.
- (36) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
 A $R = \frac{\rho L}{A}$.
 B $R = \frac{L}{\rho A}$.
 C $R = \frac{\rho A}{L}$.
 D $R = \frac{A}{\rho L}$.
- (37) Joule/coulomb is same as:
 A ohm.
 B watt.
 C volt.
 D ampere.
- (38) A positive charge released from rest:
 A moves towards the regions of higher potential.
 B moves towards the regions of equal potential.
 C moves towards the regions of lower potential.
 D does not move.

(38) The unit of resistivity is:

- A ohm/m.
- B ohm.
- C ohm/m².
- D ohm·m.

C volt.

D watt.

(39) The unit of electric power is:

- A ampere.
- B joule.

(40) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

- A $50\ \Omega$.
- B $0\ \Omega$.
- C $25\ \Omega$.
- D $100\ \Omega$.

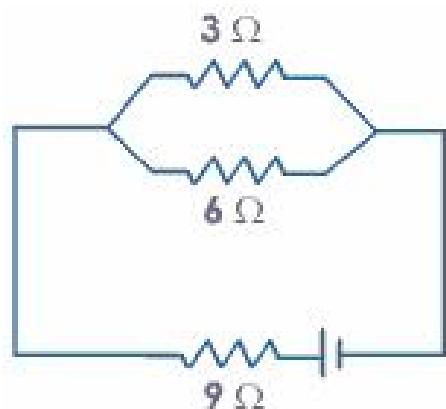


Figura 1

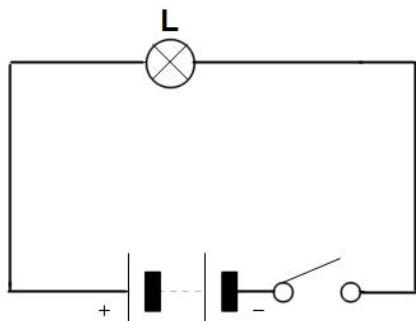


Figura 2

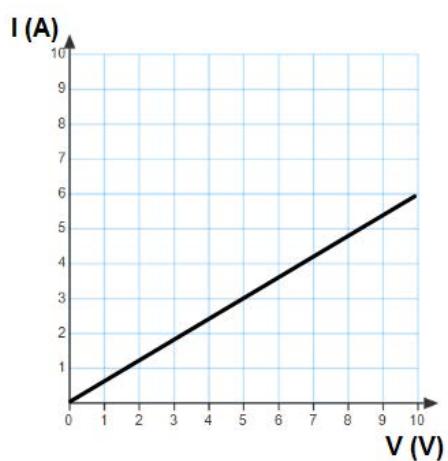


Figura 3

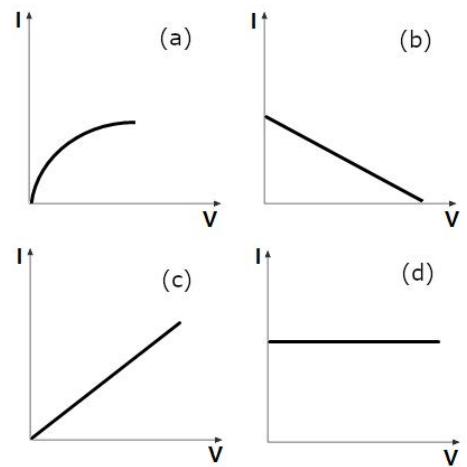


Figura 5

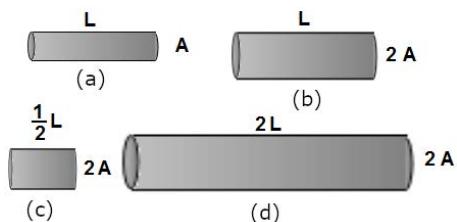


Figura 4

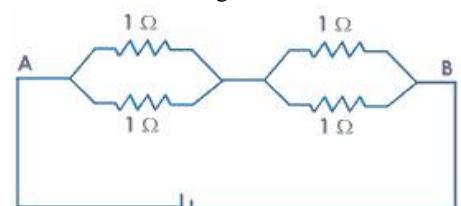


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 2

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 5 W.
 B 0.5 W.
 C 0.2 W.
 D 2 W.
- (2) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
- A $25\ \Omega$.
 B $100\ \Omega$.
 C $0\ \Omega$.
 D $50\ \Omega$.
- (3) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- A $30\ \Omega$.
 B $10\ \Omega$.
 C $270\ \Omega$.
 D $810\ \Omega$.
- (4) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- A 5 W.
 B 10 W.
 C 15 W.
 D 20 W.
- (5) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- A Power.
- (6) In Figure 2 at the end of the text, the resistance across AB is:
- A $2\ \Omega$.
 B $1\ \Omega$.
 C $0.5\ \Omega$.
 D $4\ \Omega$.
- (7) The unit of electric power is:
- A joule.
 B volt.
 C watt.
 D ampere.
- (8) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- A $25\ \Omega$.
 B $50\ \Omega$.
 C $100\ \Omega$.
 D $0\ \Omega$.
- (9) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A potential difference.
 B current.
 C power.
 D resistance.
- (10) The current in a wire:
- A depends only on the resistance of the wire.
 B does not depend on resistance and potential difference.

- C depends on both resistance and potential difference.
 D depends only on the potential difference applied.

(11) The unit of resistivity is:

- A ohm/m.
 B ohm/m².
 C ohm.
 D ohm·m.

(12) Determine which one of the following statements concerning resistors in parallel is *true*.

- A The voltage across each resistor is the same.
 B The total voltage across the resistors is the sum of the voltage across each resistor.
 C The current through each resistor is the same.
 D The power dissipated by each resistor is the same.

(13) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A I^2Rt .
 B IR^2t .
 C IRt .
 D I^2R/t .

(14) Determine which of the following statements does not represent Ohm's law.

- A potential difference = current \times resistance.
 B current / potential difference = constant.
 C potential difference / current = constant.
 D current = resistance \times potential difference.

(15) Complete the following statement: "The electromotive force is:

- A the maximum electric potential energy stored within a battery.
 B the force that accelerates protons through a wire when a battery is connected to it".
 C the force that accelerates electrons through a wire when a battery is connected to it".
 D the maximum potential difference between the terminals of a battery".

(16) Determine which one of the following statements concerning resistors in series is *true*.

- A The current through each resistor is the same.
 B The power dissipated by each resistor is the same.
 C The total current through the resistors is the sum of the current through each resistor.
 D The voltage across each resistor is the same.

(17) Ohm's law relates potential difference with:

- A current.

- B power.
 C energy.
 D time.

(18) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

- A 6Ω .
 B 1Ω .
 C 2Ω .
 D 3Ω .

(19) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- A 15 J.
 B 60 J.
 C 30 J.
 D 120 J.

(20) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D \cdot F$.
 B $D^2 \cdot F$.
 C D^2/F .
 D $D \cdot F^2$.

(21) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 400 C.
 B 200 C.
 C 600 C.
 D 500 C.

(22) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

- A all in series.
 B 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 C all in parallel.
 D 2Ω and 3Ω in series and the combination in parallel to 4Ω .

(23) The unit of current is:

- A coulomb.
 B volt.
 C ampere.
 D watt.

(24) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

- A 2.2×10^{20} .

B 6.4×10^{18} .

C 36.

D 4.8×10^{15} .

(25) The resistivity of a wire depends on:

A material.

B area of cross-section.

C length.

D length, material and area of cross-section.

(26) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{1}{1}$.

B $\frac{R_Y}{R_X} = \frac{1}{4}$.

C $\frac{R_Y}{R_X} = \frac{2}{1}$.

D $\frac{R_Y}{R_X} = \frac{1}{2}$.

(27) When there is an electric current passing through a wire, the particles moving are:

A protons.

B atoms.

C electrons.

D ions.

(28) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

A 100 V.

B 1 V.

C 4 V.

D 40 V.

(29) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

A $D \cdot P^2$.

B $D^2 \cdot P$.

C D^2/P .

D $D \cdot P$.

(30) Joule/coulomb is same as:

A ampere.

B ohm.

C watt.

D volt.

(31) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.

A (a).

B (b).

C (c).

D (d).

(32) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.

A 1Ω .

B 0.8Ω .

C 1.7Ω .

D 0.4Ω .

(33) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 4 at the end of the text.

A To the right.

B Upward.

C Downward.

D To the left.

(34) A battery is used to:

A safeguard against short-circuit.

B maintain a potential difference.

C measure electric current.

D measure electric potential.

(35) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{1}{1}$.

B $\frac{R_B}{R_A} = \frac{1}{4}$.

C $\frac{R_B}{R_A} = \frac{2}{1}$.

D $\frac{R_B}{R_A} = \frac{1}{2}$.

(36) A positive charge released from rest:

A moves towards the regions of equal potential.

B moves towards the regions of lower potential.

C moves towards the regions of higher potential.

D does not move.

(37) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 2Ω .

B 6Ω .

C 1Ω .

D 3Ω .

- (38) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{L}{\rho A}$.

B $R = \frac{\rho A}{L}$.

C $R = \frac{A}{\rho L}$.

D $R = \frac{\rho L}{A}$.

- (39) All of the wires in Figure 5 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- (a).
- (b).
- (c).
- (d).

- (40) In Figure 6 at the end of the text,

- 9 Ω and 6 Ω are in parallel and the combination is in series with 3 Ω .
- 3 Ω , 6 Ω and 9 Ω are in parallel.
- 3 Ω , 6 Ω are in parallel and 9 Ω is in series.
- 6 Ω , 3 Ω and 9 Ω are in series.

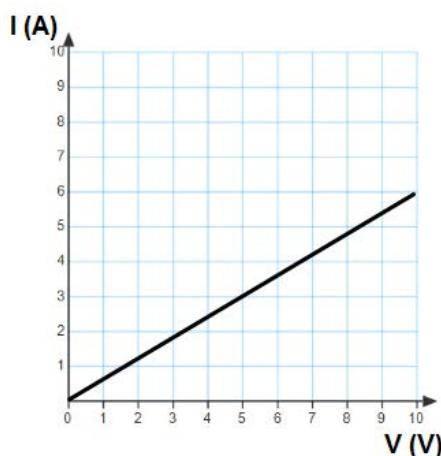


Figura 1

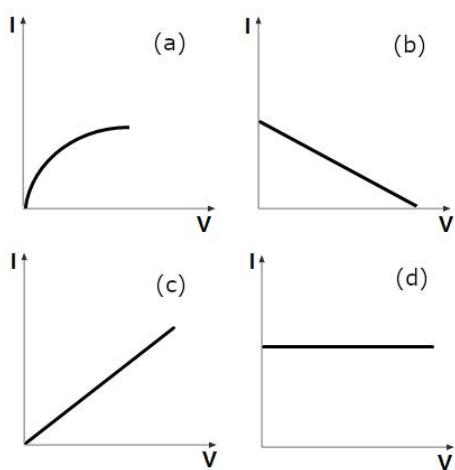


Figura 3

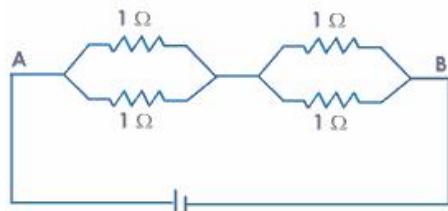


Figura 2

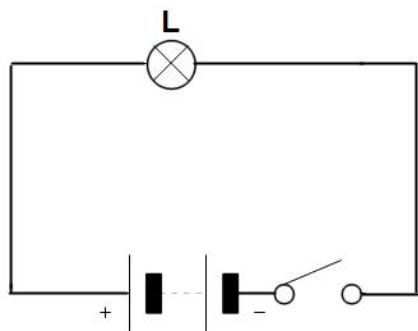


Figura 4

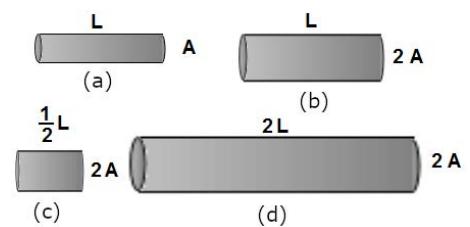


Figura 5

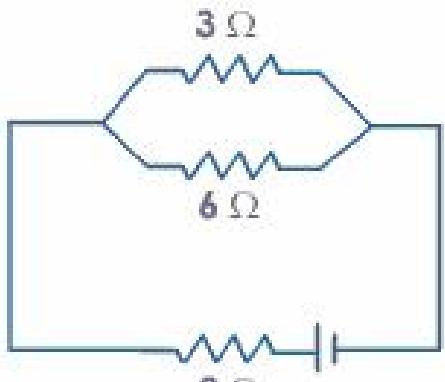


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 3

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] $D^2 \cdot P$.
 [B] $D \cdot P^2$.
 [C] D^2/P .
 [D] $D \cdot P$.
- ② Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- [A] 4.8×10^{15} .
 [B] 36.
 [C] 2.2×10^{20} .
 [D] 6.4×10^{18} .
- ③ Ohm's law relates potential difference with:
- [A] current.
 [B] time.
 [C] energy.
 [D] power.
- ④ Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.
- [A] To the right.
 [B] Downward.
 [C] Upward.
 [D] To the left.
- ⑤ Determine which one of the following statements concerning resistors in parallel is *true*.
- [A] The current through each resistor is the same.
 [B] The power dissipated by each resistor is the same.
- ⑥ If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- [A] $D \cdot F$.
 [B] D^2/F .
 [C] $D^2 \cdot F$.
 [D] $D \cdot F^2$.
- ⑦ Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:
- [A] all in series.
 [B] 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 [C] 2Ω and 3Ω in series and the combination in parallel to 4Ω .
 [D] all in parallel.
- ⑧ The unit of current is:
- [A] volt.
 [B] watt.
 [C] ampere.
 [D] coulomb.
- ⑨ Two resistors $R_1 = 3\Omega$ and $R_2 = 6\Omega$ are connected in parallel. Compute the net resistance in the circuit.
- [A] 2Ω .
 [B] 1Ω .
 [C] 6Ω .
 [D] 3Ω .
- ⑩ Complete the following statement: “The electromotive force is:

- (A) the maximum electric potential energy stored within a battery".
- (B) the force that accelerates protons through a wire when a battery is connected to it".
- (C) the force that accelerates electrons through a wire when a battery is connected to it".
- (D) the maximum potential difference between the terminals of a battery".
- (11) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
- (A) $100\ \Omega$.
- (B) $0\ \Omega$.
- (C) $50\ \Omega$.
- (D) $25\ \Omega$.
- (12) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.
- (A) $6\ \Omega$.
- (B) $3\ \Omega$.
- (C) $1\ \Omega$.
- (D) $2\ \Omega$.
- (13) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- (A) Resistance.
- (B) Voltage.
- (C) Power.
- (D) Current.
- (14) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- (A) $50\ \Omega$.
- (B) $100\ \Omega$.
- (C) $25\ \Omega$.
- (D) $0\ \Omega$.
- (15) When there is an electric current passing through a wire, the particles moving are:
- (A) electrons.
- (B) protons.
- (C) ions.
- (D) atoms.
- (16) A positive charge released from rest:
- (A) does not move.
- (B) moves towards the regions of equal potential.
- (C) moves towards the regions of lower potential.
- (D) moves towards the regions of higher potential.
- (17) The potential difference required to pass a current 0.2 A in a wire of resistance $20\ \Omega$ is:
- (A) 100 V .
- (B) 40 V .
- (C) 4 V .
- (D) 1 V .
- (18) The unit of electric power is:
- (A) watt.
- (B) volt.
- (C) joule.
- (D) ampere.
- (19) In Figure 2 at the end of the text,
- (A) $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
- (B) $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
- (C) $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
- (D) $3\ \Omega$, $6\ \Omega$ and Ω are in parallel.
- (20) Heat produced in a current carrying wire in 5 s is 60 J . The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- (A) 120 J .
- (B) 60 J .
- (C) 15 J .
- (D) 30 J .
- (21) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- (A) $270\ \Omega$.
- (B) $810\ \Omega$.
- (C) $10\ \Omega$.
- (D) $30\ \Omega$.
- (22) All of the wires in Figure 3 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- (A) (d).
- (B) (c).
- (C) (b).
- (D) (a).
- (23) In Figure 4 at the end of the text, the resistance across AB is:
- (A) $0.5\ \Omega$.
- (B) $2\ \Omega$.
- (C) $1\ \Omega$.
- (D) $4\ \Omega$.
- (24) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- (A) $\frac{R_Y}{R_X} = \frac{1}{1}$.
- (B) $\frac{R_Y}{R_X} = \frac{1}{2}$.
- (C) $\frac{R_Y}{R_X} = \frac{1}{4}$.
- (D) $\frac{R_Y}{R_X} = \frac{2}{1}$.

(25) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- (A) 20 W.
- (B) 10 W.
- (C) 5 W.
- (D) 15 W.

(26) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

- (A) $\frac{R_B}{R_A} = \frac{1}{2}$.
- (B) $\frac{R_B}{R_A} = \frac{1}{4}$.
- (C) $\frac{R_B}{R_A} = \frac{2}{1}$.
- (D) $\frac{R_B}{R_A} = \frac{1}{1}$.

(27) Determine which one of the following statements concerning resistors in series is *true*.

- (A) The power dissipated by each resistor is the same.
- (B) The voltage across each resistor is the same.
- (C) The total current through the resistors is the sum of the current through each resistor.
- (D) The current through each resistor is the same.

(28) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- (A) 5 W.
- (B) 0.2 W.
- (C) 2 W.
- (D) 0.5 W.

(29) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- (A) IR^2t .
- (B) I^2R/t .
- (C) I^2Rt .
- (D) IRt .

(30) Joule/coulomb is same as:

- (A) ohm.
- (B) ampere.

- (C) volt.
- (D) watt.

(31) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- (A) 500 C.
- (B) 200 C.
- (C) 600 C.
- (D) 400 C.

(32) The resistivity of a wire depends on:

- (A) material.
- (B) length.
- (C) area of cross-section.
- (D) length, material and area of cross-section.

(33) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- (A) potential difference.
- (B) current.
- (C) resistance.
- (D) power.

(34) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- (A) $R = \frac{L}{\rho A}$.
- (B) $R = \frac{A}{\rho L}$.
- (C) $R = \frac{\rho A}{L}$.
- (D) $R = \frac{\rho L}{A}$.

(35) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the resistance of the wire.

- (A) 0.8 Ω .
- (B) 1.7 Ω .
- (C) 0.4 Ω .
- (D) 1 Ω .

(36) The current in a wire:

- (A) depends only on the resistance of the wire.
- (B) depends on both resistance and potential difference.
- (C) does not depend on resistance and potential difference.
- (D) depends only on the potential difference applied.

(37) Determine which of the graphs in Figure 6 at the end of the text represents Ohm's law for a solid conductor.

- (A) (b).
- (B) (d).
- (C) (c).

(a).

- (38) Determine which of the following statements does not represent Ohm's law.

- A potential difference / current = constant.
- B potential difference = current \times resistance.
- C current = resistance \times potential difference.
- D current / potential difference = constant.

- (39) A battery is used to:

- A maintain a potential difference.

measure electric potential.

C safeguard against short-circuit.

D measure electric current.

- (40) The unit of resistivity is:

- A ohm·m.
- B ohm/m².
- C ohm.
- D ohm/m.

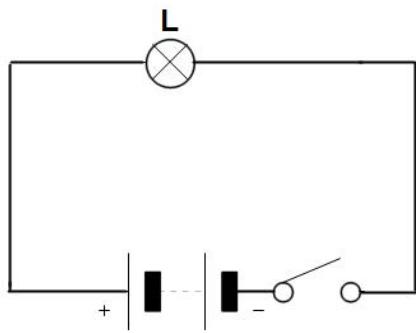


Figura 1

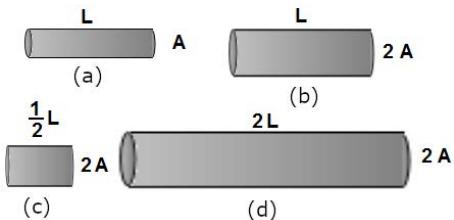


Figura 3

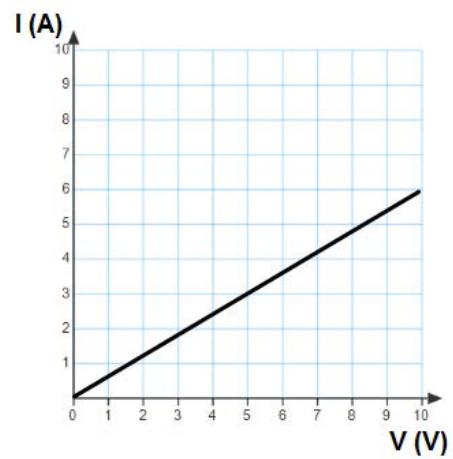


Figura 5

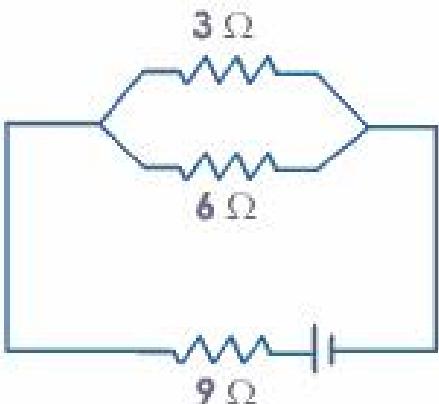


Figura 2

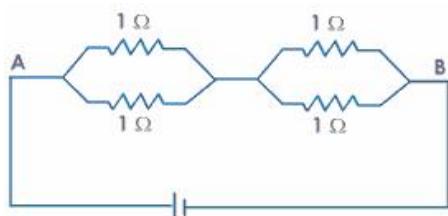


Figura 4

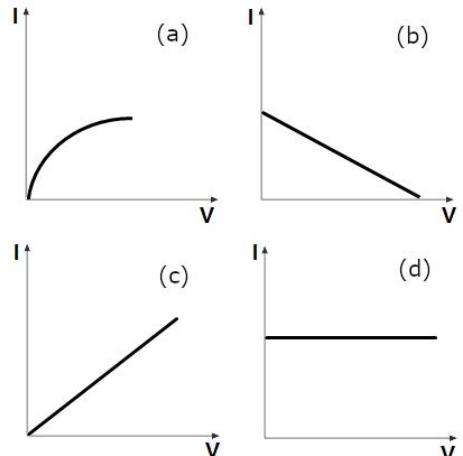


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 4

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.
- [A] Upward.
 [B] Downward.
 [C] To the right.
 [D] To the left.
- (2) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:
- [A] 100 V.
 [B] 40 V.
 [C] 1 V.
 [D] 4 V.
- (3) The unit of electric power is:
- [A] volt.
 [B] watt.
 [C] ampere.
 [D] joule.
- (4) Determine which of the graphs in Figure 2 at the end of the text represents Ohm's law for a solid conductor.
- [A] (c).
 [B] (d).
 [C] (a).
 [D] (b).
- (5) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- [A] 30 J.
 [B] 15 J.
- (6) When there is an electric current passing through a wire, the particles moving are:
- [A] atoms.
 [B] ions.
 [C] electrons.
 [D] protons.
- (7) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- [A] $\frac{R_B}{R_A} = \frac{1}{1}$.
 [B] $\frac{R_B}{R_A} = \frac{1}{4}$.
 [C] $\frac{R_B}{R_A} = \frac{1}{2}$.
 [D] $\frac{R_B}{R_A} = \frac{2}{1}$.
- (8) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:
- [A] 30 Ω .
 [B] 10 Ω .
 [C] 270 Ω .
 [D] 810 Ω .
- (9) The unit of resistivity is:
- [A] ohm.
 [B] ohm/m.
 [C] ohm/m².
 [D] ohm·m.

- (10) All of the wires in Figure 3 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (b).
 B (c).
 C (d).
 D (a).
- (11) Determine which one of the following statements concerning resistors in series is *true*.
- A The power dissipated by each resistor is the same.
 B The voltage across each resistor is the same.
 C The current through each resistor is the same.
 D The total current through the resistors is the sum of the current through each resistor.
- (12) The unit of current is:
- A volt.
 B watt.
 C ampere.
 D coulomb.
- (13) Determine which one of the following statements concerning resistors in parallel is *true*.
- A The voltage across each resistor is the same.
 B The total voltage across the resistors is the sum of the voltage across each resistor.
 C The power dissipated by each resistor is the same.
 D The current through each resistor is the same.
- (14) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:
- A all in series.
 B $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
 C $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
 D all in parallel.
- (15) Complete the following statement: "The electromotive force is:
 A the maximum electric potential energy stored within a battery".
 B the maximum potential difference between the terminals of a battery".
 C the force that accelerates electrons through a wire when a battery is connected to it".
 D the force that accelerates protons through a wire when a battery is connected to it".
- (16) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- A 10 W.
- B 20 W.
 C 15 W.
 D 5 W.
- (17) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.
- A $1\ \Omega$.
 B $6\ \Omega$.
 C $3\ \Omega$.
 D $2\ \Omega$.
- (18) Joule/coulomb is same as:
- A ampere.
 B volt.
 C watt.
 D ohm.
- (19) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- A Current.
 B Voltage.
 C Power.
 D Resistance.
- (20) In Figure 5 at the end of the text, the resistance across AB is:
- A $2\ \Omega$.
 B $0.5\ \Omega$.
 C $4\ \Omega$.
 D $1\ \Omega$.
- (21) In Figure 6 at the end of the text,
- A $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 B $3\ \Omega$, $6\ \Omega$ and Ω are in parallel.
 C $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 D $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
- (22) A $10\ A$ current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 200 C.
 B 600 C.
 C 500 C.
 D 400 C.
- (23) A battery is used to:
- A maintain a potential difference.
 B measure electric current.
 C measure electric potential.
 D safeguard against short-circuit.

- (24) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- [A] 36.
 [B] 2.2×10^{20} .
 [C] 4.8×10^{15} .
 [D] 6.4×10^{18} .
- (25) A positive charge released from rest:
- [A] moves towards the regions of lower potential.
 [B] does not move.
 [C] moves towards the regions of higher potential.
 [D] moves towards the regions of equal potential.
- (26) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- [A] $R = \frac{\rho L}{A}$.
 [B] $R = \frac{\rho A}{L}$.
 [C] $R = \frac{A}{\rho L}$.
 [D] $R = \frac{L}{\rho A}$.
- (27) Ohm's law relates potential difference with:
- [A] current.
 [B] energy.
 [C] power.
 [D] time.
- (28) The resistivity of a wire depends on:
- [A] area of cross-section.
 [B] length, material and area of cross-section.
 [C] material.
 [D] length.
- (29) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- [A] 2Ω .
 [B] 1Ω .
 [C] 6Ω .
 [D] 3Ω .
- (30) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the resistance of the wire.
- [A] 0.8Ω .
 [B] 1.7Ω .
 [C] 0.4Ω .
 [D] 1Ω .
- (31) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:
- [A] 25Ω .
 [B] 0Ω .
 [C] 100Ω .
 [D] 50Ω .
- (32) Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:
- [A] 0Ω .
 [B] 25Ω .
 [C] 50Ω .
 [D] 100Ω .
- (33) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 5 W.
 [B] 0.5 W.
 [C] 2 W.
 [D] 0.2 W.
- (34) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- [A] $D \cdot F$.
 [B] $D \cdot F^2$.
 [C] $D^2 \cdot F$.
 [D] D^2/F .
- (35) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- [A] power.
 [B] current.
 [C] potential difference.
 [D] resistance.
- (36) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] D^2/P .
 [B] $D \cdot P^2$.
 [C] $D \cdot P$.
 [D] $D^2 \cdot P$.
- (37) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- [A] $I^2 R/t$.
 [B] $IR^2 t$.
 [C] $I^2 R t$.
 [D] IRt .

- (38) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- A $\frac{R_Y}{R_X} = \frac{1}{1}$.
- B $\frac{R_Y}{R_X} = \frac{2}{1}$.
- C $\frac{R_Y}{R_X} = \frac{1}{2}$.
- D $\frac{R_Y}{R_X} = \frac{1}{4}$.
- (39) The current in a wire:
- A depends on both resistance and potential difference.
- B does not depend on resistance and potential difference.
- C depends only on the potential difference applied.
- D depends only on the resistance of the wire.
- (40) Determine which of the following statements does not represent Ohm's law.
- A current = resistance \times potential difference.
- B current / potential difference = constant.
- C potential difference = current \times resistance.
- D potential difference / current = constant.

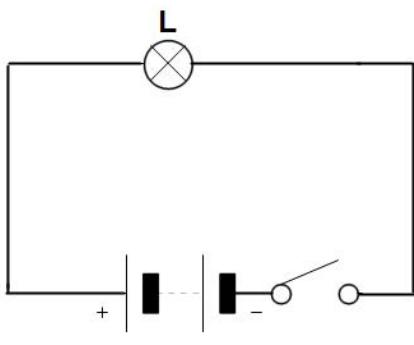


Figura 1

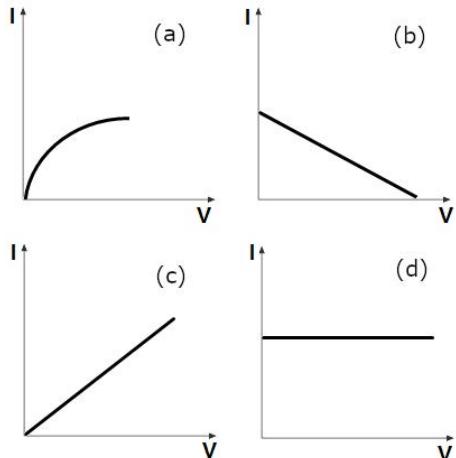


Figura 2

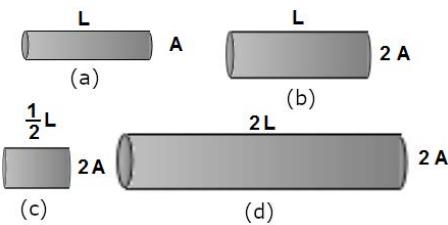


Figura 3

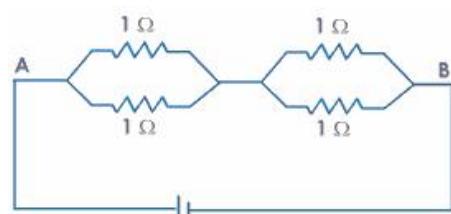


Figura 5

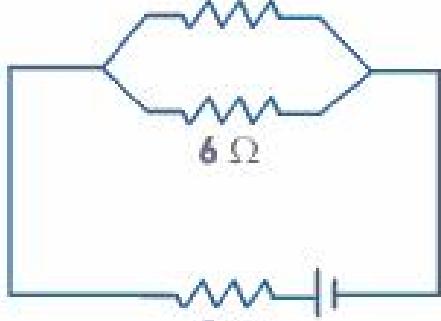


Figura 6

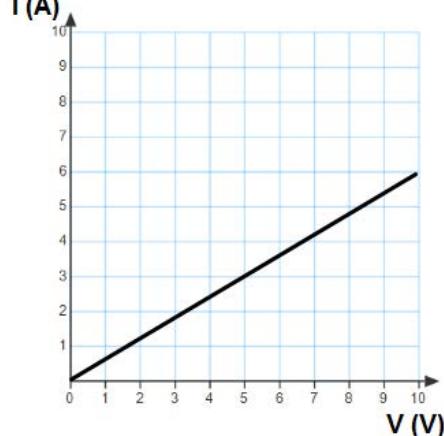


Figura 4

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 5

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																				
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	

- ① Complete the following statement: “The electromotive force is:
- A the maximum electric potential energy stored within a battery”.
 - B the maximum potential difference between the terminals of a battery”.
 - C the force that accelerates electrons through a wire when a battery is connected to it”.
 - D the force that accelerates protons through a wire when a battery is connected to it”.
- ② All of the wires in Figure 1 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (c).
 - B (b).
 - C (d).
 - D (a).
- ③ When there is an electric current passing through a wire, the particles moving are:
- A protons.
 - B atoms.
 - C electrons.
 - D ions.
- ④ The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 2 W.
 - B 5 W.
 - C 0.2 W.
 - D 0.5 W.
- ⑤ Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- ⑥ If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D^2 \cdot F$.
 - B $D \cdot F^2$.
 - C $D \cdot F$.
 - D D^2/F .
- ⑦ Ohm’s law relates potential difference with:
- A power.
 - B current.
 - C energy.
 - D time.
- ⑧ The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A power.
 - B potential difference.
 - C current.
 - D resistance.
- ⑨ In Figure 2 at the end of the text, the resistance across AB is:
- A 2 Ω .
 - B 1 Ω .
 - C 0.5 Ω .
 - D 4 Ω .
- ⑩ Two resistances of 100 Ω and zero ohm are connected in parallel. The overall resistance will be:

- A 100 Ω .
 B 0 Ω .
 C 50 Ω .
 D 25 Ω .

(11) Joule/coulomb is same as:

- A watt.
 B ampere.
 C volt.
 D ohm.

(12) In Figure 3 at the end of the text,

- A 6 Ω , 3 Ω and 9 Ω are in series.
 B 3 Ω , 6 Ω are in parallel and 9 Ω is in series.
 C 3 Ω , 6 Ω and 9 Ω are in parallel.
 D 9 Ω and 6 Ω are in parallel and the combination is in series with 3 Ω .

(13) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A 3 Ω .
 B 1 Ω .
 C 6 Ω .
 D 2 Ω .

(14) The unit of current is:

- A ampere.
 B volt.
 C coulomb.
 D watt.

(15) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:

- A 100 V.
 B 40 V.
 C 4 V.
 D 1 V.

(16) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the resistance of the wire.

- A 1 Ω .
 B 0.8 Ω .
 C 1.7 Ω .
 D 0.4 Ω .

(17) Determine which one of the following statements concerning resistors in series is *true*.

- A The current through each resistor is the same.
 B The power dissipated by each resistor is the same.

- C The voltage across each resistor is the same.

- D The total current through the resistors is the sum of the current through each resistor.

(18) Determine which of the graphs in Figure 5 at the end of the text represents Ohm's law for a solid conductor.

- A (a).
 B (c).
 C (d).
 D (b).

(19) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A $D^2 \cdot P$.
 B $D \cdot P^2$.
 C $D \cdot P$.
 D D^2/P .

(20) A positive charge released from rest:

- A moves towards the regions of equal potential.
 B moves towards the regions of higher potential.
 C does not move.
 D moves towards the regions of lower potential.

(21) Two resistances of 100 Ω and zero ohm are connected in series. The overall resistance will be:

- A 100 Ω .
 B 50 Ω .
 C 25 Ω .
 D 0 Ω .

(22) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- A 5 W.
 B 20 W.
 C 15 W.
 D 10 W.

(23) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- A $\frac{R_Y}{R_X} = \frac{1}{1}$.
 B $\frac{R_Y}{R_X} = \frac{2}{1}$.
 C $\frac{R_Y}{R_X} = \frac{1}{2}$.
 D $\frac{R_Y}{R_X} = \frac{1}{4}$.

(24) Three resistors 2 Ω , 3 Ω and 4 Ω are connected so that the equivalent resistance is 9 Ω . The resistors are connected:

- A all in parallel.

- (B) 2 Ω and 3 Ω in series and the combination in parallel to 4 Ω .
- (C) all in series.
- (D) 2 Ω and 3 Ω in parallel and the combination in series with 4 Ω .
- (25) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- (A) 1 Ω .
- (B) 3 Ω .
- (C) 6 Ω .
- (D) 2 Ω .
- (26) Determine which of the following statements does not represent Ohm's law.
- (A) current / potential difference = constant.
- (B) potential difference / current = constant.
- (C) current = resistance \times potential difference.
- (D) potential difference = current \times resistance.
- (27) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 6 at the end of the text.
- (A) Downward.
- (B) To the left.
- (C) To the right.
- (D) Upward.
- (28) The current in a wire:
- (A) does not depend on resistance and potential difference.
- (B) depends on both resistance and potential difference.
- (C) depends only on the potential difference applied.
- (D) depends only on the resistance of the wire.
- (29) Determine which one of the following statements concerning resistors in parallel is *true*.
- (A) The voltage across each resistor is the same.
- (B) The power dissipated by each resistor is the same.
- (C) The current through each resistor is the same.
- (D) The total voltage across the resistors is the sum of the voltage across each resistor.
- (30) The resistivity of a wire depends on:
- (A) material.
- (B) length.
- (C) length, material and area of cross-section.
- (D) area of cross-section.
- (31) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- (A) Power.
- (B) Voltage.
- (C) Current.
- (D) Resistance.
- (32) The unit of electric power is:
- (A) watt.
- (B) joule.
- (C) ampere.
- (D) volt.
- (33) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- (A) 600 C.
- (B) 500 C.
- (C) 400 C.
- (D) 200 C.
- (34) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- (A) 15 J.
- (B) 30 J.
- (C) 60 J.
- (D) 120 J.
- (35) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:
- (A) 30 Ω .
- (B) 270 Ω .
- (C) 10 Ω .
- (D) 810 Ω .
- (36) The unit of resistivity is:
- (A) ohm/m.
- (B) ohm \cdot m.
- (C) ohm.
- (D) ohm/m².
- (37) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- (A) $R = \frac{\rho L}{A}$.
- (B) $R = \frac{\rho A}{L}$.
- (C) $R = \frac{L}{\rho A}$.
- (D) $R = \frac{A}{\rho L}$.
- (38) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

- [A] $\frac{R_B}{R_A} = \frac{1}{4}$.
 [B] $\frac{R_B}{R_A} = \frac{2}{1}$.
 [C] $\frac{R_B}{R_A} = \frac{1}{1}$.
 [D] $\frac{R_B}{R_A} = \frac{1}{2}$.

(39) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- [A] IR^2t .

- [B] I^2Rt .
 [C] I^2R/t .
 [D] IRt .

(40) A battery is used to:

- [A] measure electric potential.
 [B] safeguard against short-circuit.
 [C] maintain a potential difference.
 [D] measure electric current.

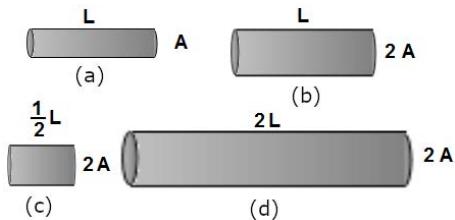


Figura 1

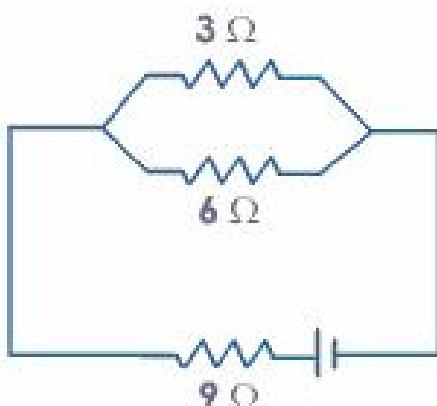


Figura 3

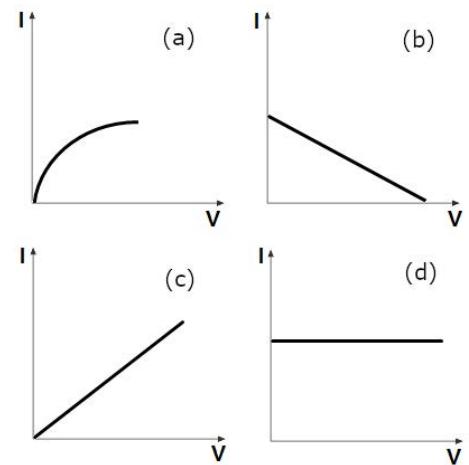


Figura 5

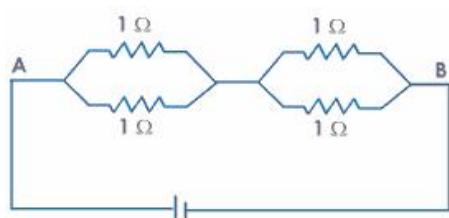


Figura 2

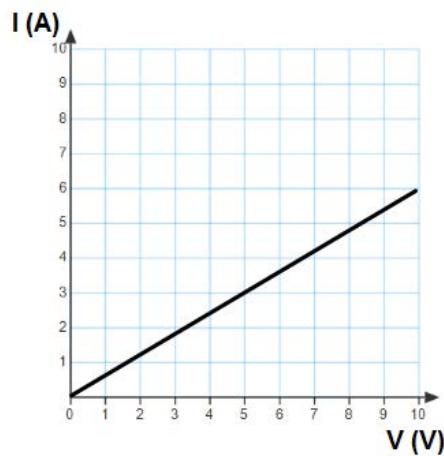


Figura 4

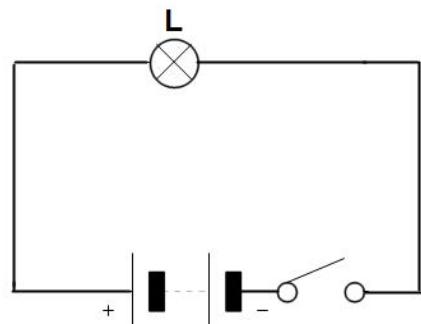


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 6

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																				
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	

1) The current in a wire:

- A depends on both resistance and potential difference.
- B does not depend on resistance and potential difference.
- C depends only on the potential difference applied.
- D depends only on the resistance of the wire.

2) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- A $R = \frac{A}{\rho L}$.
- B $R = \frac{\rho L}{A}$.
- C $R = \frac{L}{\rho A}$.
- D $R = \frac{\rho A}{L}$.

3) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:

- A 100Ω .
- B 0Ω .
- C 50Ω .
- D 25Ω .

4) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 200 C .
- B 400 C .
- C 600 C .
- D 500 C .

5) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

A power.

B potential difference.

C resistance.

D current.

6) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

- A all in series.
- B 2Ω and 3Ω in parallel and the combination in series with 4Ω .
- C 2Ω and 3Ω in series and the combination in parallel to 4Ω .
- D all in parallel.

7) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A D^2/F .
- B $D \cdot F^2$.
- C $D^2 \cdot F$.
- D $D \cdot F$.

8) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A $D^2 \cdot P$.
- B D^2/P .
- C $D \cdot P$.
- D $D \cdot P^2$.

9) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

- A 1Ω .
- B 2Ω .
- C 6Ω .

D 3Ω .

- (10) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 2Ω .
 B 1Ω .
 C 3Ω .
 D 6Ω .

- (11) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

A 0.2 W.
 B 5 W.
 C 0.5 W.
 D 2 W.

- (12) Determine which one of the following statements concerning resistors in parallel is *true*.

A The total voltage across the resistors is the sum of the voltage across each resistor.
 B The voltage across each resistor is the same.
 C The power dissipated by each resistor is the same.
 D The current through each resistor is the same.

- (13) Determine which of the following statements does not represent Ohm's law.

A $\text{current} = \text{resistance} \times \text{potential difference}$.
 B $\text{potential difference} / \text{current} = \text{constant}$.
 C $\text{current} / \text{potential difference} = \text{constant}$.
 D $\text{potential difference} = \text{current} \times \text{resistance}$.

- (14) Joule/coulomb is same as:

A watt.
 B ampere.
 C volt.
 D ohm.

- (15) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

A 100 V.
 B 40 V.
 C 4 V.
 D 1 V.

- (16) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{2}{1}$.
 B $\frac{R_B}{R_A} = \frac{1}{2}$.

C $\frac{R_B}{R_A} = \frac{1}{4}$.

D $\frac{R_B}{R_A} = \frac{1}{1}$.

- (17) The resistivity of a wire depends on:

A length, material and area of cross-section.
 B length.
 C area of cross-section.
 D material.

- (18) When there is an electric current passing through a wire, the particles moving are:

A ions.
 B protons.
 C atoms.
 D electrons.

- (19) In Figure 1 at the end of the text,

A 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
 B 3Ω , 6Ω and Ω are in parallel.
 C 3Ω , 6Ω are in parallel and 9Ω is in series.
 D 6Ω , 3Ω and 9Ω are in series.

- (20) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{2}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{2}$.
 C $\frac{R_Y}{R_X} = \frac{1}{4}$.
 D $\frac{R_Y}{R_X} = \frac{1}{1}$.

- (21) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the power dissipated in the resistor when the applied voltage is 5 V.

A 20 W.
 B 5 W.
 C 10 W.
 D 15 W.

- (22) Complete the following statement: "The electromotive force is:

A the maximum electric potential energy stored within a battery".
 B the maximum potential difference between the terminals of a battery".
 C the force that accelerates electrons through a wire when a battery is connected to it".
 D the force that accelerates protons through a wire when a battery is connected to it".

(23) Determine which one of the following statements concerning resistors in series is *true*.

- [A] The voltage across each resistor is the same.
- [B] The power dissipated by each resistor is the same.
- [C] The current through each resistor is the same.
- [D] The total current through the resistors is the sum of the current through each resistor.

(24) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

- [A] $50\ \Omega$.
- [B] $100\ \Omega$.
- [C] $0\ \Omega$.
- [D] $25\ \Omega$.

(25) The unit of resistivity is:

- [A] ohm/m^2 .
- [B] ohm/m .
- [C] ohm .
- [D] $\text{ohm}\cdot\text{m}$.

(26) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- [A] 120 J.
- [B] 30 J.
- [C] 60 J.
- [D] 15 J.

(27) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.

- [A] (c).
- [B] (d).
- [C] (b).
- [D] (a).

(28) The unit of current is:

- [A] ampere.
- [B] coulomb.
- [C] volt.
- [D] watt.

(29) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 4 at the end of the text.

- [A] Upward.
- [B] To the right.
- [C] Downward.
- [D] To the left.

(30) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- [A] I^2Rt .
- [B] IRt .
- [C] IR^2t .
- [D] I^2R/t .

(31) A battery is used to:

- [A] maintain a potential difference.
- [B] measure electric current.
- [C] safeguard against short-circuit.
- [D] measure electric potential.

(32) In Figure 5 at the end of the text, the resistance across AB is:

- [A] $1\ \Omega$.
- [B] $4\ \Omega$.
- [C] $2\ \Omega$.
- [D] $0.5\ \Omega$.

(33) All of the wires in Figure 6 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- [A] (b).
- [B] (c).
- [C] (d).
- [D] (a).

(34) A positive charge released from rest:

- [A] moves towards the regions of lower potential.
- [B] moves towards the regions of higher potential.
- [C] does not move.
- [D] moves towards the regions of equal potential.

(35) The unit of electric power is:

- [A] watt.
- [B] joule.
- [C] volt.
- [D] ampere.

(36) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

- [A] 36.
- [B] 2.2×10^{20} .
- [C] 6.4×10^{18} .
- [D] 4.8×10^{15} .

(37) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- [A] Current.
- [B] Power.
- [C] Resistance.
- [D] Voltage.

(38) Ohm's law relates potential difference with:

- A current.
- B power.
- C energy.
- D time.

(39) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the resistance of the wire.

- A 0.8Ω .
- B 0.4Ω .

C 1.7Ω .

D 1Ω .

(40) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:

- A 270Ω .
- B 30Ω .
- C 810Ω .
- D 10Ω .

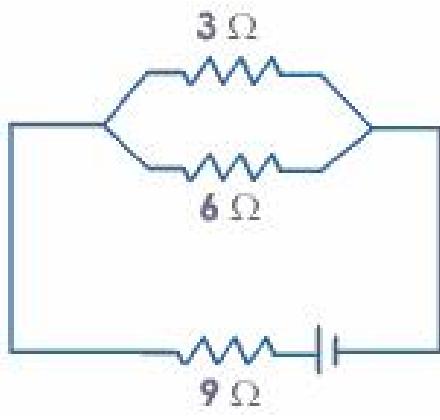


Figura 1

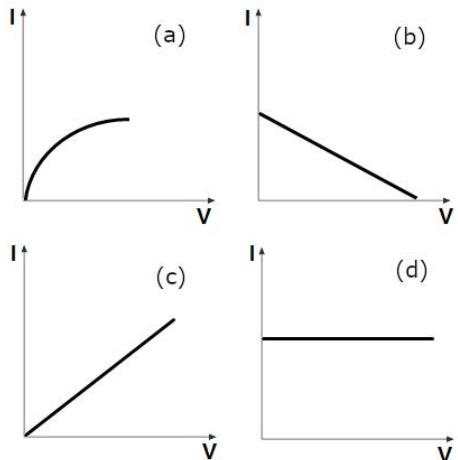


Figura 3

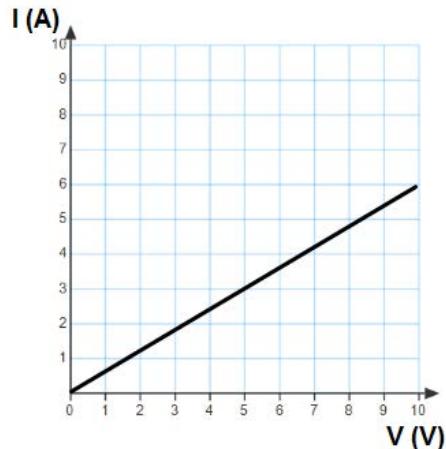


Figura 2

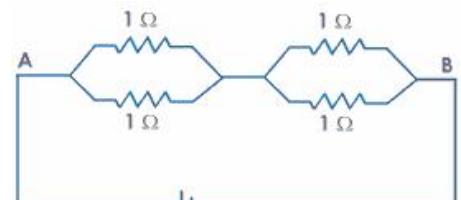


Figura 5

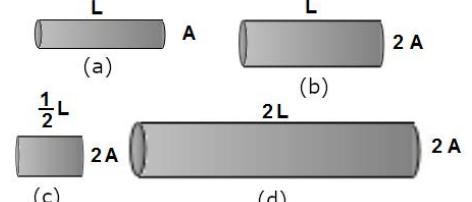


Figura 6

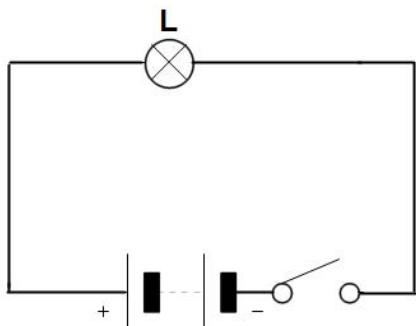


Figura 4

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 7

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] D^2/P .
 [B] $D \cdot P$.
 [C] $D \cdot P^2$.
 [D] $D^2 \cdot P$.
- ② A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- [A] 200 C.
 [B] 500 C.
 [C] 400 C.
 [D] 600 C.
- ③ Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.
- [A] To the left.
 [B] Downward.
 [C] To the right.
 [D] Upward.
- ④ The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 5 W.
 [B] 0.2 W.
 [C] 0.5 W.
 [D] 2 W.
- ⑤ Two resistances of 100 Ω and zero ohm are connected in parallel. The overall resistance will be:
- [A] 50 Ω .
- ⑥ Determine which of the graphs in Figure 2 at the end of the text represents Ohm's law for a solid conductor.
- [A] (b).
 [B] (c).
 [C] (d).
 [D] (a).
- ⑦ Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- [A] 36.
 [B] 6.4×10^{18} .
 [C] 4.8×10^{15} .
 [D] 2.2×10^{20} .
- ⑧ The unit of electric power is:
- [A] ampere.
 [B] volt.
 [C] watt.
 [D] joule.
- ⑨ The unit of resistivity is:
- [A] ohm/m².
 [B] ohm-m.
 [C] ohm/m.
 [D] ohm.
- ⑩ Joule/coulomb is same as:
- [A] ohm.
 [B] watt.

C ampere.

D volt.

- (11) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:

A 4 V.
 B 100 V.
 C 40 V.
 D 1 V.

- (12) All of the wires in Figure 3 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (c).
 B (b).
 C (a).
 D (d).

- (13) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{\rho L}{A}$.
 B $R = \frac{\rho A}{L}$.
 C $R = \frac{L}{\rho A}$.
 D $R = \frac{A}{\rho L}$.

- (14) Determine which of the following statements does not represent Ohm's law.

A current = resistance \times potential difference.
 B potential difference / current = constant.
 C current / potential difference = constant.
 D potential difference = current \times resistance.

- (15) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

A 15 J.
 B 30 J.
 C 60 J.
 D 120 J.

- (16) In Figure 4 at the end of the text, the resistance across AB is:

A 0.5 Ω .
 B 4 Ω .
 C 2 Ω .
 D 1 Ω .

- (17) Three resistors 2 Ω , 3 Ω and 4 Ω are connected so that the equivalent resistance is 9 Ω . The resistors are connected:

A all in series.

B 2 Ω and 3 Ω in series and the combination in parallel to 4 Ω .

C 2 Ω and 3 Ω in parallel and the combination in series with 4 Ω .

D all in parallel.

- (18) The current in a wire:

A does not depend on resistance and potential difference.
 B depends only on the potential difference applied.
 C depends only on the resistance of the wire.
 D depends on both resistance and potential difference.

- (19) A battery is used to:

A measure electric current.
 B measure electric potential.
 C safeguard against short-circuit.
 D maintain a potential difference.

- (20) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{1}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{2}$.
 C $\frac{R_Y}{R_X} = \frac{2}{1}$.
 D $\frac{R_Y}{R_X} = \frac{1}{4}$.

- (21) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{1}{4}$.
 B $\frac{R_B}{R_A} = \frac{1}{2}$.
 C $\frac{R_B}{R_A} = \frac{1}{1}$.
 D $\frac{R_B}{R_A} = \frac{2}{1}$.

- (22) Complete the following statement: "The electromotive force is:

A the force that accelerates protons through a wire when a battery is connected to it".
 B the maximum potential difference between the terminals of a battery".
 C the force that accelerates electrons through a wire when a battery is connected to it".
 D the maximum electric potential energy stored within a battery".

- (23) Determine which one of the following statements concerning resistors in series is true.

A The power dissipated by each resistor is the same.

- (B) The voltage across each resistor is the same.
 (C) The current through each resistor is the same.
 (D) The total current through the resistors is the sum of the current through each resistor.
- (24) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the power dissipated in the resistor when the applied voltage is 5 V.
 (A) 20 W.
 (B) 10 W.
 (C) 15 W.
 (D) 5 W.
- (25) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
 (A) $D \cdot F$.
 (B) $D \cdot F^2$.
 (C) D^2/F .
 (D) $D^2 \cdot F$.
- (26) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
 (A) $810\ \Omega$.
 (B) $270\ \Omega$.
 (C) $30\ \Omega$.
 (D) $10\ \Omega$.
- (27) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.
 (A) $2\ \Omega$.
 (B) $6\ \Omega$.
 (C) $3\ \Omega$.
 (D) $1\ \Omega$.
- (28) When there is an electric current passing through a wire, the particles moving are:
 (A) protons.
 (B) electrons.
 (C) atoms.
 (D) ions.
- (29) A positive charge released from rest:
 (A) moves towards the regions of equal potential.
 (B) moves towards the regions of lower potential.
 (C) does not move.
 (D) moves towards the regions of higher potential.
- (30) The resistivity of a wire depends on:
 (A) material.
- (B) length, material and area of cross-section.
 (C) length.
 (D) area of cross-section.
- (31) In Figure 6 at the end of the text,
 (A) $3\ \Omega$, $6\ \Omega$ and Ω are in parallel.
 (B) $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 (C) $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 (D) $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
- (32) Ohm's law relates potential difference with:
 (A) power.
 (B) current.
 (C) time.
 (D) energy.
- (33) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
 (A) $0\ \Omega$.
 (B) $25\ \Omega$.
 (C) $50\ \Omega$.
 (D) $100\ \Omega$.
- (34) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
 (A) Power.
 (B) Voltage.
 (C) Current.
 (D) Resistance.
- (35) Determine which one of the following statements concerning resistors in parallel is *true*.
 (A) The total voltage across the resistors is the sum of the voltage across each resistor.
 (B) The voltage across each resistor is the same.
 (C) The current through each resistor is the same.
 (D) The power dissipated by each resistor is the same.
- (36) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the resistance of the wire.
 (A) $0.8\ \Omega$.
 (B) $1\ \Omega$.
 (C) $0.4\ \Omega$.
 (D) $1.7\ \Omega$.
- (37) When a current I flows through a resistance R for time t the electrical energy spent is given by:
 (A) IRt .
 (B) I^2R/t .
 (C) I^2Rt .

D IR^2t .

- (38) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A power.
- B current.
- C resistance.
- D potential difference.

- (39) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 6Ω .

B 1Ω .

C 2Ω .

D 3Ω .

- (40) The unit of current is:

- A watt.
- B volt.
- C coulomb.
- D ampere.

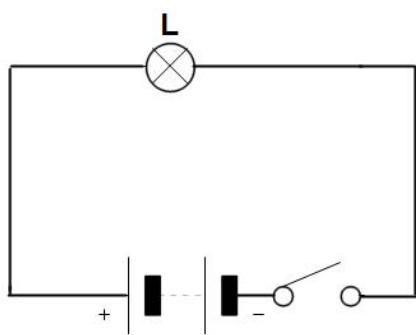


Figura 1

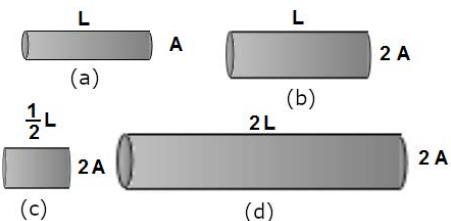


Figura 3

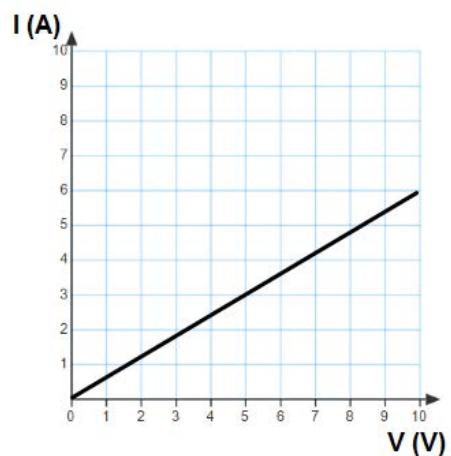


Figura 5

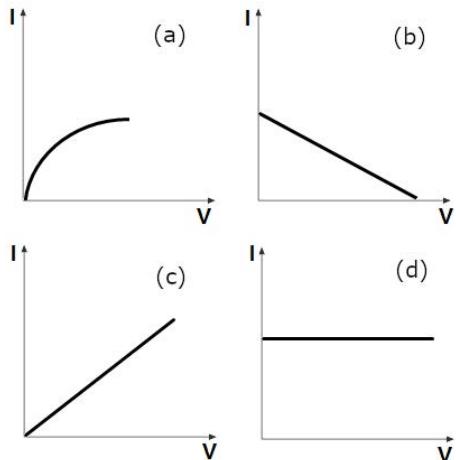


Figura 2

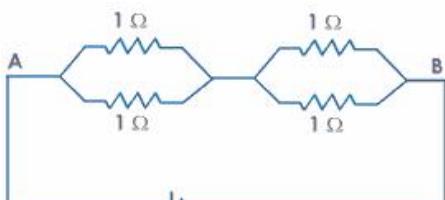


Figura 4

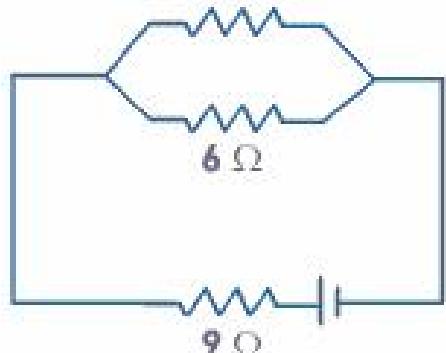


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 8

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① The unit of electric power is:
- A watt.
B ampere.
C volt.
D joule.
- ② Determine which one of the following statements concerning resistors in series is *true*.
- A The current through each resistor is the same.
B The power dissipated by each resistor is the same.
C The total current through the resistors is the sum of the current through each resistor.
D The voltage across each resistor is the same.
- ③ Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- A $\frac{R_Y}{R_X} = \frac{1}{4}$.
B $\frac{R_Y}{R_X} = \frac{1}{2}$.
C $\frac{R_Y}{R_X} = \frac{2}{1}$.
D $\frac{R_Y}{R_X} = \frac{1}{1}$.
- ④ Determine which of the following statements does not represent Ohm's law.
- A current / potential difference = constant.
B potential difference = current \times resistance.
C potential difference / current = constant.
D current = resistance \times potential difference.
- ⑤ Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- ⑥ The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- A 15 W.
B 5 W.
C 10 W.
D 20 W.
- ⑦ A positive charge released from rest:
- A moves towards the regions of higher potential.
B moves towards the regions of equal potential.
C does not move.
D moves towards the regions of lower potential.
- ⑧ Complete the following statement: “The electromotive force is:
- A the maximum electric potential energy stored within a battery”.
B the maximum potential difference between the terminals of a battery”.
C the force that accelerates electrons through a wire when a battery is connected to it”.
D the force that accelerates protons through a wire when a battery is connected to it”.
- ⑨ In Figure 2 at the end of the text, the resistance across AB is:
- A 1 Ω .
B 2 Ω .
C 4 Ω .

D 0.5Ω .

- (10) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

A power.
 B resistance.
 C potential difference.
 D current.

- (11) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

A 500 C.
 B 400 C.
 C 600 C.
 D 200 C.

- (12) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 3 at the end of the text.

A Downward.
 B To the right.
 C Upward.
 D To the left.

- (13) Determine which of the graphs in Figure 4 at the end of the text represents Ohm's law for a solid conductor.

A (c).
 B (b).
 C (a).
 D (d).

- (14) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

A D^2/P .
 B $D \cdot P$.
 C $D^2 \cdot P$.
 D $D \cdot P^2$.

- (15) Determine which one of the following statements concerning resistors in parallel is *true*.

A The power dissipated by each resistor is the same.
 B The current through each resistor is the same.
 C The total voltage across the resistors is the sum of the voltage across each resistor.
 D The voltage across each resistor is the same.

- (16) When a current I flows through a resistance R for time t the electrical energy spent is given by:

A I^2R/t .
 B IRt .

C IR^2t .

D I^2Rt .

- (17) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

A all in series.
 B all in parallel.
 C 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 D 2Ω and 3Ω in series and the combination in parallel to 4Ω .

- (18) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

A D^2/F .
 B $D \cdot F^2$.
 C $D \cdot F$.
 D $D^2 \cdot F$.

- (19) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 3Ω .
 B 1Ω .
 C 6Ω .
 D 2Ω .

- (20) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A . Determine how the resistance of wire B compares to the resistance of wire A .

A $\frac{R_B}{R_A} = \frac{1}{2}$.
 B $\frac{R_B}{R_A} = \frac{2}{1}$.
 C $\frac{R_B}{R_A} = \frac{1}{4}$.
 D $\frac{R_B}{R_A} = \frac{1}{1}$.

- (21) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{\rho L}{A}$.
 B $R = \frac{L}{\rho A}$.
 C $R = \frac{A}{\rho L}$.
 D $R = \frac{\rho A}{L}$.

- (22) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

A 6Ω .
 B 1Ω .
 C 2Ω .
 D 3Ω .

- (23) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
- A $25\ \Omega$.
 B $0\ \Omega$.
 C $50\ \Omega$.
 D $100\ \Omega$.
- (24) A battery is used to:
- A measure electric potential.
 B measure electric current.
 C safeguard against short-circuit.
 D maintain a potential difference.
- (25) The resistivity of a wire depends on:
- A area of cross-section.
 B length.
 C length, material and area of cross-section.
 D material.
- (26) Ohm's law relates potential difference with:
- A time.
 B energy.
 C current.
 D power.
- (27) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- A Current.
 B Resistance.
 C Power.
 D Voltage.
- (28) The potential difference required to pass a current $0.2\ A$ in a wire of resistance $20\ \Omega$ is:
- A $4\ V$.
 B $40\ V$.
 C $100\ V$.
 D $1\ V$.
- (29) In Figure 5 at the end of the text,
- A $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 B $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 C $3\ \Omega$, $6\ \Omega$ and Ω are in parallel.
 D $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
- (30) All of the wires in Figure 6 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (c).
- B (a).
 C (b).
 D (d).
- (31) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- A $50\ \Omega$.
 B $0\ \Omega$.
 C $100\ \Omega$.
 D $25\ \Omega$.
- (32) The current in a wire:
- A does not depend on resistance and potential difference.
 B depends on both resistance and potential difference.
 C depends only on the resistance of the wire.
 D depends only on the potential difference applied.
- (33) The unit of resistivity is:
- A ohm·m.
 B ohm/m².
 C ohm/m.
 D ohm.
- (34) Joule/coulomb is same as:
- A ohm.
 B watt.
 C volt.
 D ampere.
- (35) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.
- A $1\ \Omega$.
 B $0.8\ \Omega$.
 C $1.7\ \Omega$.
 D $0.4\ \Omega$.
- (36) When there is an electric current passing through a wire, the particles moving are:
- A protons.
 B atoms.
 C ions.
 D electrons.
- (37) The unit of current is:
- A volt.
 B watt.
 C coulomb.
 D ampere.

- (38) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- [A] 30 J.
 [B] 120 J.
 [C] 15 J.
 [D] 60 J.
- (39) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- [A] $30\ \Omega$.
- (40) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 5 W.
 [B] 2 W.
 [C] 0.5 W.
 [D] 0.2 W.

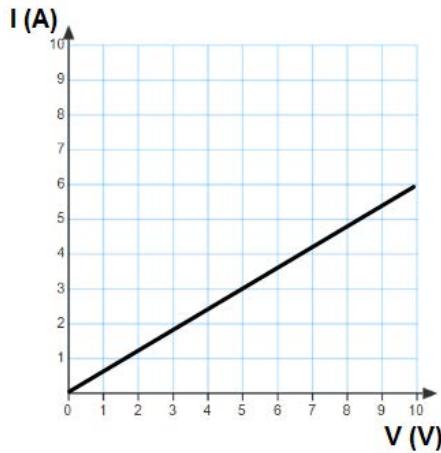


Figura 1

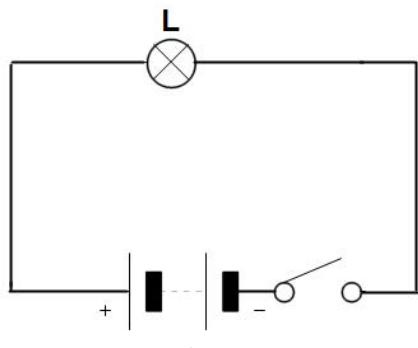


Figura 3

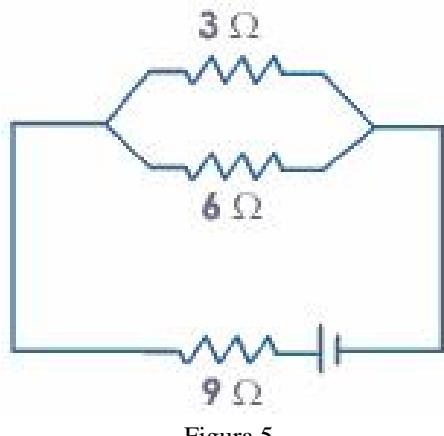


Figura 5

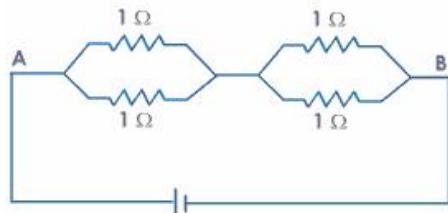


Figura 2

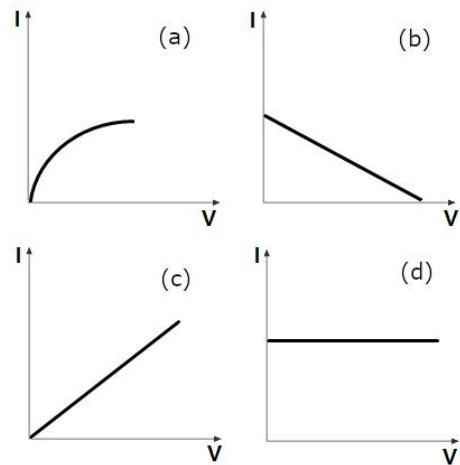


Figura 4

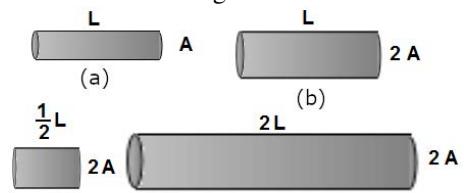


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 9

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 3Ω .
 [B] 6Ω .
 [C] 2Ω .
 [D] 1Ω .
- ② In Figure 1 at the end of the text,
- [A] 3Ω , 6Ω are in parallel and 9Ω is in series.
 [B] 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
 [C] 3Ω , 6Ω and 9Ω are in parallel.
 [D] 6Ω , 3Ω and 9Ω are in series.
- ③ Determine which one of the following statements concerning resistors in parallel is *true*.
- [A] The current through each resistor is the same.
 [B] The voltage across each resistor is the same.
 [C] The power dissipated by each resistor is the same.
 [D] The total voltage across the resistors is the sum of the voltage across each resistor.
- ④ Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:
- [A] 100Ω .
 [B] 0Ω .
 [C] 50Ω .
 [D] 25Ω .
- ⑤ When there is an electric current passing through a wire, the particles moving are:
- [A] atoms.
- ⑥ protons.
 [C] electrons.
 [D] ions.
- ⑦ Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .
- [A] 4.8×10^{15} .
 [B] 2.2×10^{20} .
 [C] 36.
 [D] 6.4×10^{18} .
- ⑧ The unit of resistivity is:
- [A] ohm.
 [B] ohm/m.
 [C] ohm/m².
 [D] ohm·m.
- ⑨ Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:
- [A] 10Ω .
 [B] 810Ω .
 [C] 270Ω .
 [D] 30Ω .
- ⑩ If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- [A] $D^2 \cdot F$.
 [B] D^2/F .
 [C] $D \cdot F^2$.
 [D] $D \cdot F$.
- ⑪ The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Current.
- B Voltage.
- C Power.
- D Resistance.

(11) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A I^2R/t .
- B I^2Rt .
- C IR^2t .
- D IRt .

(12) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- A $R = \frac{\rho L}{A}$.
- B $R = \frac{L}{\rho A}$.
- C $R = \frac{A}{\rho L}$.
- D $R = \frac{\rho A}{L}$.

(13) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A resistance.
- B power.
- C current.
- D potential difference.

(14) Ohm's law relates potential difference with:

- A time.
- B current.
- C energy.
- D power.

(15) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A . Determine how the resistance of wire B compares to the resistance of wire A .

- A $\frac{R_B}{R_A} = \frac{1}{1}$.
- B $\frac{R_B}{R_A} = \frac{2}{1}$.
- C $\frac{R_B}{R_A} = \frac{1}{4}$.
- D $\frac{R_B}{R_A} = \frac{1}{2}$.

(16) Determine which one of the following statements concerning resistors in series is true.

- A The power dissipated by each resistor is the same.
- B The voltage across each resistor is the same.

- C The total current through the resistors is the sum of the current through each resistor.
- D The current through each resistor is the same.

(17) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- A 5 W.
- B 0.2 W.
- C 2 W.
- D 0.5 W.

(18) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 200 C.
- B 400 C.
- C 600 C.
- D 500 C.

(19) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:

- A 50Ω .
- B 0Ω .
- C 100Ω .
- D 25Ω .

(20) The current in a wire:

- A depends only on the resistance of the wire.
- B depends only on the potential difference applied.
- C does not depend on resistance and potential difference.
- D depends on both resistance and potential difference.

(21) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the resistance of the wire.

- A 1.7Ω .
- B 0.8Ω .
- C 0.4Ω .
- D 1Ω .

(22) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A $D^2 \cdot P$.
- B D^2/P .
- C $D \cdot P^2$.
- D $D \cdot P$.

(23) The unit of electric power is:

- A ampere.
- B joule.
- C volt.
- D watt.

- (24) The potential difference required to pass a current 0.2 A in a wire of resistance $20\ \Omega$ is:
- [A] 4 V.
 [B] 1 V.
 [C] 100 V.
 [D] 40 V.
- (25) A positive charge released from rest:
- [A] does not move.
 [B] moves towards the regions of equal potential.
 [C] moves towards the regions of lower potential.
 [D] moves towards the regions of higher potential.
- (26) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.
- [A] (b).
 [B] (c).
 [C] (a).
 [D] (d).
- (27) All of the wires in Figure 4 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- [A] (c).
 [B] (d).
 [C] (b).
 [D] (a).
- (28) The unit of current is:
- [A] ampere.
 [B] watt.
 [C] coulomb.
 [D] volt.
- (29) Determine which of the following statements does not represent Ohm's law.
- [A] potential difference = current \times resistance.
 [B] potential difference / current = constant.
 [C] current = resistance \times potential difference.
 [D] current / potential difference = constant.
- (30) The resistivity of a wire depends on:
- [A] area of cross-section.
 [B] length.
 [C] length, material and area of cross-section.
 [D] material.
- (31) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- [A] 120 J.
 [B] 30 J.
 [C] 60 J.
 [D] 15 J.
- (32) Complete the following statement: "The electromotive force is:
- [A] the force that accelerates protons through a wire when a battery is connected to it".
 [B] the force that accelerates electrons through a wire when a battery is connected to it".
 [C] the maximum electric potential energy stored within a battery".
 [D] the maximum potential difference between the terminals of a battery".
- (33) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 5 at the end of the text.
- [A] Downward.
 [B] To the left.
 [C] To the right.
 [D] Upward.
- (34) A battery is used to:
- [A] measure electric potential.
 [B] maintain a potential difference.
 [C] measure electric current.
 [D] safeguard against short-circuit.
- (35) Joule/coulomb is same as:
- [A] volt.
 [B] ampere.
 [C] watt.
 [D] ohm.
- (36) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- [A] 20 W.
 [B] 10 W.
 [C] 15 W.
 [D] 5 W.
- (37) Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- [A] 2 Ω .
 [B] 6 Ω .
 [C] 1 Ω .
 [D] 3 Ω .
- (38) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:

- A 2 Ω and 3 Ω in parallel and the combination in series with 4 Ω .
- B all in series.
- C all in parallel.
- D 2 Ω and 3 Ω in series and the combination in parallel to 4 Ω .

- (39) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{1}{2}$.

- B $\frac{R_Y}{R_X} = \frac{2}{1}$.
- C $\frac{R_Y}{R_X} = \frac{1}{4}$.
- D $\frac{R_Y}{R_X} = \frac{1}{1}$.

- (40) In Figure 6 at the end of the text, the resistance across AB is:

- A 2 Ω .
- B 4 Ω .
- C 1 Ω .
- D 0.5 Ω .

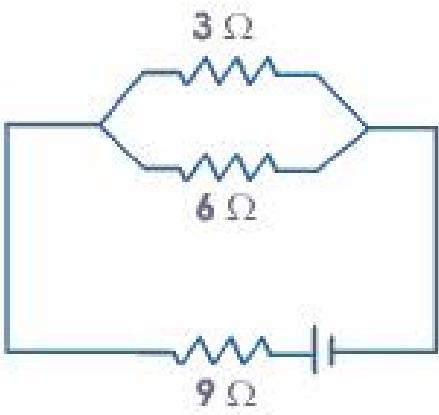


Figura 1

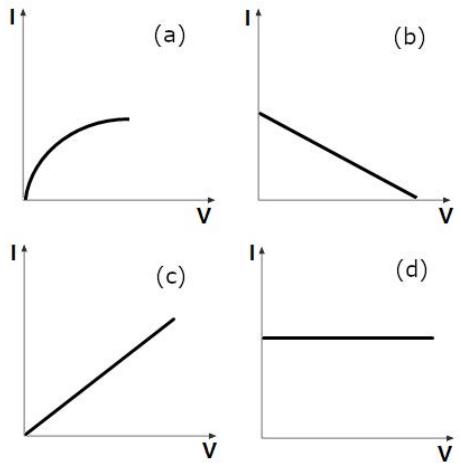


Figura 3

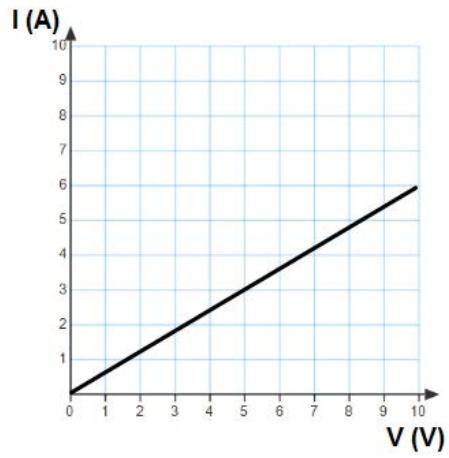


Figura 2

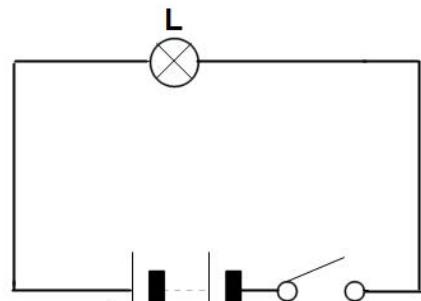


Figura 5

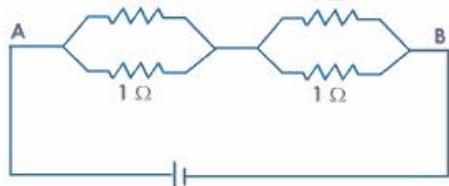


Figura 6

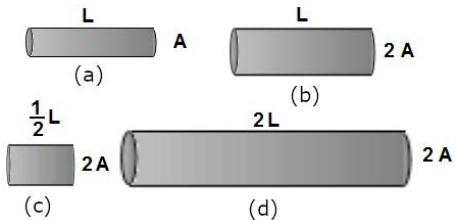


Figura 4

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 10

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① In Figure 1 at the end of the text, the resistance across AB is:
- [A] 1 Ω .
 [B] 4 Ω .
 [C] 2 Ω .
 [D] 0.5 Ω .
- ② Ohm's law relates potential difference with:
- [A] energy.
 [B] power.
 [C] time.
 [D] current.
- ③ When there is an electric current passing through a wire, the particles moving are:
- [A] protons.
 [B] atoms.
 [C] ions.
 [D] electrons.
- ④ When a current I flows through a resistance R for time t the electrical energy spent is given by:
- [A] IRt .
 [B] I^2R/t .
 [C] IR^2t .
 [D] I^2Rt .
- ⑤ A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- [A] 400 C.
 [B] 500 C.
 [C] 600 C.
- ⑥ In Figure 1 at the end of the text, the unit of resistivity is:
- [A] ohm/m.
 [B] ohm.
 [C] ohm/ m^2 .
 [D] ohm·m.
- ⑦ Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- [A] 4.8×10^{15} .
 [B] 36.
 [C] 2.2×10^{20} .
 [D] 6.4×10^{18} .
- ⑧ Determine which one of the following statements concerning resistors in series is *true*.
- [A] The current through each resistor is the same.
 [B] The total current through the resistors is the sum of the current through each resistor.
 [C] The voltage across each resistor is the same.
 [D] The power dissipated by each resistor is the same.
- ⑨ The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the resistance of the wire.
- [A] 0.4 Ω .
 [B] 1 Ω .
 [C] 0.8 Ω .
 [D] 1.7 Ω .
- ⑩ The unit of electric power is:
- [A] joule.
 [B] volt.
 [C] ampere.

D watt.

- (11) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

A $50\ \Omega$.
 B $0\ \Omega$.
 C $100\ \Omega$.
 D $25\ \Omega$.

- (12) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.

A $2\ \Omega$.
 B $6\ \Omega$.
 C $3\ \Omega$.
 D $1\ \Omega$.

- (13) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{L}{\rho A}$.
 B $R = \frac{A}{\rho L}$.
 C $R = \frac{\rho L}{A}$.
 D $R = \frac{\rho A}{L}$.

- (14) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 3 at the end of the text.

A Downward.
 B Upward.
 C To the left.
 D To the right.

- (15) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the power dissipated in the resistor when the applied voltage is $5\ V$.

A $15\ W$.
 B $10\ W$.
 C $20\ W$.
 D $5\ W$.

- (16) Determine which of the following statements does not represent Ohm's law.

A current / potential difference = constant.
 B current = resistance \times potential difference.
 C potential difference / current = constant.
 D potential difference = current \times resistance.

- (17) A battery is used to:

A measure electric potential.

B measure electric current.

C safeguard against short-circuit.

D maintain a potential difference.

- (18) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

A $0\ \Omega$.
 B $50\ \Omega$.
 C $25\ \Omega$.
 D $100\ \Omega$.

- (19) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

A current.
 B power.
 C resistance.
 D potential difference.

- (20) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

A $D \cdot P^2$.
 B D^2/P .
 C $D \cdot P$.
 D $D^2 \cdot P$.

- (21) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:

A $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
 B all in parallel.
 C $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
 D all in series.

- (22) All of the wires in Figure 4 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (a).
 B (d).
 C (b).
 D (c).

- (23) In Figure 5 at the end of the text,

A $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 B $3\ \Omega$, $6\ \Omega$ and $9\ \Omega$ are in parallel.
 C $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 D $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.

- (24) A positive charge released from rest:

A does not move.
 B moves towards the regions of equal potential.

- C moves towards the regions of higher potential.
 D moves towards the regions of lower potential.

(25) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- A $\frac{R_Y}{R_X} = \frac{2}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{2}$.
 C $\frac{R_Y}{R_X} = \frac{1}{1}$.
 D $\frac{R_Y}{R_X} = \frac{1}{4}$.

(26) The current in a wire:

- A depends only on the potential difference applied.
 B depends only on the resistance of the wire.
 C depends on both resistance and potential difference.
 D does not depend on resistance and potential difference.

(27) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Power.
 B Voltage.
 C Resistance.
 D Current.

(28) Determine which of the graphs in Figure 6 at the end of the text represents Ohm's law for a solid conductor.

- A (d).
 B (b).
 C (c).
 D (a).

(29) Complete the following statement: "The electromotive force is:

- A the force that accelerates protons through a wire when a battery is connected to it".
 B the maximum potential difference between the terminals of a battery".
 C the force that accelerates electrons through a wire when a battery is connected to it".
 D the maximum electric potential energy stored within a battery".

(30) Determine which one of the following statements concerning resistors in parallel is *true*.

- A The current through each resistor is the same.
 B The voltage across each resistor is the same.
 C The power dissipated by each resistor is the same.
 D The total voltage across the resistors is the sum of the voltage across each resistor.

(31) The unit of current is:

- A watt.
 B volt.
 C coulomb.
 D ampere.

(32) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A . Determine how the resistance of wire B compares to the resistance of wire A .

- A $\frac{R_B}{R_A} = \frac{2}{1}$.
 B $\frac{R_B}{R_A} = \frac{1}{4}$.
 C $\frac{R_B}{R_A} = \frac{1}{2}$.
 D $\frac{R_B}{R_A} = \frac{1}{1}$.

(33) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:

- A $810\ \Omega$.
 B $30\ \Omega$.
 C $10\ \Omega$.
 D $270\ \Omega$.

(34) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D^2 \cdot F$.
 B D^2/F .
 C $D \cdot F^2$.
 D $D \cdot F$.

(35) Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A $1\ \Omega$.
 B $6\ \Omega$.
 C $3\ \Omega$.
 D $2\ \Omega$.

(36) The resistivity of a wire depends on:

- A material.
 B area of cross-section.
 C length, material and area of cross-section.
 D length.

(37) The resistance of an electric bulb drawing $1.2\ A$ current at $6.0\ V$ is:

- A $2\ W$.
 B $5\ W$.
 C $0.5\ W$.
 D $0.2\ W$.

(38) Joule/coulomb is same as:

- A watt.
- B volt.
- C ampere.
- D ohm.

C 4 V.

D 100 V.

(39) The potential difference required to pass a current 0.2 A in a wire of resistance $20\ \Omega$ is:

- A 40 V.
- B 1 V.

(40) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- A 60 J.
- B 15 J.
- C 120 J.
- D 30 J.

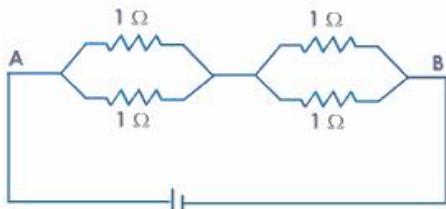


Figura 1

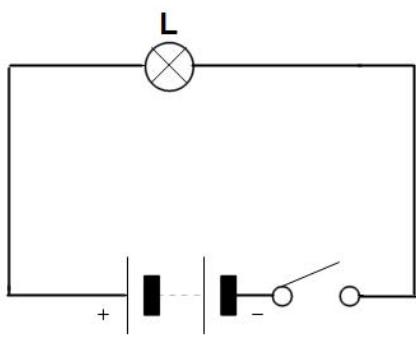


Figura 3

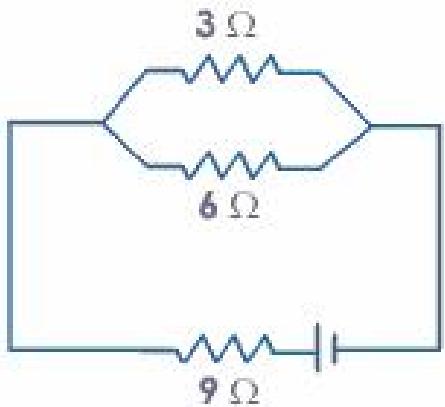


Figura 5

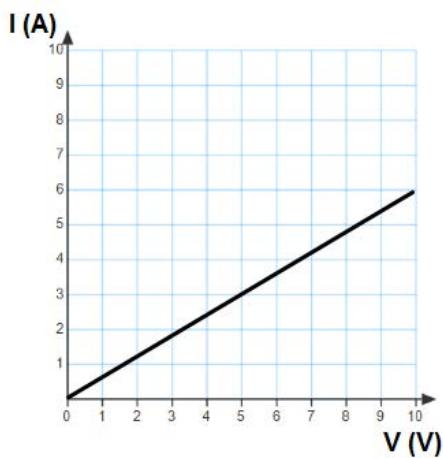


Figura 2

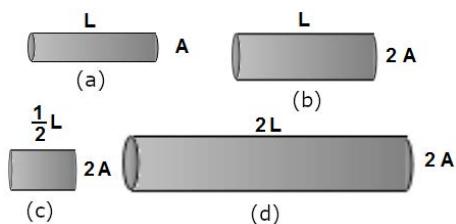


Figura 4

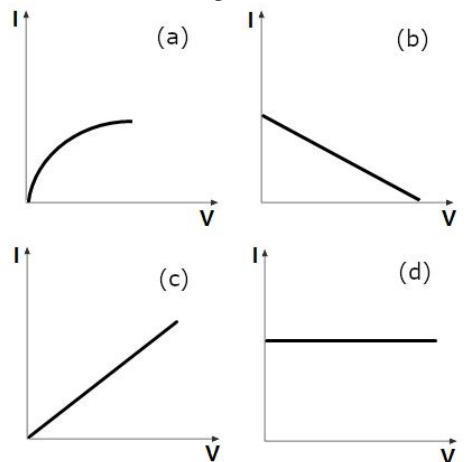


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 11

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) The unit of electric power is:
- A watt.
 B volt.
 C joule.
 D ampere.
- (2) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:
- A all in parallel.
 B $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
 C $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
 D all in series.
- (3) A battery is used to:
- A measure electric potential.
 B maintain a potential difference.
 C safeguard against short-circuit.
 D measure electric current.
- (4) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 200 C .
 B 600 C .
 C 400 C .
 D 500 C .
- (5) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A resistance.
 B current.
- (6) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{1}{1}$.
 B $\frac{R_B}{R_A} = \frac{2}{1}$.
 C $\frac{R_B}{R_A} = \frac{1}{2}$.
 D $\frac{R_B}{R_A} = \frac{1}{4}$.
- (7) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D^2 \cdot F$.
 B $D \cdot F$.
 C D^2/F .
 D $D \cdot F^2$.
- (8) The potential difference required to pass a current 0.2 A in a wire of resistance $20\ \Omega$ is:
- A 100 V .
 B 1 V .
 C 40 V .
 D 4 V .
- (9) Heat produced in a current carrying wire in 5 s is 60 J . The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A 60 J .
 B 15 J .
 C 120 J .

D 30 J.

- (10) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

A $25\ \Omega$.
 B $100\ \Omega$.
 C $50\ \Omega$.
 D $0\ \Omega$.

- (11) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{2}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{1}$.
 C $\frac{R_Y}{R_X} = \frac{1}{2}$.
 D $\frac{R_Y}{R_X} = \frac{1}{4}$.

- (12) The unit of current is:

A watt.
 B volt.
 C ampere.
 D coulomb.

- (13) When a current I flows through a resistance R for time t the electrical energy spent is given by:

A I^2R/t .
 B IRt .
 C IR^2t .
 D I^2Rt .

- (14) Determine which one of the following statements concerning resistors in series is *true*.

A The total current through the resistors is the sum of the current through each resistor.
 B The current through each resistor is the same.
 C The voltage across each resistor is the same.
 D The power dissipated by each resistor is the same.

- (15) The unit of resistivity is:

A ohm.
 B ohm·m.
 C ohm/m.
 D ohm/m².

- (16) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{A}{\rho L}$.

B $R = \frac{\rho L}{A}$.

C $R = \frac{\rho A}{L}$.

D $R = \frac{L}{\rho A}$.

- (17) Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A $2\ \Omega$.
 B $1\ \Omega$.
 C $3\ \Omega$.
 D $6\ \Omega$.

- (18) Joule/coulomb is same as:

A ampere.
 B volt.
 C watt.
 D ohm.

- (19) Complete the following statement: "The electromotive force is:

A the maximum electric potential energy stored within a battery".
 B the force that accelerates protons through a wire when a battery is connected to it".
 C the maximum potential difference between the terminals of a battery".
 D the force that accelerates electrons through a wire when a battery is connected to it".

- (20) A positive charge released from rest:

A does not move.
 B moves towards the regions of lower potential.
 C moves towards the regions of higher potential.
 D moves towards the regions of equal potential.

- (21) Determine which one of the following statements concerning resistors in parallel is *true*.

A The total voltage across the resistors is the sum of the voltage across each resistor.
 B The voltage across each resistor is the same.
 C The power dissipated by each resistor is the same.
 D The current through each resistor is the same.

- (22) In Figure 1 at the end of the text, the resistance across AB is:

A $0.5\ \Omega$.
 B $2\ \Omega$.
 C $4\ \Omega$.
 D $1\ \Omega$.

- (23) The current in a wire:

A depends on both resistance and potential difference.
 B does not depend on resistance and potential difference.

- C depends only on the potential difference applied.
 D depends only on the resistance of the wire.

(24) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- A 5 W.
 B 0.5 W.
 C 2 W.
 D 0.2 W.

(25) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Power.
 B Current.
 C Voltage.
 D Resistance.

(26) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- A 20 W.
 B 5 W.
 C 15 W.
 D 10 W.

(27) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A $D \cdot P$.
 B D^2/P .
 C $D \cdot P^2$.
 D $D^2 \cdot P$.

(28) When there is an electric current passing through a wire, the particles moving are:

- A ions.
 B protons.
 C electrons.
 D atoms.

(29) Determine which of the following statements does not represent Ohm's law.

- A potential difference = current \times resistance.
 B potential difference / current = constant.
 C current = resistance \times potential difference.
 D current / potential difference = constant.

(30) All of the wires in Figure 3 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- A (b).
 B (c).

- (a).
 (d).

(31) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:

- A $30\ \Omega$.
 B $270\ \Omega$.
 C $810\ \Omega$.
 D $10\ \Omega$.

(32) The resistivity of a wire depends on:

- A material.
 B length.
 C length, material and area of cross-section.
 D area of cross-section.

(33) In Figure 4 at the end of the text,

- A $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 B $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 C $3\ \Omega$, $6\ \Omega$ and $9\ \Omega$ are in parallel.
 D $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.

(34) Compute the number of electrons flowing through a battery that delivers a current of $3.0\ A$ for $12\ s$.

- A 6.4×10^{18} .
 B 2.2×10^{20} .
 C 36.
 D 4.8×10^{15} .

(35) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 5 at the end of the text.

- A To the right.
 B Upward.
 C Downward.
 D To the left.

(36) Determine which of the graphs in Figure 6 at the end of the text represents Ohm's law for a solid conductor.

- A (c).
 B (a).
 C (b).
 D (d).

(37) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the resistance of the wire.

- A $1.7\ \Omega$.
 B $0.4\ \Omega$.
 C $0.8\ \Omega$.
 D $1\ \Omega$.

(38) Ohm's law relates potential difference with:

- A time.
- B power.
- C energy.
- D current.

(39) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

- A $100\ \Omega$.
- B $25\ \Omega$.

C $0\ \Omega$.

D $50\ \Omega$.

(40) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.

A $6\ \Omega$.

B $1\ \Omega$.

C $2\ \Omega$.

D $3\ \Omega$.

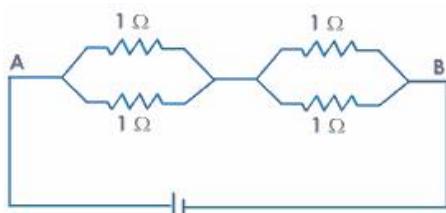


Figura 1

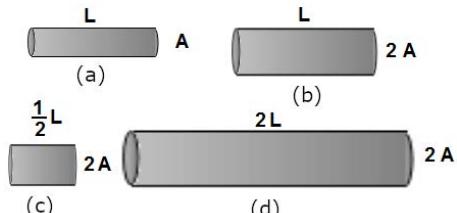


Figura 3

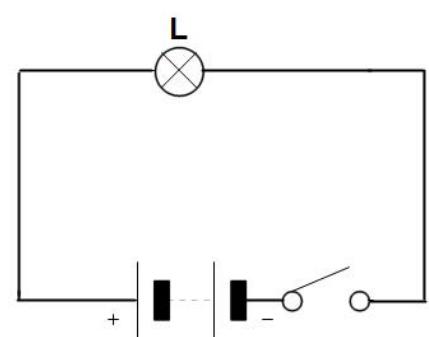


Figura 5

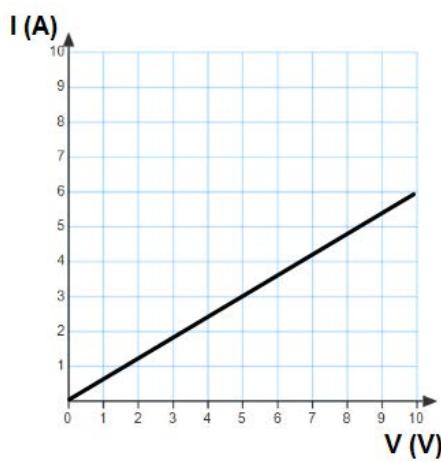


Figura 2

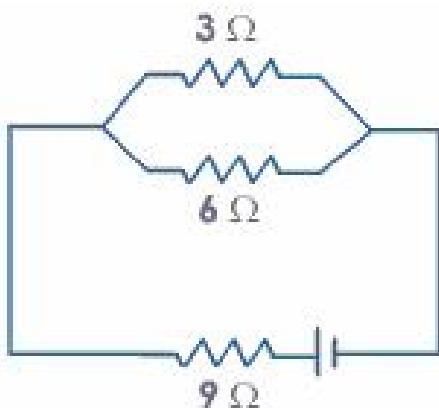


Figura 4

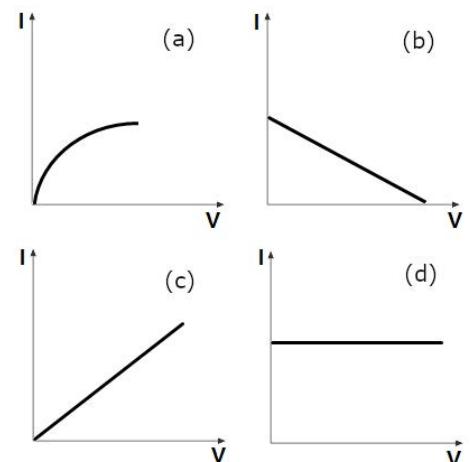


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 12

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- [A] $\frac{R_B}{R_A} = \frac{2}{1}$.
 [B] $\frac{R_B}{R_A} = \frac{1}{1}$.
 [C] $\frac{R_B}{R_A} = \frac{1}{4}$.
 [D] $\frac{R_B}{R_A} = \frac{1}{2}$.
- (2) The resistivity of a wire depends on:
- [A] material.
 [B] length.
 [C] area of cross-section.
 [D] length, material and area of cross-section.
- (3) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- [A] 20 W.
 [B] 10 W.
 [C] 5 W.
 [D] 15 W.
- (4) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- [A] 60 J.
 [B] 120 J.
 [C] 30 J.
 [D] 15 J.
- (5) A positive charge released from rest:
- [A] moves towards the regions of equal potential.
 [B] moves towards the regions of lower potential.
 [C] moves towards the regions of higher potential.
 [D] does not move.
- (6) The unit of resistivity is:
- [A] ohm/m².
 [B] ohm·m.
 [C] ohm/m.
 [D] ohm.
- (7) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.
- [A] 1 Ω.
 [B] 0.8 Ω.
 [C] 0.4 Ω.
 [D] 1.7 Ω.
- (8) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- [A] $I^2 R t$.
 [B] IRt .
 [C] $I^2 R/t$.
 [D] $IR^2 t$.
- (9) The unit of electric power is:
- [A] ampere.
 [B] joule.
 [C] watt.
 [D] volt.

- (10) All of the wires in Figure 2 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- [A] (c).
 [B] (a).
 [C] (b).
 [D] (d).
- (11) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 5 W.
 [B] 0.2 W.
 [C] 2 W.
 [D] 0.5 W.
- (12) The unit of current is:
- [A] coulomb.
 [B] volt.
 [C] ampere.
 [D] watt.
- (13) A battery is used to:
- [A] measure electric current.
 [B] safeguard against short-circuit.
 [C] measure electric potential.
 [D] maintain a potential difference.
- (14) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- [A] Current.
 [B] Voltage.
 [C] Power.
 [D] Resistance.
- (15) Determine which of the following statements does not represent Ohm's law.
- [A] current = resistance × potential difference.
 [B] potential difference / current = constant.
 [C] potential difference = current × resistance.
 [D] current / potential difference = constant.
- (16) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- [A] $R = \frac{\rho A}{L}$.
 [B] $R = \frac{\rho L}{A}$.
 [C] $R = \frac{L}{\rho A}$.
 [D] $R = \frac{A}{\rho L}$.
- (17) Joule/coulomb is same as:
- [A] volt.
 [B] ampere.
 [C] watt.
 [D] ohm.
- (18) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- [A] 500 C.
 [B] 400 C.
 [C] 200 C.
 [D] 600 C.
- (19) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 3 at the end of the text.
- [A] Downward.
 [B] To the right.
 [C] To the left.
 [D] Upward.
- (20) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 2 Ω .
 [B] 6 Ω .
 [C] 1 Ω .
 [D] 3 Ω .
- (21) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:
- [A] 10 Ω .
 [B] 270 Ω .
 [C] 810 Ω .
 [D] 30 Ω .
- (22) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- [A] $\frac{R_Y}{R_X} = \frac{1}{2}$.
 [B] $\frac{R_Y}{R_X} = \frac{2}{1}$.
 [C] $\frac{R_Y}{R_X} = \frac{1}{4}$.
 [D] $\frac{R_Y}{R_X} = \frac{1}{1}$.
- (23) Two resistances of 100 Ω and zero ohm are connected in parallel. The overall resistance will be:
- [A] 25 Ω .
 [B] 100 Ω .

- C 0 Ω .
 D 50 Ω .

(24) When there is an electric current passing through a wire, the particles moving are:

- A atoms.
 B ions.
 C protons.
 D electrons.

(25) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

- A 2.2×10^{20} .
 B 4.8×10^{15} .
 C 36.
 D 6.4×10^{18} .

(26) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A 2 Ω .
 B 1 Ω .
 C 6 Ω .
 D 3 Ω .

(27) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D \cdot F$.
 B D^2/F .
 C $D^2 \cdot F$.
 D $D \cdot F^2$.

(28) In Figure 4 at the end of the text, the resistance across AB is:

- A 0.5 Ω .
 B 2 Ω .
 C 4 Ω .
 D 1 Ω .

(29) Two resistances of 100 Ω and zero ohm are connected in series. The overall resistance will be:

- A 50 Ω .
 B 100 Ω .
 C 0 Ω .
 D 25 Ω .

(30) The current in a wire:

- A depends only on the resistance of the wire.
 B depends only on the potential difference applied.
 C depends on both resistance and potential difference.
 D does not depend on resistance and potential difference.

(31) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A power.
 B potential difference.
 C current.
 D resistance.

(32) Determine which of the graphs in Figure 5 at the end of the text represents Ohm's law for a solid conductor.

- A (a).
 B (b).
 C (d).
 D (c).

(33) Three resistors 2 Ω , 3 Ω and 4 Ω are connected so that the equivalent resistance is 9 Ω . The resistors are connected:

- A 2 Ω and 3 Ω in parallel and the combination in series with 4 Ω .
 B 2 Ω and 3 Ω in series and the combination in parallel to 4 Ω .
 C all in series.
 D all in parallel.

(34) Determine which one of the following statements concerning resistors in parallel is *true*.

- A The power dissipated by each resistor is the same.
 B The voltage across each resistor is the same.
 C The current through each resistor is the same.
 D The total voltage across the resistors is the sum of the voltage across each resistor.

(35) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A D^2/P .
 B $D^2 \cdot P$.
 C $D \cdot P^2$.
 D $D \cdot P$.

(36) In Figure 6 at the end of the text,

- A 3 Ω , 6 Ω and Ω are in parallel.
 B 6 Ω , 3 Ω and 9 Ω are in series.
 C 3 Ω , 6 Ω are in parallel and 9 Ω is in series.
 D 9 Ω and 6 Ω are in parallel and the combination is in series with 3 Ω .

(37) Complete the following statement: "The electromotive force is:

- A the force that accelerates electrons through a wire when a battery is connected to it".
 B the maximum electric potential energy stored within a battery".
 C the maximum potential difference between the terminals of a battery".

- D the force that accelerates protons through a wire when a battery is connected to it".

- (38) The potential difference required to pass a current 0.2 A in a wire of resistance $20\ \Omega$ is:

- A 4 V.
- B 1 V.
- C 100 V.
- D 40 V.

- (39) Ohm's law relates potential difference with:

- A energy.

B power.

C current.

D time.

- (40) Determine which one of the following statements concerning resistors in series is *true*.

- A The total current through the resistors is the sum of the current through each resistor.
- B The power dissipated by each resistor is the same.
- C The current through each resistor is the same.
- D The voltage across each resistor is the same.

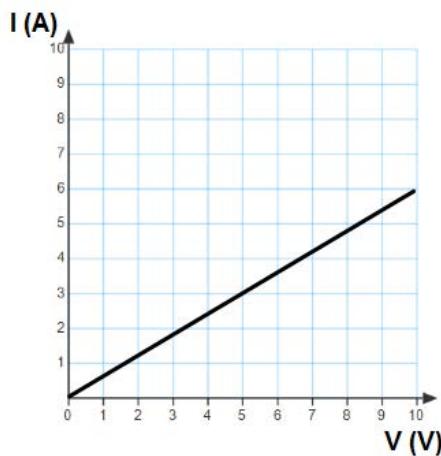


Figura 1

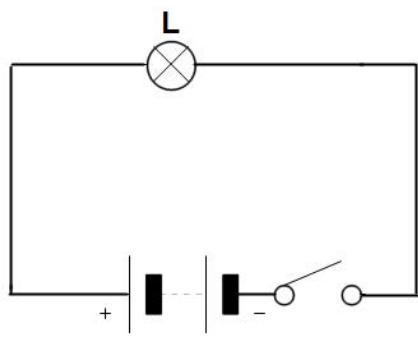


Figura 3

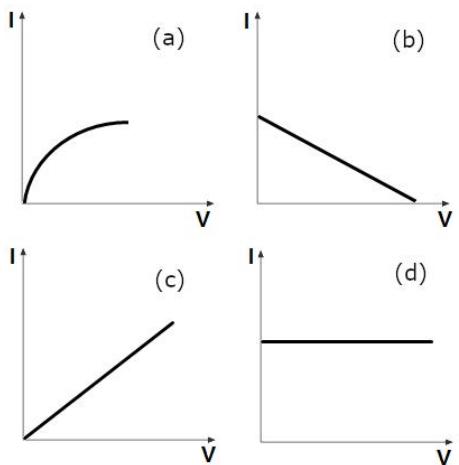


Figura 5

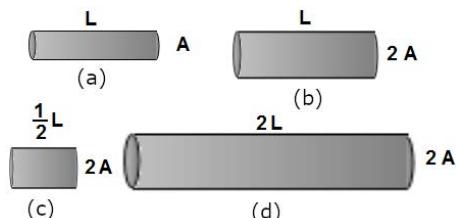


Figura 2

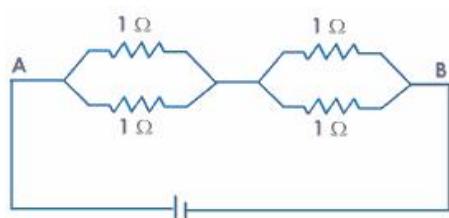


Figura 4

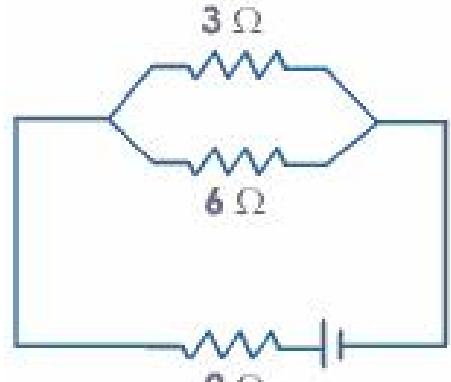


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 13

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- 1) When there is an electric current passing through a wire, the particles moving are:
- A ions.
 B electrons.
 C atoms.
 D protons.
- 2) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:
- A all in series.
 B all in parallel.
 C $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
 D $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
- 3) Determine which one of the following statements concerning resistors in parallel is *true*.
- A The current through each resistor is the same.
 B The total voltage across the resistors is the sum of the voltage across each resistor.
 C The power dissipated by each resistor is the same.
 D The voltage across each resistor is the same.
- 4) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A 30 J.
 B 60 J.
 C 120 J.
 D 15 J.
- 5) In Figure 1 at the end of the text, the resistance across AB is:
- A $1\ \Omega$.
- 6) A battery is used to:
- A safeguard against short-circuit.
 B measure electric potential.
 C maintain a potential difference.
 D measure electric current.
- 7) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{1}{1}$.
 B $\frac{R_B}{R_A} = \frac{2}{1}$.
 C $\frac{R_B}{R_A} = \frac{1}{4}$.
 D $\frac{R_B}{R_A} = \frac{1}{2}$.
- 8) The unit of current is:
- A volt.
 B ampere.
 C watt.
 D coulomb.
- 9) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.
- A To the right.
 B To the left.
 C Downward.
 D Upward.

- (10) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- A D^2/P .
 B $D \cdot P$.
 C $D^2 \cdot P$.
 D $D \cdot P^2$.
- (11) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D \cdot F$.
 B $D \cdot F^2$.
 C D^2/F .
 D $D^2 \cdot F$.
- (12) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A resistance.
 B current.
 C potential difference.
 D power.
- (13) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- A 1Ω .
 B 2Ω .
 C 3Ω .
 D 6Ω .
- (14) A positive charge released from rest:
- A moves towards the regions of equal potential.
 B moves towards the regions of lower potential.
 C does not move.
 D moves towards the regions of higher potential.
- (15) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:
- A 10Ω .
 B 810Ω .
 C 270Ω .
 D 30Ω .
- (16) Complete the following statement: "The electromotive force is:
 A the maximum potential difference between the terminals of a battery".
 B the maximum electric potential energy stored within a battery".
 C the force that accelerates protons through a wire when a battery is connected to it".
- (17) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- A $R = \frac{L}{\rho A}$.
 B $R = \frac{\rho A}{L}$.
 C $R = \frac{\rho L}{A}$.
 D $R = \frac{A}{\rho L}$.
- (18) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .
- A 4.8×10^{15} .
 B 36.
 C 2.2×10^{20} .
 D 6.4×10^{18} .
- (19) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the resistance of the wire.
- A 1.7Ω .
 B 0.8Ω .
 C 1Ω .
 D 0.4Ω .
- (20) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the power dissipated in the resistor when the applied voltage is 5 V .
- A 20 W .
 B 5 W .
 C 10 W .
 D 15 W .
- (21) Determine which of the graphs in Figure 4 at the end of the text represents Ohm's law for a solid conductor.
- A (a).
 B (c).
 C (b).
 D (d).
- (22) All of the wires in Figure 5 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (d).
 B (a).
 C (b).
 D (c).
- (23) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 200 C.
 B 600 C.
 C 500 C.
 D 400 C.

(24) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

- A $50\ \Omega$.
 B $25\ \Omega$.
 C $0\ \Omega$.
 D $100\ \Omega$.

(25) The unit of resistivity is:

- A ohm/m².
 B ohm·m.
 C ohm/m.
 D ohm.

(26) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.

- A $3\ \Omega$.
 B $6\ \Omega$.
 C $1\ \Omega$.
 D $2\ \Omega$.

(27) Determine which of the following statements does not represent Ohm's law.

- A potential difference = current \times resistance.
 B current / potential difference = constant.
 C potential difference / current = constant.
 D current = resistance \times potential difference.

(28) The resistivity of a wire depends on:

- A length.
 B length, material and area of cross-section.
 C material.
 D area of cross-section.

(29) The potential difference required to pass a current $0.2\ A$ in a wire of resistance $20\ \Omega$ is:

- A 1 V.
 B 4 V.
 C 40 V.
 D 100 V.

(30) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A IR^2t .
 B IRt .

- C I^2Rt .
 D I^2R/t .

(31) The resistance of an electric bulb drawing $1.2\ A$ current at $6.0\ V$ is:

- A 0.5 W.
 B 2 W.
 C 0.2 W.
 D 5 W.

(32) The current in a wire:

- A depends on both resistance and potential difference.
 B depends only on the resistance of the wire.
 C does not depend on resistance and potential difference.
 D depends only on the potential difference applied.

(33) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- A $\frac{R_Y}{R_X} = \frac{1}{2}$.
 B $\frac{R_Y}{R_X} = \frac{2}{1}$.
 C $\frac{R_Y}{R_X} = \frac{1}{1}$.
 D $\frac{R_Y}{R_X} = \frac{1}{4}$.

(34) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Voltage.
 B Resistance.
 C Power.
 D Current.

(35) Determine which one of the following statements concerning resistors in series is *true*.

- A The total current through the resistors is the sum of the current through each resistor.
 B The current through each resistor is the same.
 C The voltage across each resistor is the same.
 D The power dissipated by each resistor is the same.

(36) In Figure 6 at the end of the text,

- A $3\ \Omega$, $6\ \Omega$ and Ω are in parallel.
 B $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 C $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
 D $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.

(37) Joule/coulomb is same as:

- A watt.
 B ohm.
 C volt.

D ampere.

(38) The unit of electric power is:

A volt.

B joule.

C ampere.

D watt.

(39) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

A $0\ \Omega$.

B $25\ \Omega$.

C $100\ \Omega$.

D $50\ \Omega$.

(40) Ohm's law relates potential difference with:

A power.

B time.

C current.

D energy.

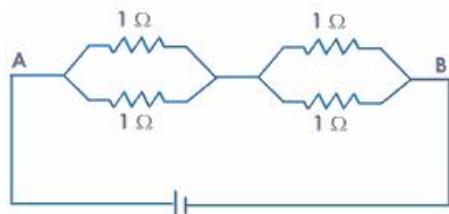


Figura 1

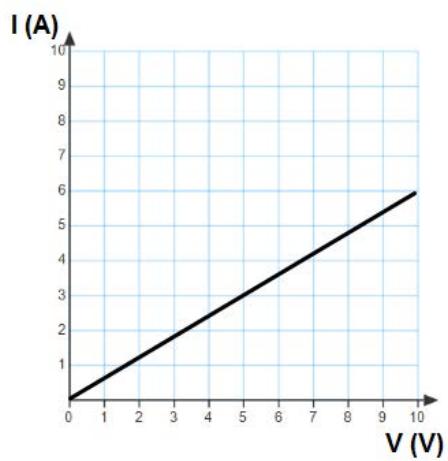


Figura 3

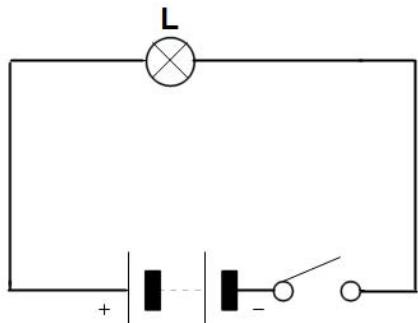


Figura 2

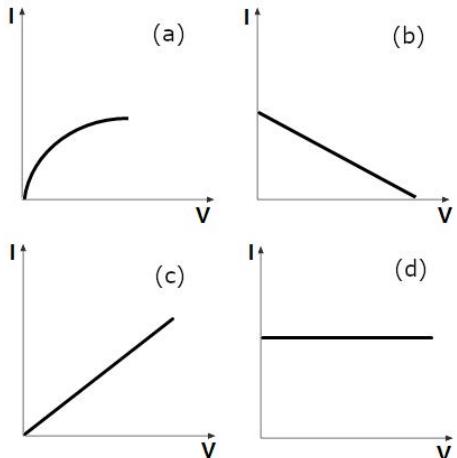


Figura 4

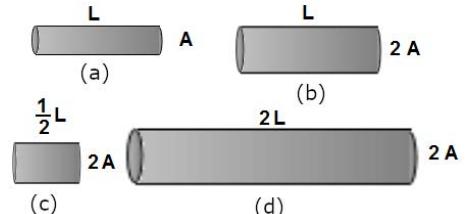


Figura 5

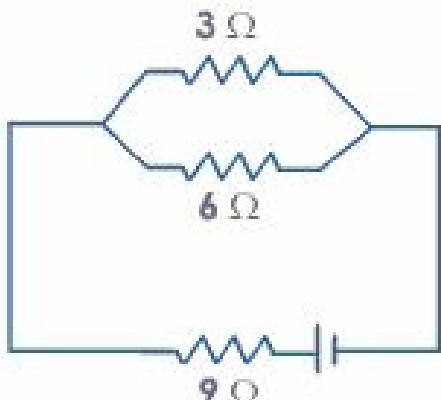


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 14

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- [A] $\frac{R_B}{R_A} = \frac{2}{1}$.
 [B] $\frac{R_B}{R_A} = \frac{1}{2}$.
 [C] $\frac{R_B}{R_A} = \frac{1}{4}$.
 [D] $\frac{R_B}{R_A} = \frac{1}{1}$.
- (2) All of the wires in Figure 1 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- [A] (d).
 [B] (b).
 [C] (c).
 [D] (a).
- (3) Determine which one of the following statements concerning resistors in parallel is *true*.
- [A] The current through each resistor is the same.
 [B] The voltage across each resistor is the same.
 [C] The power dissipated by each resistor is the same.
 [D] The total voltage across the resistors is the sum of the voltage across each resistor.
- (4) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- [A] Power.
 [B] Voltage.
 [C] Resistance.
 [D] Current.
- (5) Determine which one of the following statements concerning resistors in series is *true*.
- [A] The current through each resistor is the same.
 [B] The power dissipated by each resistor is the same.
 [C] The total current through the resistors is the sum of the current through each resistor.
 [D] The voltage across each resistor is the same.
- (6) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- [A] potential difference.
 [B] resistance.
 [C] current.
 [D] power.
- (7) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- [A] D^2/F .
 [B] $D \cdot F$.
 [C] $D^2 \cdot F$.
 [D] $D \cdot F^2$.
- (8) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- [A] $R = \frac{A}{\rho L}$.
 [B] $R = \frac{L}{\rho A}$.
 [C] $R = \frac{\rho L}{A}$.
 [D] $R = \frac{\rho A}{L}$.
- (9) Joule/coulomb is same as:
- [A] volt.

- B watt.
- C ampere.
- D ohm.

(10) Determine which of the following statements does not represent Ohm's law:

- A current / potential difference = constant.
- B potential difference = current \times resistance.
- C current = resistance \times potential difference.
- D potential difference / current = constant.

(11) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

- A $0\ \Omega$.
- B $25\ \Omega$.
- C $50\ \Omega$.
- D $100\ \Omega$.

(12) A positive charge released from rest:

- A moves towards the regions of lower potential.
- B moves towards the regions of higher potential.
- C does not move.
- D moves towards the regions of equal potential.

(13) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:

- A $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
- B all in series.
- C $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
- D all in parallel.

(14) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.

- A To the right.
- B Downward.
- C Upward.
- D To the left.

(15) Complete the following statement: "The electromotive force is:

- A the force that accelerates electrons through a wire when a battery is connected to it".
- B the maximum potential difference between the terminals of a battery".
- C the maximum electric potential energy stored within a battery".
- D the force that accelerates protons through a wire when a battery is connected to it".

(16) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.

- A $1\ \Omega$.
- B $6\ \Omega$.
- C $3\ \Omega$.
- D $2\ \Omega$.

(17) Ohm's law relates potential difference with:

- A time.
- B current.
- C power.
- D energy.

(18) The resistance of an electric bulb drawing $1.2\ A$ current at $6.0\ V$ is:

- A $5\ W$.
- B $0.2\ W$.
- C $0.5\ W$.
- D $2\ W$.

(19) A battery is used to:

- A measure electric potential.
- B safeguard against short-circuit.
- C maintain a potential difference.
- D measure electric current.

(20) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the resistance of the wire.

- A $0.8\ \Omega$.
- B $1.7\ \Omega$.
- C $0.4\ \Omega$.
- D $1\ \Omega$.

(21) The current in a wire:

- A depends on both resistance and potential difference.
- B depends only on the potential difference applied.
- C does not depend on resistance and potential difference.
- D depends only on the resistance of the wire.

(22) The unit of resistivity is:

- A ohm-m.
- B ohm.
- C ohm/m².
- D ohm/m.

(23) In Figure 4 at the end of the text,

- A $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
- B $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
- C $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.

- (D) $3\ \Omega$, $6\ \Omega$ and Ω are in parallel.
- (24) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- (A) 20 W.
 (B) 15 W.
 (C) 10 W.
 (D) 5 W.
- (25) In Figure 5 at the end of the text, the resistance across AB is:
- (A) $4\ \Omega$.
 (B) $0.5\ \Omega$.
 (C) $1\ \Omega$.
 (D) $2\ \Omega$.
- (26) The potential difference required to pass a current 0.2 A in a wire of resistance $20\ \Omega$ is:
- (A) 100 V.
 (B) 4 V.
 (C) 1 V.
 (D) 40 V.
- (27) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- (A) I^2Rt .
 (B) IR^2t .
 (C) IRt .
 (D) I^2R/t .
- (28) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- (A) $D \cdot P$.
 (B) $D^2 \cdot P$.
 (C) D^2/P .
 (D) $D \cdot P^2$.
- (29) Determine which of the graphs in Figure 6 at the end of the text represents Ohm's law for a solid conductor.
- (A) (d).
 (B) (c).
 (C) (a).
 (D) (b).
- (30) The resistivity of a wire depends on:
- (A) area of cross-section.
 (B) material.
 (C) length, material and area of cross-section.
 (D) length.
- (31) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- (A) 30 J.
 (B) 15 J.
 (C) 120 J.
 (D) 60 J.
- (32) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- (A) $270\ \Omega$.
 (B) $810\ \Omega$.
 (C) $30\ \Omega$.
 (D) $10\ \Omega$.
- (33) The unit of current is:
- (A) ampere.
 (B) coulomb.
 (C) volt.
 (D) watt.
- (34) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- (A) $\frac{R_Y}{R_X} = \frac{1}{4}$.
 (B) $\frac{R_Y}{R_X} = \frac{2}{1}$.
 (C) $\frac{R_Y}{R_X} = \frac{1}{1}$.
 (D) $\frac{R_Y}{R_X} = \frac{1}{2}$.
- (35) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- (A) 600 C.
 (B) 200 C.
 (C) 500 C.
 (D) 400 C.
- (36) Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- (A) $1\ \Omega$.
 (B) $6\ \Omega$.
 (C) $3\ \Omega$.
 (D) $2\ \Omega$.
- (37) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- (A) $0\ \Omega$.
 (B) $50\ \Omega$.
 (C) $100\ \Omega$.

D 25Ω .

- (38) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

A 36.

B 2.2×10^{20} .

C 6.4×10^{18} .

D 4.8×10^{15} .

B volt.

C watt.

D joule.

- (39) The unit of electric power is:

A ampere.

- (40) When there is an electric current passing through a wire, the particles moving are:

A atoms.

B ions.

C electrons.

D protons.

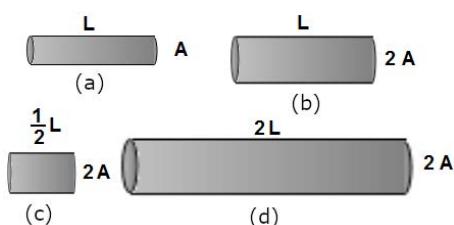


Figura 1

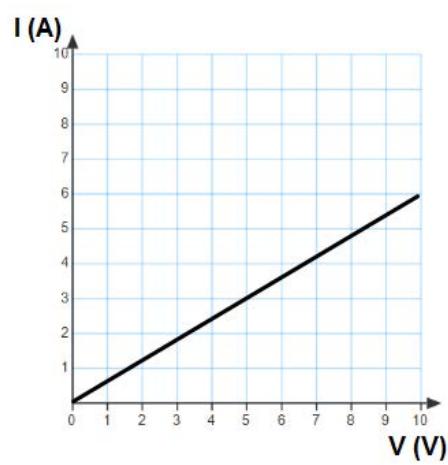


Figura 3

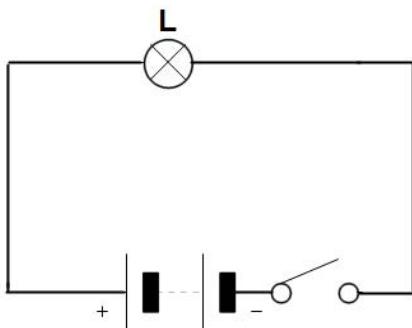


Figura 2

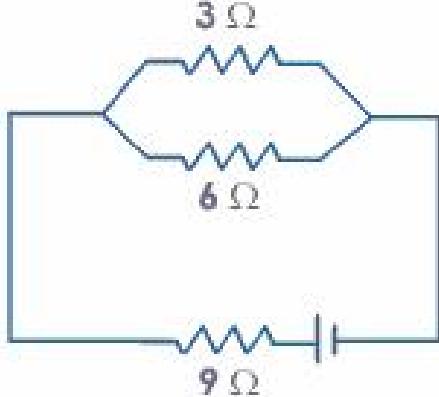


Figura 4

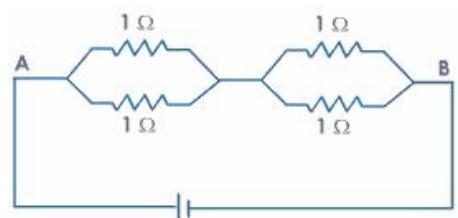


Figura 5

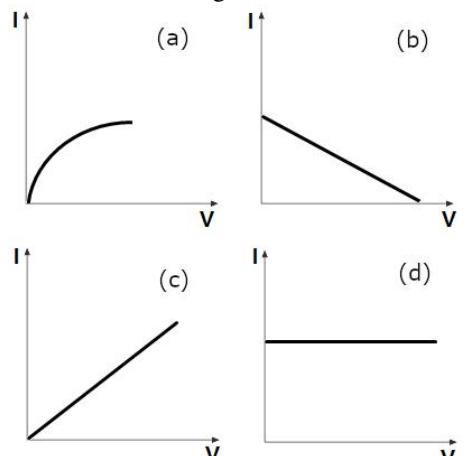


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 15

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) The resistivity of a wire depends on:
- [A] area of cross-section.
 [B] length, material and area of cross-section.
 [C] length.
 [D] material.
- (2) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 1Ω .
 [B] 2Ω .
 [C] 6Ω .
 [D] 3Ω .
- (3) A battery is used to:
- [A] measure electric current.
 [B] measure electric potential.
 [C] maintain a potential difference.
 [D] safeguard against short-circuit.
- (4) A positive charge released from rest:
- [A] moves towards the regions of equal potential.
 [B] moves towards the regions of lower potential.
 [C] moves towards the regions of higher potential.
 [D] does not move.
- (5) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] $D \cdot P$.
 [B] $D \cdot P^2$.
 [C] $D^2 \cdot P$.
- (6) When there is an electric current passing through a wire, the particles moving are:
- [A] electrons.
 [B] atoms.
 [C] protons.
 [D] ions.
- (7) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.
- [A] To the left.
 [B] Downward.
 [C] Upward.
 [D] To the right.
- (8) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .
- [A] 2.2×10^{20} .
 [B] 4.8×10^{15} .
 [C] 36.
 [D] 6.4×10^{18} .
- (9) Determine which one of the following statements concerning resistors in parallel is *true*.
- [A] The voltage across each resistor is the same.
 [B] The current through each resistor is the same.
 [C] The power dissipated by each resistor is the same.
 [D] The total voltage across the resistors is the sum of the voltage across each resistor.
- (10) In Figure 2 at the end of the text,
- [A] 3Ω , 6Ω are in parallel and 9Ω is in series.
 [B] 6Ω , 3Ω and 9Ω are in series.

- (C) 9 Ω and 6 Ω are in parallel and the combination is in series with 3 Ω .
 (D) 3 Ω , 6 Ω and Ω are in parallel.
- (11) Two resistances of 100 Ω and zero ohm are connected in parallel. The overall resistance will be:
 (A) 0 Ω .
 (B) 100 Ω .
 (C) 25 Ω .
 (D) 50 Ω .
- (12) Ohm's law relates potential difference with:
 (A) time.
 (B) energy.
 (C) power.
 (D) current.
- (13) The unit of electric power is:
 (A) ampere.
 (B) volt.
 (C) watt.
 (D) joule.
- (14) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
 (A) Current.
 (B) Power.
 (C) Resistance.
 (D) Voltage.
- (15) Determine which one of the following statements concerning resistors in series is true.
 (A) The total current through the resistors is the sum of the current through each resistor.
 (B) The power dissipated by each resistor is the same.
 (C) The voltage across each resistor is the same.
 (D) The current through each resistor is the same.
- (16) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the resistance of the wire.
 (A) 1 Ω .
 (B) 0.4 Ω .
 (C) 0.8 Ω .
 (D) 1.7 Ω .
- (17) The current in a wire:
 (A) depends only on the potential difference applied.
 (B) depends only on the resistance of the wire.
 (C) depends on both resistance and potential difference.
 (D) does not depend on resistance and potential difference.
- (18) When a current I flows through a resistance R for time t the electrical energy spent is given by:
 (A) I^2Rt .
 (B) IR^2t .
 (C) I^2R/t .
 (D) IRt .
- (19) Two resistances of 100 Ω and zero ohm are connected in series. The overall resistance will be:
 (A) 50 Ω .
 (B) 100 Ω .
 (C) 0 Ω .
 (D) 25 Ω .
- (20) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
 (A) 1 Ω .
 (B) 3 Ω .
 (C) 2 Ω .
 (D) 6 Ω .
- (21) Joule/coulomb is same as:
 (A) ampere.
 (B) ohm.
 (C) volt.
 (D) watt.
- (22) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
 (A) $D \cdot F$.
 (B) D^2/F .
 (C) $D \cdot F^2$.
 (D) $D^2 \cdot F$.
- (23) Three resistors 2 Ω , 3 Ω and 4 Ω are connected so that the equivalent resistance is 9 Ω . The resistors are connected:
 (A) 2 Ω and 3 Ω in parallel and the combination in series with 4 Ω .
 (B) all in parallel.
 (C) all in series.
 (D) 2 Ω and 3 Ω in series and the combination in parallel to 4 Ω .
- (24) Determine which of the graphs in Figure 4 at the end of the text represents Ohm's law for a solid conductor.
 (A) (b).
 (B) (a).
 (C) (c).
 (D) (d).

- (25) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- [A] $R = \frac{\rho A}{L}$.
- [B] $R = \frac{\rho L}{A}$.
- [C] $R = \frac{L}{\rho A}$.
- [D] $R = \frac{A}{\rho L}$.

- (26) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A . Determine how the resistance of wire B compares to the resistance of wire A .

- [A] $\frac{R_B}{R_A} = \frac{2}{1}$.
- [B] $\frac{R_B}{R_A} = \frac{1}{1}$.
- [C] $\frac{R_B}{R_A} = \frac{1}{4}$.
- [D] $\frac{R_B}{R_A} = \frac{1}{2}$.

- (27) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- [A] 400 C.
- [B] 500 C.
- [C] 600 C.
- [D] 200 C.

- (28) All of the wires in Figure 5 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- [A] (b).
- [B] (a).
- [C] (d).
- [D] (c).

- (29) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- [A] 30 J.
- [B] 15 J.
- [C] 120 J.
- [D] 60 J.

- (30) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- [A] $\frac{R_Y}{R_X} = \frac{2}{1}$.
- [B] $\frac{R_Y}{R_X} = \frac{1}{2}$.

[C] $\frac{R_Y}{R_X} = \frac{1}{1}$.

[D] $\frac{R_Y}{R_X} = \frac{1}{4}$.

- (31) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- [A] power.
- [B] potential difference.
- [C] resistance.
- [D] current.

- (32) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- [A] 0.2 W.
- [B] 0.5 W.
- [C] 5 W.
- [D] 2 W.

- (33) In Figure 6 at the end of the text, the resistance across AB is:

- [A] 4 Ω .
- [B] 2 Ω .
- [C] 1 Ω .
- [D] 0.5 Ω .

- (34) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:

- [A] 100 V.
- [B] 40 V.
- [C] 4 V.
- [D] 1 V.

- (35) The unit of current is:

- [A] coulomb.
- [B] ampere.
- [C] watt.
- [D] volt.

- (36) Complete the following statement: “The electromotive force is:

- [A] the maximum potential difference between the terminals of a battery”.
- [B] the force that accelerates protons through a wire when a battery is connected to it”.
- [C] the force that accelerates electrons through a wire when a battery is connected to it”.
- [D] the maximum electric potential energy stored within a battery”.

- (37) The electric current as a function of voltage of a wire is presented by the graph in Figure 3. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- [A] 20 W.
- [B] 15 W.
- [C] 5 W.

D 10 W.

(38) The unit of resistivity is:

- A ohm.
 B ohm/m².
 C ohm/m.
 D ohm·m.

(39) Three equal resistances when combined in series are equivalent to 90 Ω. Their equivalent resistance when combined in parallel will be:

- A 10 Ω.

B 270 Ω.

C 30 Ω.

D 810 Ω.

(40) Determine which of the following statements does not represent Ohm's law.

- A current = resistance × potential difference.
 B potential difference = current × resistance.
 C potential difference / current = constant.
 D current / potential difference = constant.

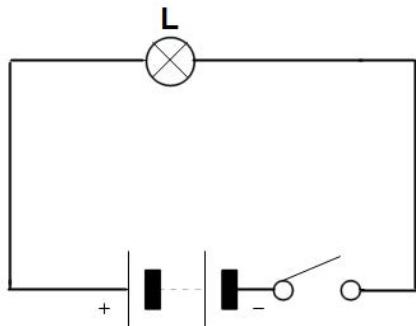


Figura 1

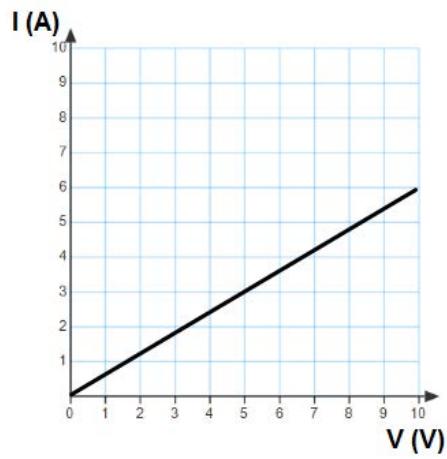


Figura 3

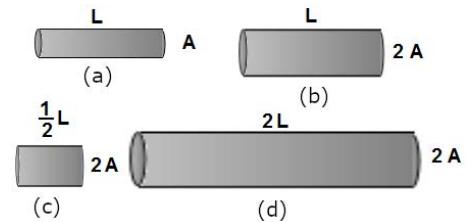


Figura 5

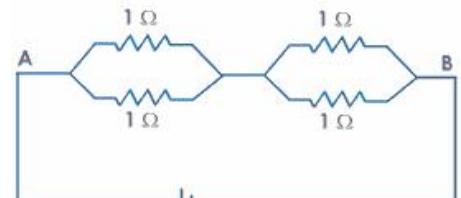


Figura 6

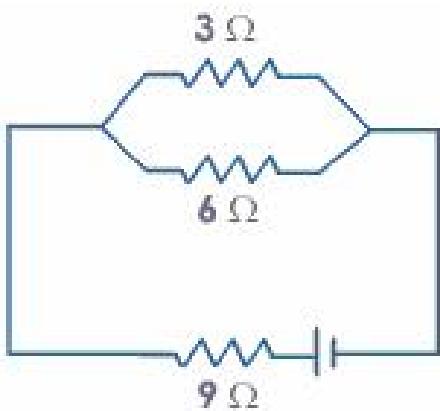


Figura 2

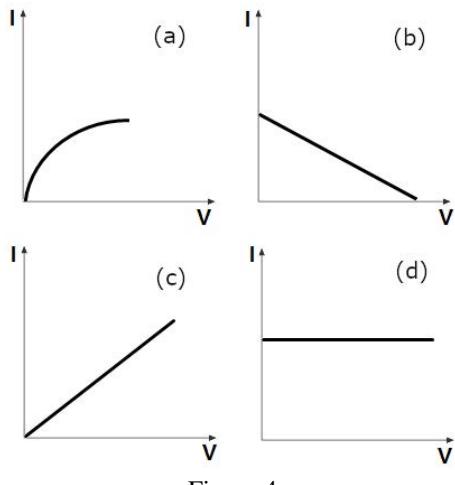


Figura 4

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 16

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① Determine which of the following statements does not represent Ohm's law.
- [A] potential difference = current × resistance.
 [B] potential difference / current = constant.
 [C] current / potential difference = constant.
 [D] current = resistance × potential difference.
- ② Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- [A] 3Ω .
 [B] 2Ω .
 [C] 1Ω .
 [D] 6Ω .
- ③ Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:
- [A] 25Ω .
 [B] 50Ω .
 [C] 0Ω .
 [D] 100Ω .
- ④ Joule/coulomb is same as:
- [A] ohm.
 [B] volt.
 [C] watt.
 [D] ampere.
- ⑤ The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:
- [A] 1 V.
 [B] 100 V.
 [C] 40 V.
- ⑥ [D] 4 V.
- ⑦ The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.
- [A] 1Ω .
 [B] 0.4Ω .
 [C] 0.8Ω .
 [D] 1.7Ω .
- ⑧ A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- [A] 500 C.
 [B] 400 C.
 [C] 600 C.
 [D] 200 C.
- ⑨ Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.
- [A] To the left.
 [B] To the right.
 [C] Upward.
 [D] Downward.
- ⑩ Ohm's law relates potential difference with:
- [A] time.
 [B] energy.
 [C] current.
 [D] power.
- ⑪ In Figure 3 at the end of the text,
- [A] 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .

A 6Ω , 3Ω and 9Ω are in series.

C 3Ω , 6Ω are in parallel and 9Ω is in series.

D 3Ω , 6Ω and Ω are in parallel.

(11) The unit of current is:

A ampere.

B coulomb.

C watt.

D volt.

(12) Determine which of the graphs in Figure 4 at the end of the text represents Ohm's law for a solid conductor.

A (d).

B (b).

C (a).

D (c).

(13) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

A $D^2 \cdot F$.

B $D \cdot F$.

C D^2/F .

D $D \cdot F^2$.

(14) Complete the following statement: "The electromotive force is:

A the force that accelerates electrons through a wire when a battery is connected to it".

B the maximum potential difference between the terminals of a battery".

C the maximum electric potential energy stored within a battery".

D the force that accelerates protons through a wire when a battery is connected to it".

(15) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

A 2.2×10^{20} .

B 6.4×10^{18} .

C 4.8×10^{15} .

D 36.

(16) Determine which one of the following statements concerning resistors in parallel is *true*.

A The total voltage across the resistors is the sum of the voltage across each resistor.

B The current through each resistor is the same.

C The power dissipated by each resistor is the same.

D The voltage across each resistor is the same.

(17) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

A $D^2 \cdot P$.

B $D \cdot P$.

C $D \cdot P^2$.

D D^2/P .

(18) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A . Determine how the resistance of wire B compares to the resistance of wire A .

A $\frac{R_B}{R_A} = \frac{2}{1}$.

B $\frac{R_B}{R_A} = \frac{1}{2}$.

C $\frac{R_B}{R_A} = \frac{1}{1}$.

D $\frac{R_B}{R_A} = \frac{1}{4}$.

(19) All of the wires in Figure 5 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (b).

B (a).

C (c).

D (d).

(20) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

A 2Ω and 3Ω in parallel and the combination in series with 4Ω .

B all in series.

C all in parallel.

D 2Ω and 3Ω in series and the combination in parallel to 4Ω .

(21) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{1}{4}$.

B $\frac{R_Y}{R_X} = \frac{1}{1}$.

C $\frac{R_Y}{R_X} = \frac{2}{1}$.

D $\frac{R_Y}{R_X} = \frac{1}{2}$.

(22) The resistivity of a wire depends on:

A area of cross-section.

B material.

C length.

D length, material and area of cross-section.

(23) The unit of electric power is:

A volt.

- B watt.
- C ampere.
- D joule.

(24) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A power.
- B potential difference.
- C resistance.
- D current.

(25) The current in a wire:

- A depends only on the potential difference applied.
- B depends on both resistance and potential difference.
- C depends only on the resistance of the wire.
- D does not depend on resistance and potential difference.

(26) A battery is used to:

- A measure electric current.
- B measure electric potential.
- C safeguard against short-circuit.
- D maintain a potential difference.

(27) The unit of resistivity is:

- A ohm.
- B ohm/m².
- C ohm/m.
- D ohm·m.

(28) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Resistance.
- B Power.
- C Voltage.
- D Current.

(29) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- A 15 J.
- B 30 J.
- C 60 J.
- D 120 J.

(30) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

- A 2 Ω .
- B 3 Ω .
- C 1 Ω .

- D 6 Ω .

(31) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- A $R = \frac{L}{\rho A}$.
- B $R = \frac{A}{\rho L}$.
- C $R = \frac{\rho L}{A}$.
- D $R = \frac{\rho A}{L}$.

(32) When there is an electric current passing through a wire, the particles moving are:

- A electrons.
- B atoms.
- C ions.
- D protons.

(33) In Figure 6 at the end of the text, the resistance across AB is:

- A 1 Ω .
- B 0.5 Ω .
- C 4 Ω .
- D 2 Ω .

(34) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- A 15 W.
- B 10 W.
- C 20 W.
- D 5 W.

(35) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- A 0.2 W.
- B 0.5 W.
- C 2 W.
- D 5 W.

(36) A positive charge released from rest:

- A does not move.
- B moves towards the regions of higher potential.
- C moves towards the regions of equal potential.
- D moves towards the regions of lower potential.

(37) Determine which one of the following statements concerning resistors in series is true.

- A The current through each resistor is the same.
- B The power dissipated by each resistor is the same.
- C The total current through the resistors is the sum of the current through each resistor.
- D The voltage across each resistor is the same.

- (38) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- [A] IRt .
 [B] I^2Rt .
 [C] IR^2t .
 [D] I^2R/t .
- (39) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- [A] $30\ \Omega$.
- (40) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- [A] $0\ \Omega$.
 [B] $100\ \Omega$.
 [C] $25\ \Omega$.
 [D] $50\ \Omega$.

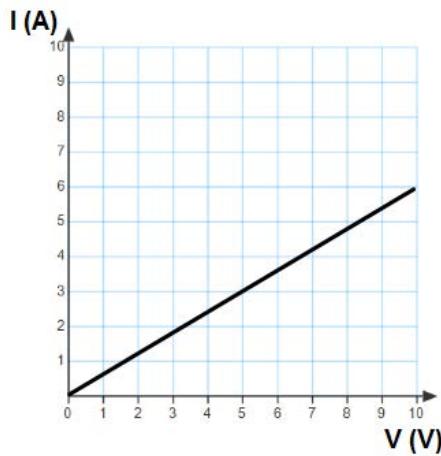


Figura 1

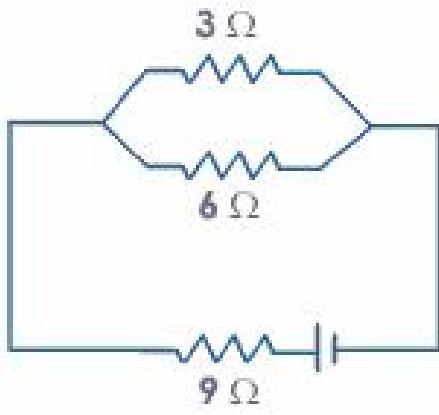


Figura 3

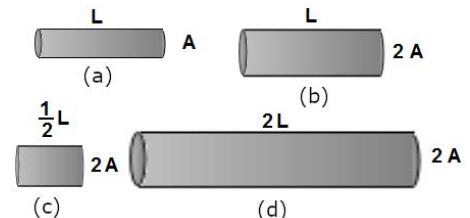


Figura 5

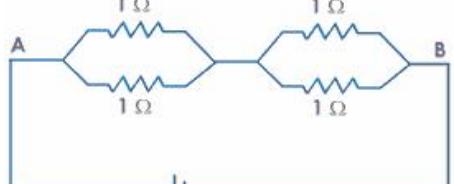


Figura 6

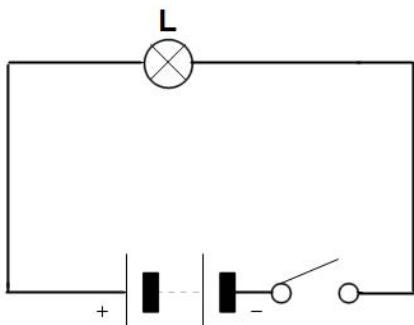


Figura 2

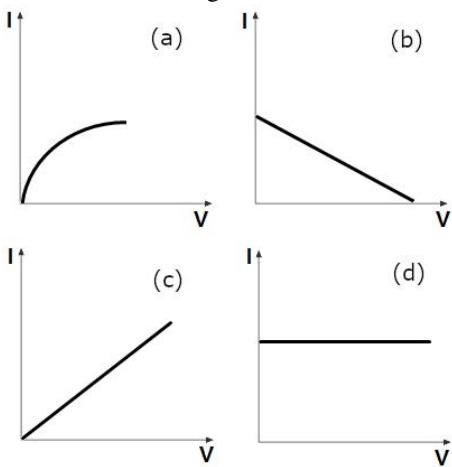


Figura 4

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 17

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A 60 J.
 B 120 J.
 C 15 J.
 D 30 J.
- ② Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- A 1Ω .
 B 2Ω .
 C 3Ω .
 D 6Ω .
- ③ A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 400 C.
 B 500 C.
 C 200 C.
 D 600 C.
- ④ Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.
- A Downward.
 B To the left.
 C To the right.
 D Upward.
- ⑤ When a current I flows through a resistance R for time t the electrical energy spent is given by:
- A IR^2t .
- ⑥ Ohm's law relates potential difference with:
- A power.
 B current.
 C time.
 D energy.
- ⑦ A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- A $R = \frac{\rho A}{L}$.
 B $R = \frac{L}{\rho A}$.
 C $R = \frac{A}{\rho L}$.
 D $R = \frac{\rho L}{A}$.
- ⑧ The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A resistance.
 B current.
 C potential difference.
 D power.
- ⑨ The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 5 W.
 B 0.2 W.
 C 0.5 W.
 D 2 W.

- (10) A positive charge released from rest:
- A moves towards the regions of equal potential.
 - B moves towards the regions of higher potential.
 - C does not move.
 - D moves towards the regions of lower potential.
- (11) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- A 6.4×10^{18} .
 - B 4.8×10^{15} .
 - C 2.2×10^{20} .
 - D 36.
- (12) Determine which one of the following statements concerning resistors in parallel is *true*.
- A The voltage across each resistor is the same.
 - B The power dissipated by each resistor is the same.
 - C The current through each resistor is the same.
 - D The total voltage across the resistors is the sum of the voltage across each resistor.
- (13) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- A $25\ \Omega$.
 - B $50\ \Omega$.
 - C $100\ \Omega$.
 - D $0\ \Omega$.
- (14) The resistivity of a wire depends on:
- A area of cross-section.
 - B material.
 - C length, material and area of cross-section.
 - D length.
- (15) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- A $810\ \Omega$.
 - B $30\ \Omega$.
 - C $270\ \Omega$.
 - D $10\ \Omega$.
- (16) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:
- A $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
 - B all in series.
 - C $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
 - D all in parallel.
- (17) All of the wires in Figure 2 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (c).
 - B (d).
 - C (a).
 - D (b).
- (18) The unit of resistivity is:
- A ohm/m^2 .
 - B $\text{ohm}\cdot\text{m}$.
 - C ohm/m .
 - D ohm .
- (19) A battery is used to:
- A safeguard against short-circuit.
 - B maintain a potential difference.
 - C measure electric current.
 - D measure electric potential.
- (20) The current in a wire:
- A depends only on the potential difference applied.
 - B depends on both resistance and potential difference.
 - C does not depend on resistance and potential difference.
 - D depends only on the resistance of the wire.
- (21) In Figure 3 at the end of the text,
- A $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 - B $3\ \Omega$, $6\ \Omega$ and $9\ \Omega$ are in parallel.
 - C $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
 - D $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
- (22) The unit of current is:
- A coulomb.
 - B watt.
 - C volt.
 - D ampere.
- (23) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- A $D \cdot P^2$.
 - B D^2/P .
 - C $D \cdot P$.
 - D $D^2 \cdot P$.
- (24) Complete the following statement: "The electromotive force is:
- A the maximum electric potential energy stored within a battery".

- (B)** the force that accelerates protons through a wire when a battery is connected to it".
- (C)** the force that accelerates electrons through a wire when a battery is connected to it".
- (D)** the maximum potential difference between the terminals of a battery".
- (25)** Two aluminum wires have the same length and different cross-sectional area. Wire *B* has twice the radius of that of wire *A*. Determine how the resistance of wire *B* compares to the resistance of wire *A*.
- [A]** $\frac{R_B}{R_A} = \frac{1}{1}$.
- [B]** $\frac{R_B}{R_A} = \frac{1}{2}$.
- [C]** $\frac{R_B}{R_A} = \frac{1}{4}$.
- [D]** $\frac{R_B}{R_A} = \frac{2}{1}$.
- (26)** Determine which one of the following statements concerning resistors in series is *true*.
- [A]** The power dissipated by each resistor is the same.
- [B]** The voltage across each resistor is the same.
- [C]** The current through each resistor is the same.
- [D]** The total current through the resistors is the sum of the current through each resistor.
- (27)** When there is an electric current passing through a wire, the particles moving are:
- [A]** atoms.
- [B]** ions.
- [C]** protons.
- [D]** electrons.
- (28)** In Figure 4 at the end of the text, the resistance across *AB* is:
- [A]** 1 Ω .
- [B]** 2 Ω .
- [C]** 4 Ω .
- [D]** 0.5 Ω .
- (29)** The unit of electric power is:
- [A]** joule.
- [B]** ampere.
- [C]** watt.
- [D]** volt.
- (30)** Determine which of the graphs in Figure 5 at the end of the text represents Ohm's law for a solid conductor.
- [A]** (a).
- [B]** (c).
- [C]** (d).
- [D]** (b).
- (31)** Two resistances of 100 Ω and zero ohm are connected in series. The overall resistance will be:
- [A]** 100 Ω .
- [B]** 0 Ω .
- [C]** 25 Ω .
- [D]** 50 Ω .
- (32)** Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A]** 6 Ω .
- [B]** 3 Ω .
- [C]** 2 Ω .
- [D]** 1 Ω .
- (33)** The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:
- [A]** 40 V.
- [B]** 100 V.
- [C]** 1 V.
- [D]** 4 V.
- (34)** Joule/coulomb is same as:
- [A]** watt.
- [B]** volt.
- [C]** ohm.
- [D]** ampere.
- (35)** Determine which of the following statements does not represent Ohm's law.
- [A]** potential difference = current \times resistance.
- [B]** current / potential difference = constant.
- [C]** current = resistance \times potential difference.
- [D]** potential difference / current = constant.
- (36)** The electric current as a function of voltage of a wire is presented by the graph in Figure 6. Compute the resistance of the wire.
- [A]** 0.4 Ω .
- [B]** 1 Ω .
- [C]** 0.8 Ω .
- [D]** 1.7 Ω .
- (37)** If *D* is the intensity of current circulating in a resistor with resistance *F*, the power dissipated by the resistor is described by the formula:
- [A]** $D \cdot F$.
- [B]** D^2/F .
- [C]** $D \cdot F^2$.
- [D]** $D^2 \cdot F$.
- (38)** The electric current as a function of voltage of a wire is presented by the graph in Figure 6. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- A 20 W.
 B 15 W.
 C 10 W.
 D 5 W.

(39) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- A $\frac{R_Y}{R_X} = \frac{1}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{4}$.

- C $\frac{R_Y}{R_X} = \frac{1}{2}$.
 D $\frac{R_Y}{R_X} = \frac{2}{1}$.

(40) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Resistance.
 B Current.
 C Power.
 D Voltage.

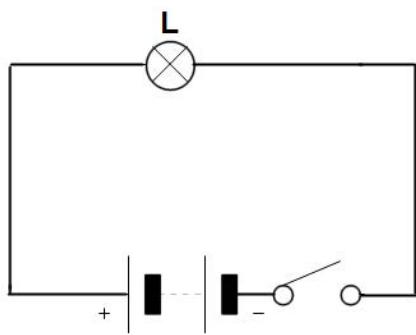


Figura 1

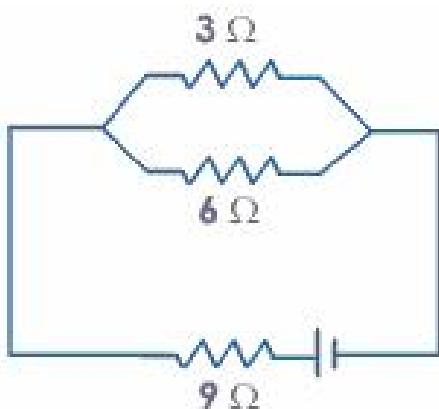


Figura 3

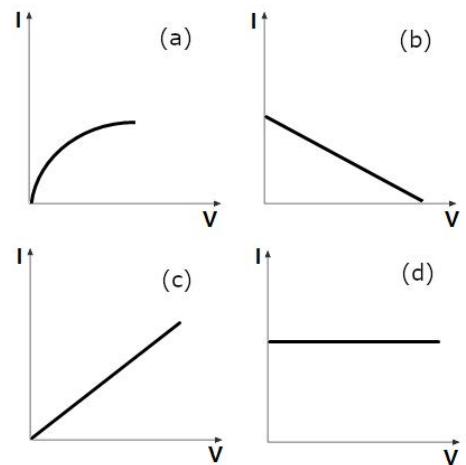


Figura 5

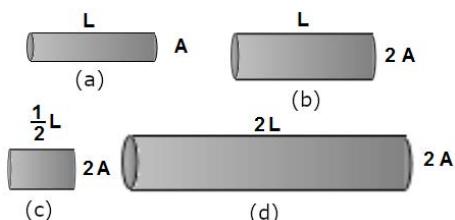


Figura 2

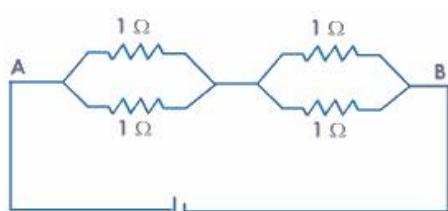


Figura 4

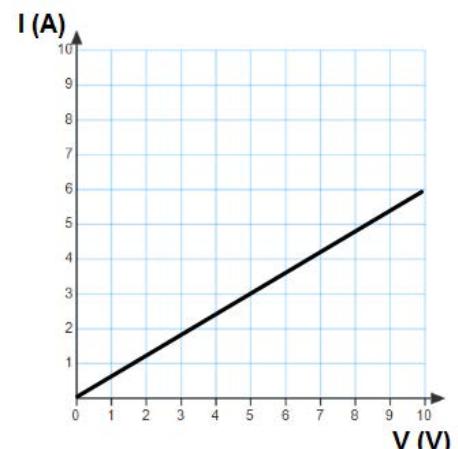


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 18

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- 1 When a current I flows through a resistance R for time t the electrical energy spent is given by:
- A $I^2 R/t$.
 B $I^2 R t$.
 C IRt .
 D $IR^2 t$.
- 2 When there is an electric current passing through a wire, the particles moving are:
- A ions.
 B atoms.
 C protons.
 D electrons.
- 3 Determine which one of the following statements concerning resistors in parallel is *true*.
- A The voltage across each resistor is the same.
 B The power dissipated by each resistor is the same.
 C The current through each resistor is the same.
 D The total voltage across the resistors is the sum of the voltage across each resistor.
- 4 The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 0.2 W.
 B 5 W.
 C 0.5 W.
 D 2 W.
- 5 If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- A $D^2 \cdot P$.
- 6 The unit of electric power is:
- A volt.
 B joule.
 C ampere.
 D watt.
- 7 Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{1}{4}$.
 B $\frac{R_B}{R_A} = \frac{1}{2}$.
 C $\frac{R_B}{R_A} = \frac{1}{1}$.
 D $\frac{R_B}{R_A} = \frac{2}{1}$.
- 8 Determine which one of the following statements concerning resistors in series is *true*.
- A The total current through the resistors is the sum of the current through each resistor.
 B The voltage across each resistor is the same.
 C The current through each resistor is the same.
 D The power dissipated by each resistor is the same.
- 9 If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A D^2/F .
 B $D \cdot F^2$.
 C $D^2 \cdot F$.

D $D \cdot F.$

- (10) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.

A 1 Ω .
 B 0.8 Ω .
 C 0.4 Ω .
 D 1.7 Ω .

- (11) Determine which of the following statements does not represent Ohm's law.

A potential difference = current \times resistance.
 B potential difference / current = constant.
 C current / potential difference = constant.
 D current = resistance \times potential difference.

- (12) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{L}{\rho A}$.
 B $R = \frac{\rho L}{A}$.
 C $R = \frac{A}{\rho L}$.
 D $R = \frac{\rho A}{L}$.

- (13) The resistivity of a wire depends on:

A material.
 B length.
 C length, material and area of cross-section.
 D area of cross-section.

- (14) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:

A 270 Ω .
 B 10 Ω .
 C 30 Ω .
 D 810 Ω .

- (15) In Figure 2 at the end of the text,

A 3 Ω , 6 Ω are in parallel and 9 Ω is in series.
 B 3 Ω , 6 Ω and 9 Ω are in parallel.
 C 9 Ω and 6 Ω are in parallel and the combination is in series with 3 Ω .
 D 6 Ω , 3 Ω and 9 Ω are in series.

- (16) Two resistances of 100 Ω and zero ohm are connected in parallel. The overall resistance will be:

A 100 Ω .
 B 0 Ω .

C 50 Ω .

D 25 Ω .

- (17) The current in a wire:

A depends on both resistance and potential difference.
 B does not depend on resistance and potential difference.
 C depends only on the potential difference applied.
 D depends only on the resistance of the wire.

- (18) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.

A 20 W.
 B 5 W.
 C 15 W.
 D 10 W.

- (19) A battery is used to:

A measure electric current.
 B maintain a potential difference.
 C safeguard against short-circuit.
 D measure electric potential.

- (20) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 1 Ω .
 B 3 Ω .
 C 6 Ω .
 D 2 Ω .

- (21) Two resistances of 100 Ω and zero ohm are connected in series. The overall resistance will be:

A 100 Ω .
 B 0 Ω .
 C 25 Ω .
 D 50 Ω .

- (22) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

A 200 C.
 B 600 C.
 C 500 C.
 D 400 C.

- (23) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

A power.
 B resistance.
 C potential difference.
 D current.

(24) Complete the following statement: "The electromotive force is:

- [A] the force that accelerates protons through a wire when a battery is connected to it".
- [B] the maximum potential difference between the terminals of a battery".
- [C] the maximum electric potential energy stored within a battery".
- [D] the force that accelerates electrons through a wire when a battery is connected to it".

(25) The unit of current is:

- [A] volt.
- [B] watt.
- [C] ampere.
- [D] coulomb.

(26) The unit of resistivity is:

- [A] ohm·m.
- [B] ohm/m.
- [C] ohm/m².
- [D] ohm.

(27) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

- [A] 1Ω .
- [B] 6Ω .
- [C] 3Ω .
- [D] 2Ω .

(28) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.

- [A] (b).
- [B] (d).
- [C] (a).
- [D] (c).

(29) Joule/coulomb is same as:

- [A] ohm.
- [B] watt.
- [C] volt.
- [D] ampere.

(30) Ohm's law relates potential difference with:

- [A] current.
- [B] power.
- [C] energy.
- [D] time.

(31) In Figure 4 at the end of the text, the resistance across AB is:

- [A] 0.5Ω .
- [B] 1Ω .
- [C] 2Ω .
- [D] 4Ω .

(32) All of the wires in Figure 5 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- [A] (d).
- [B] (a).
- [C] (b).
- [D] (c).

(33) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

- [A] 2Ω and 3Ω in series and the combination in parallel to 4Ω .
- [B] all in series.
- [C] all in parallel.
- [D] 2Ω and 3Ω in parallel and the combination in series with 4Ω .

(34) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- [A] Voltage.
- [B] Resistance.
- [C] Power.
- [D] Current.

(35) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- [A] $\frac{R_Y}{R_X} = \frac{1}{1}$.
- [B] $\frac{R_Y}{R_X} = \frac{1}{4}$.
- [C] $\frac{R_Y}{R_X} = \frac{2}{1}$.
- [D] $\frac{R_Y}{R_X} = \frac{1}{2}$.

(36) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 6 at the end of the text.

- [A] To the left.
- [B] Downward.
- [C] To the right.
- [D] Upward.

(37) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

- [A] 100 V.
- [B] 1 V.
- [C] 40 V.
- [D] 4 V.

- (38) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- [A] 60 J.
 [B] 30 J.
 [C] 120 J.
 [D] 15 J.
- (39) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- [A] 36.
- (40) A positive charge released from rest:
- [A] moves towards the regions of lower potential.
 [B] moves towards the regions of equal potential.
 [C] does not move.
 [D] moves towards the regions of higher potential.

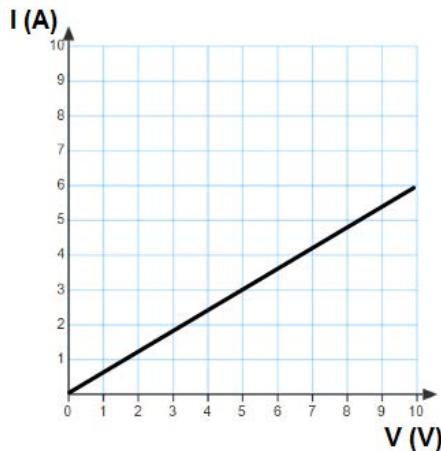


Figura 1

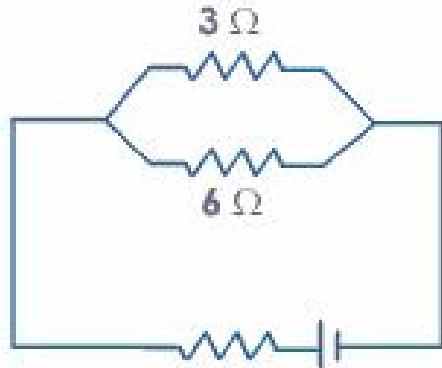


Figura 2

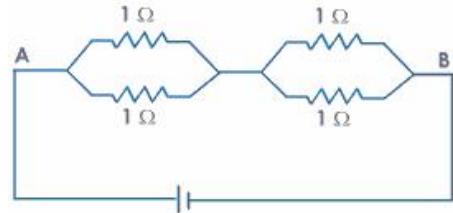


Figura 4

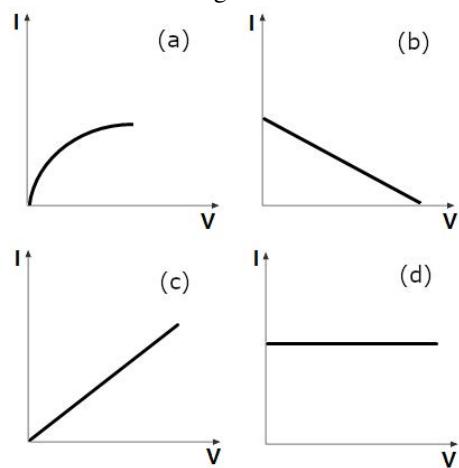


Figura 3

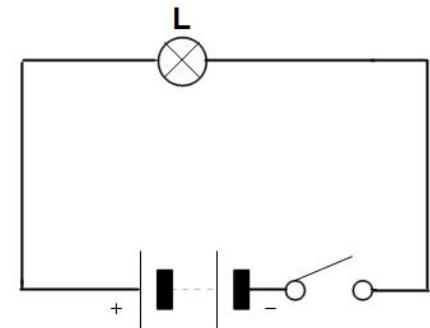


Figura 5

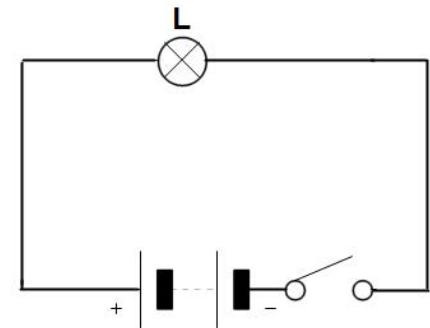


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 19

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) In Figure 1 at the end of the text, the resistance across AB is:
- [A] 2 Ω .
 [B] 0.5 Ω .
 [C] 4 Ω .
 [D] 1 Ω .
- (2) The unit of resistivity is:
- [A] ohm/m².
 [B] ohm.
 [C] ohm/m.
 [D] ohm·m.
- (3) The unit of electric power is:
- [A] volt.
 [B] joule.
 [C] ampere.
 [D] watt.
- (4) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] $D \cdot P$.
 [B] D^2/P .
 [C] $D^2 \cdot P$.
 [D] $D \cdot P^2$.
- (5) Three resistors 2 Ω , 3 Ω and 4 Ω are connected so that the equivalent resistance is 9 Ω . The resistors are connected:
- [A] all in parallel.
 [B] all in series.
 [C] 2 Ω and 3 Ω in series and the combination in parallel to 4 Ω .
- (6) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 6 Ω .
 [B] 3 Ω .
 [C] 1 Ω .
 [D] 2 Ω .
- (7) The resistivity of a wire depends on:
- [A] material.
 [B] area of cross-section.
 [C] length.
 [D] length, material and area of cross-section.
- (8) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- [A] $D \cdot F$.
 [B] $D^2 \cdot F$.
 [C] $D \cdot F^2$.
 [D] D^2/F .
- (9) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- [A] $\frac{R_Y}{R_X} = \frac{1}{1}$.
 [B] $\frac{R_Y}{R_X} = \frac{1}{4}$.
 [C] $\frac{R_Y}{R_X} = \frac{2}{1}$.
 [D] $\frac{R_Y}{R_X} = \frac{1}{2}$.

- (10) When there is an electric current passing through a wire, the particles moving are:
- A protons.
 - B electrons.
 - C atoms.
 - D ions.
- (11) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 400 C.
 - B 600 C.
 - C 200 C.
 - D 500 C.
- (12) A battery is used to:
- A maintain a potential difference.
 - B safeguard against short-circuit.
 - C measure electric potential.
 - D measure electric current.
- (13) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.
- A Upward.
 - B To the left.
 - C Downward.
 - D To the right.
- (14) Determine which one of the following statements concerning resistors in parallel is *true*.
- A The current through each resistor is the same.
 - B The voltage across each resistor is the same.
 - C The power dissipated by each resistor is the same.
 - D The total voltage across the resistors is the sum of the voltage across each resistor.
- (15) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
- A $100\ \Omega$.
 - B $50\ \Omega$.
 - C $0\ \Omega$.
 - D $25\ \Omega$.
- (16) The unit of current is:
- A ampere.
 - B coulomb.
 - C volt.
 - D watt.
- (17) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- A $270\ \Omega$.
 - B $810\ \Omega$.
 - C $30\ \Omega$.
 - D $10\ \Omega$.
- (18) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 5 W.
 - B 0.2 W.
 - C 0.5 W.
 - D 2 W.
- (19) Ohm's law relates potential difference with:
- A power.
 - B energy.
 - C time.
 - D current.
- (20) A positive charge released from rest:
- A does not move.
 - B moves towards the regions of higher potential.
 - C moves towards the regions of lower potential.
 - D moves towards the regions of equal potential.
- (21) Joule/coulomb is same as:
- A volt.
 - B ampere.
 - C watt.
 - D ohm.
- (22) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{2}{1}$.
 - B $\frac{R_B}{R_A} = \frac{1}{4}$.
 - C $\frac{R_B}{R_A} = \frac{1}{1}$.
 - D $\frac{R_B}{R_A} = \frac{1}{2}$.
- (23) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- A $R = \frac{\rho A}{L}$.
 - B $R = \frac{\rho L}{A}$.
 - C $R = \frac{A}{\rho L}$.
 - D $R = \frac{L}{\rho A}$.

- (24) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A current.
 - B resistance.
 - C power.
 - D potential difference.
- (25) Determine which of the following statements does not represent Ohm's law.
- A potential difference / current = constant.
 - B current = resistance × potential difference.
 - C current / potential difference = constant.
 - D potential difference = current × resistance.
- (26) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- A 6Ω .
 - B 3Ω .
 - C 1Ω .
 - D 2Ω .
- (27) The current in a wire:
- A depends only on the resistance of the wire.
 - B does not depend on resistance and potential difference.
 - C depends on both resistance and potential difference.
 - D depends only on the potential difference applied.
- (28) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.
- A (a).
 - B (c).
 - C (d).
 - D (b).
- (29) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:
- A 0Ω .
 - B 25Ω .
 - C 50Ω .
 - D 100Ω .
- (30) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- A I^2R/t .
 - B IR^2t .
 - C IRt .
 - D I^2Rt .
- (31) Determine which one of the following statements concerning resistors in series is true.
- A The total current through the resistors is the sum of the current through each resistor.
 - B The voltage across each resistor is the same.
 - C The current through each resistor is the same.
 - D The power dissipated by each resistor is the same.
- (32) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the resistance of the wire.
- A 0.8Ω .
 - B 1.7Ω .
 - C 1Ω .
 - D 0.4Ω .
- (33) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the power dissipated in the resistor when the applied voltage is 5 V .
- A 10 W .
 - B 5 W .
 - C 20 W .
 - D 15 W .
- (34) In Figure 5 at the end of the text,
- A 3Ω , 6Ω and Ω are in parallel.
 - B 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
 - C 3Ω , 6Ω are in parallel and 9Ω is in series.
 - D 6Ω , 3Ω and 9Ω are in series.
- (35) All of the wires in Figure 6 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (b).
 - B (d).
 - C (a).
 - D (c).
- (36) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:
- A 1 V .
 - B 4 V .
 - C 40 V .
 - D 100 V .
- (37) Heat produced in a current carrying wire in 5s is 60 J . The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A 60 J .
 - B 30 J .
 - C 15 J .
 - D 120 J .
- (38) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Voltage.
- B Resistance.
- C Current.
- D Power.

(39) Complete the following statement: "The electromotive force is:

- A the maximum potential difference between the terminals of a battery".
- B the maximum electric potential energy stored within a battery".

C the force that accelerates electrons through a wire when a battery is connected to it".

D the force that accelerates protons through a wire when a battery is connected to it".

(40) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

- A 4.8×10^{15} .
- B 2.2×10^{20} .
- C 6.4×10^{18} .
- D 36.

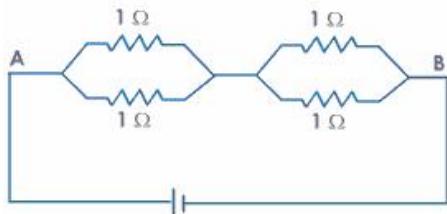


Figura 1

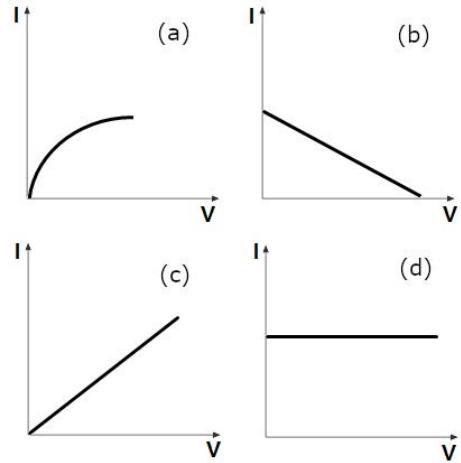


Figura 3

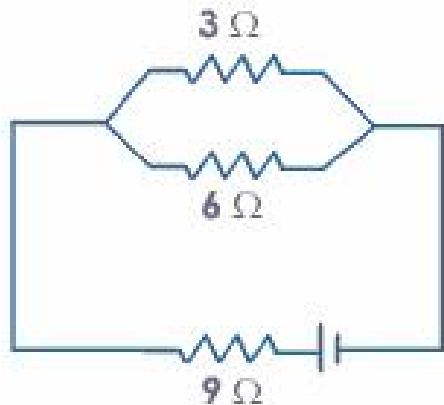


Figura 5

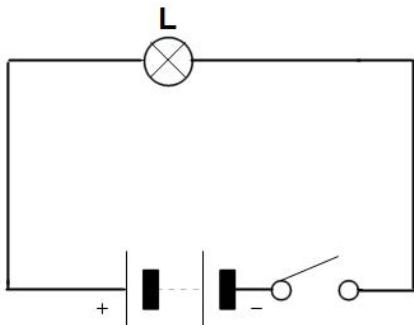


Figura 2

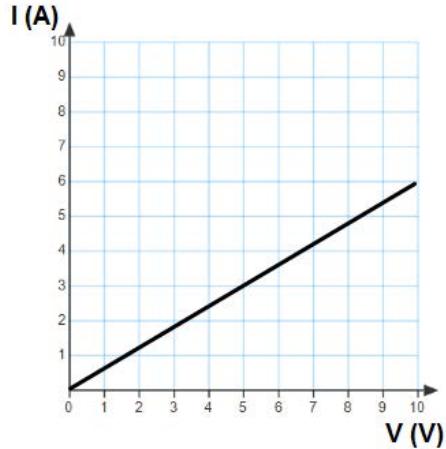


Figura 4

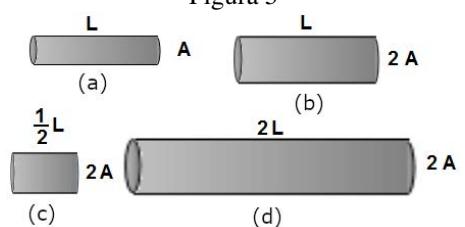


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 20

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

- A $100\ \Omega$.
- B $0\ \Omega$.
- C $50\ \Omega$.
- D $25\ \Omega$.

A $\frac{R_Y}{R_X} = \frac{1}{2}$.

B $\frac{R_Y}{R_X} = \frac{1}{4}$.

C $\frac{R_Y}{R_X} = \frac{1}{1}$.

D $\frac{R_Y}{R_X} = \frac{2}{1}$.

- ② Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.

- A To the left.
- B To the right.
- C Upward.
- D Downward.

- ⑥ Ohm's law relates potential difference with:

- A energy.
- B power.
- C time.
- D current.

- ③ All of the wires in Figure 2 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- A (a).
- B (d).
- C (c).
- D (b).

- ⑦ The unit of electric power is:

- A ampere.
- B joule.
- C watt.
- D volt.

- ④ Determine which one of the following statements concerning resistors in parallel is *true*.

- A The voltage across each resistor is the same.
- B The power dissipated by each resistor is the same.
- C The total voltage across the resistors is the sum of the voltage across each resistor.
- D The current through each resistor is the same.

- ⑧ Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{1}{2}$.

B $\frac{R_B}{R_A} = \frac{2}{1}$.

C $\frac{R_B}{R_A} = \frac{1}{1}$.

D $\frac{R_B}{R_A} = \frac{1}{4}$.

- ⑤ Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- ⑨ The potential difference required to pass a current $0.2\ A$ in a wire of resistance $20\ \Omega$ is:

- A 4 V.

- B 40 V.
- C 100 V.
- D 1 V.

(10) A battery is used to:

- A measure electric potential.
- B measure electric current.
- C safeguard against short-circuit.
- D maintain a potential difference.

(11) Determine which one of the following statements concerning resistors in series is *true*.

- A The voltage across each resistor is the same.
- B The power dissipated by each resistor is the same.
- C The current through each resistor is the same.
- D The total current through the resistors is the sum of the current through each resistor.

(12) The current in a wire:

- A depends only on the resistance of the wire.
- B does not depend on resistance and potential difference.
- C depends only on the potential difference applied.
- D depends on both resistance and potential difference.

(13) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

- A $25\ \Omega$.
- B $50\ \Omega$.
- C $0\ \Omega$.
- D $100\ \Omega$.

(14) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:

- A $30\ \Omega$.
- B $270\ \Omega$.
- C $10\ \Omega$.
- D $810\ \Omega$.

(15) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.

- A (b).
- B (d).
- C (c).
- D (a).

(16) Compute the number of electrons flowing through a battery that delivers a current of $3.0\ A$ for $12\ s$.

- A 4.8×10^{15} .
- B 6.4×10^{18} .
- C 2.2×10^{20} .

- D 36.

(17) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A power.
- B potential difference.
- C resistance.
- D current.

(18) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- A $R = \frac{\rho A}{L}$.
- B $R = \frac{L}{\rho A}$.
- C $R = \frac{\rho L}{A}$.
- D $R = \frac{A}{\rho L}$.

(19) Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A $6\ \Omega$.
- B $3\ \Omega$.
- C $1\ \Omega$.
- D $2\ \Omega$.

(20) In Figure 4 at the end of the text,

- A $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
- B $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
- C $3\ \Omega$, $6\ \Omega$ and $9\ \Omega$ are in parallel.
- D $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.

(21) Joule/coulomb is same as:

- A ohm.
- B volt.
- C ampere.
- D watt.

(22) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the power dissipated in the resistor when the applied voltage is $5\ V$.

- A 5 W.
- B 15 W.
- C 20 W.
- D 10 W.

(23) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A IRt .
- B I^2Rt .
- C IR^2t .

D I^2R/t .

(24) The resistivity of a wire depends on:

- A length, material and area of cross-section.
- B material.
- C area of cross-section.
- D length.

(25) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- A 5 W.
- B 0.5 W.
- C 0.2 W.
- D 2 W.

(26) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Voltage.
- B Current.
- C Resistance.
- D Power.

(27) Complete the following statement: "The electromotive force is:

- A the maximum potential difference between the terminals of a battery".
- B the maximum electric potential energy stored within a battery".
- C the force that accelerates electrons through a wire when a battery is connected to it".
- D the force that accelerates protons through a wire when a battery is connected to it".

(28) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 600 C.
- B 500 C.
- C 200 C.
- D 400 C.

(29) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A D^2/P .
- B $D \cdot P$.
- C $D^2 \cdot P$.
- D $D \cdot P^2$.

(30) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the resistance of the wire.

- A 1Ω .

B 1.7Ω .

C 0.4Ω .

D 0.8Ω .

(31) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

- A 2Ω and 3Ω in parallel and the combination in series with 4Ω .
- B all in series.
- C all in parallel.
- D 2Ω and 3Ω in series and the combination in parallel to 4Ω .

(32) Determine which of the following statements does not represent Ohm's law.

- A potential difference = current \times resistance.
- B current = resistance \times potential difference.
- C potential difference / current = constant.
- D current / potential difference = constant.

(33) A positive charge released from rest:

- A does not move.
- B moves towards the regions of lower potential.
- C moves towards the regions of higher potential.
- D moves towards the regions of equal potential.

(34) In Figure 6 at the end of the text, the resistance across AB is:

- A 2Ω .
- B 0.5Ω .
- C 1Ω .
- D 4Ω .

(35) The unit of current is:

- A volt.
- B ampere.
- C watt.
- D coulomb.

(36) The unit of resistivity is:

- A ohm/m.
- B ohm/m².
- C ohm.m.
- D ohm.

(37) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D \cdot F$.
- B D^2/F .
- C $D^2 \cdot F$.
- D $D \cdot F^2$.

- (38) When there is an electric current passing through a wire, the particles moving are:
- A protons.
 B atoms.
 C electrons.
 D ions.
- (39) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- A 2Ω .
- (40) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A 60 J.
 B 120 J.
 C 30 J.
 D 15 J.

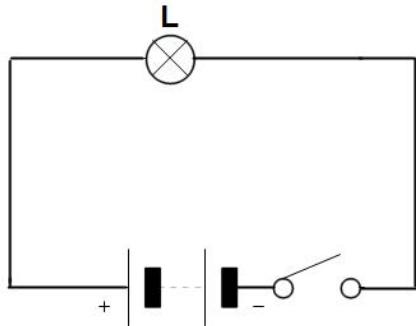


Figura 1

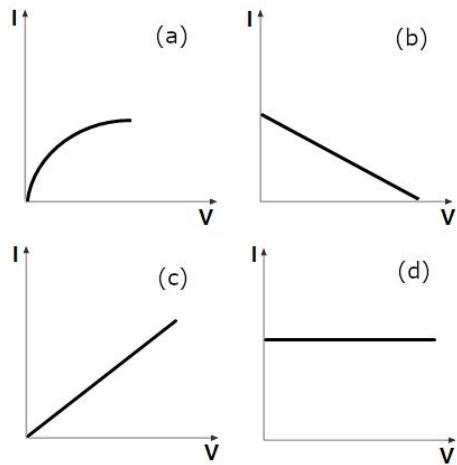


Figura 3

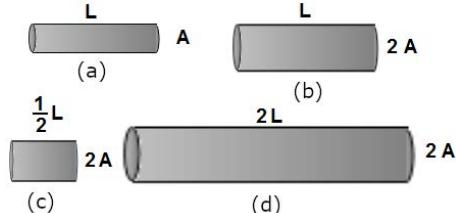


Figura 2

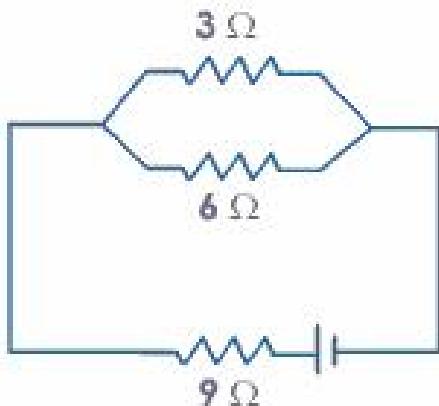


Figura 4

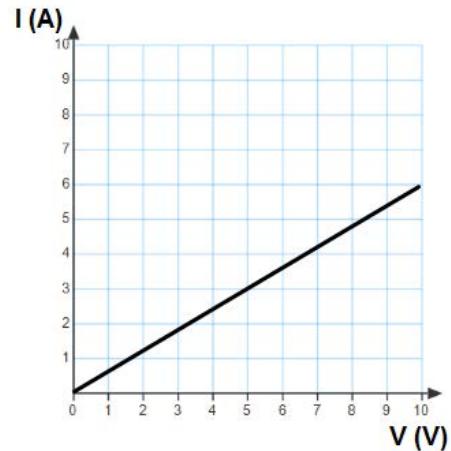


Figura 5

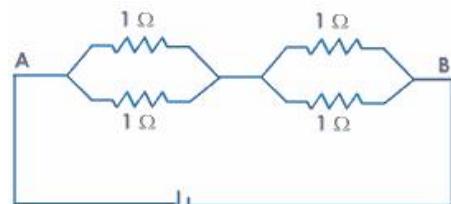


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 21

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																				
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	

- (1) When there is an electric current passing through a wire, the particles moving are:
- A atoms.
 B protons.
 C ions.
 D electrons.
- (2) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $R_B = \frac{1}{4} R_A$.
 B $R_B = \frac{1}{2} R_A$.
 C $R_B = \frac{2}{R_A}$.
 D $R_B = \frac{1}{R_A}$.
- (3) The unit of current is:
- A volt.
 B watt.
 C coulomb.
 D ampere.
- (4) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A resistance.
 B current.
 C potential difference.
 D power.
- (5) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- (6) The potential difference required to pass a current $0.2\ A$ in a wire of resistance $20\ \Omega$ is:
- A $40\ V$.
 B $4\ V$.
 C $100\ V$.
 D $1\ V$.
- (7) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.
- A $2\ \Omega$.
 B $3\ \Omega$.
 C $1\ \Omega$.
 D $6\ \Omega$.
- (8) The current in a wire:
- A depends on both resistance and potential difference.
 B does not depend on resistance and potential difference.
 C depends only on the resistance of the wire.
 D depends only on the potential difference applied.
- (9) The unit of electric power is:
- A ampere.
 B watt.
 C joule.
 D volt.
- (10) Determine which one of the following statements concerning resistors in series is *true*.

- (A) The total current through the resistors is the sum of the current through each resistor.
 (B) The current through each resistor is the same.
 (C) The power dissipated by each resistor is the same.
 (D) The voltage across each resistor is the same.
- (11) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.
 (A) Upward.
 (B) To the right.
 (C) To the left.
 (D) Downward.
- (12) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
 (A) 200 C.
 (B) 400 C.
 (C) 600 C.
 (D) 500 C.
- (13) All of the wires in Figure 2 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
 (A) (c).
 (B) (b).
 (C) (a).
 (D) (d).
- (14) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
 (A) 0.2 W.
 (B) 0.5 W.
 (C) 5 W.
 (D) 2 W.
- (15) When a current I flows through a resistance R for time t the electrical energy spent is given by:
 (A) I^2R/t .
 (B) I^2Rt .
 (C) IR^2t .
 (D) IRt .
- (16) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
 (A) D^2/F .
 (B) $D^2 \cdot F$.
 (C) $D \cdot F^2$.
 (D) $D \cdot F$.
- (17) The resistivity of a wire depends on:
 (A) length.
 (B) length, material and area of cross-section.
 (C) material.
 (D) area of cross-section.
- (18) Joule/coulomb is same as:
 (A) volt.
 (B) watt.
 (C) ohm.
 (D) ampere.
- (19) The unit of resistivity is:
 (A) ohm·m.
 (B) ohm/m.
 (C) ohm/m².
 (D) ohm.
- (20) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
 (A) 2Ω .
 (B) 6Ω .
 (C) 1Ω .
 (D) 3Ω .
- (21) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:
 (A) 10Ω .
 (B) 810Ω .
 (C) 270Ω .
 (D) 30Ω .
- (22) Determine which of the following statements does not represent Ohm's law.
 (A) current = resistance × potential difference.
 (B) potential difference = current × resistance.
 (C) current / potential difference = constant.
 (D) potential difference / current = constant.
- (23) Ohm's law relates potential difference with:
 (A) current.
 (B) energy.
 (C) power.
 (D) time.
- (24) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
 (A) 15 J.
 (B) 30 J.
 (C) 120 J.

D 60 J.

- (25) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.

A (c).
 B (b).
 C (d).
 D (a).

- (26) In Figure 4 at the end of the text,

A $3\ \Omega$, $6\ \Omega$ and Ω are in parallel.
 B $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 C $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 D $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.

- (27) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

A $D^2 \cdot P$.
 B $D \cdot P$.
 C $D \cdot P^2$.
 D D^2/P .

- (28) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .

A 4.8×10^{15} .
 B 36.
 C 2.2×10^{20} .
 D 6.4×10^{18} .

- (29) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the power dissipated in the resistor when the applied voltage is 5 V .

A 20 W.
 B 15 W.
 C 5 W.
 D 10 W.

- (30) Determine which one of the following statements concerning resistors in parallel is *true*.

A The total voltage across the resistors is the sum of the voltage across each resistor.
 B The current through each resistor is the same.
 C The power dissipated by each resistor is the same.
 D The voltage across each resistor is the same.

- (31) Complete the following statement: "The electromotive force is:

A the force that accelerates protons through a wire when a battery is connected to it".
 B the force that accelerates electrons through a wire when a battery is connected to it".

C the maximum electric potential energy stored within a battery".

D the maximum potential difference between the terminals of a battery".

- (32) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{1}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{2}$.
 C $\frac{R_Y}{R_X} = \frac{1}{4}$.
 D $\frac{R_Y}{R_X} = \frac{2}{1}$.

- (33) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:

A $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
 B all in parallel.
 C all in series.
 D $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.

- (34) A positive charge released from rest:

A does not move.
 B moves towards the regions of equal potential.
 C moves towards the regions of lower potential.
 D moves towards the regions of higher potential.

- (35) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

A $25\ \Omega$.
 B $0\ \Omega$.
 C $100\ \Omega$.
 D $50\ \Omega$.

- (36) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

A Voltage.
 B Current.
 C Power.
 D Resistance.

- (37) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{\rho A}{L}$.
 B $R = \frac{L}{\rho A}$.
 C $R = \frac{A}{\rho L}$.
 D $R = \frac{\rho L}{A}$.

(38) A battery is used to:

- A measure electric current.
- B maintain a potential difference.
- C safeguard against short-circuit.
- D measure electric potential.

(39) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the resistance of the wire.

- A 0.8Ω .

B 1Ω .

C 1.7Ω .

D 0.4Ω .

(40) In Figure 6 at the end of the text, the resistance across AB is:

A 1Ω .

B 0.5Ω .

C 4Ω .

D 2Ω .

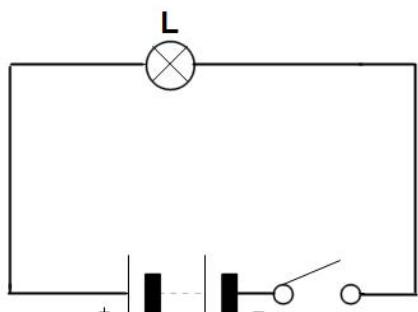


Figura 1

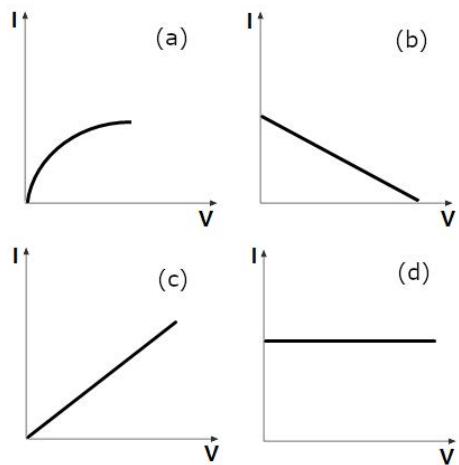


Figura 3

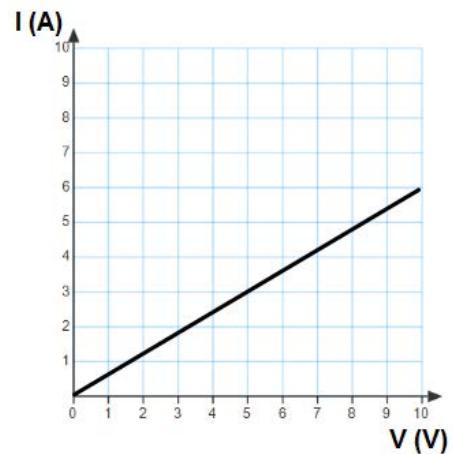


Figura 5

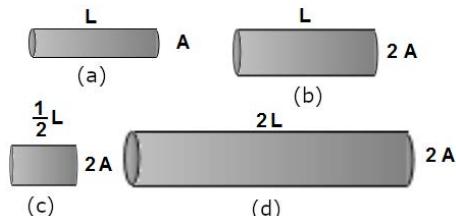


Figura 2

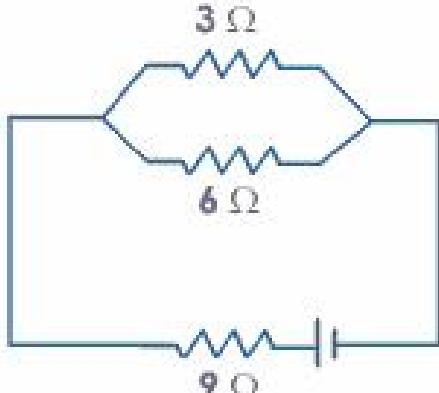


Figura 4

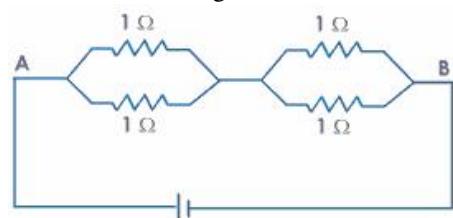


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 22

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 3 Ω.
 [B] 2 Ω.
 [C] 6 Ω.
 [D] 1 Ω.
- (2) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 2 W.
 [B] 5 W.
 [C] 0.5 W.
 [D] 0.2 W.
- (3) In Figure 1 at the end of the text,
- [A] 3 Ω, 6 Ω are in parallel and 9 Ω is in series.
 [B] 6 Ω, 3 Ω and 9 Ω are in series.
 [C] 3 Ω, 6 Ω and 9 Ω are in parallel.
 [D] 9 Ω and 6 Ω are in parallel and the combination is in series with 3 Ω.
- (4) The unit of current is:
- [A] watt.
 [B] ampere.
 [C] volt.
 [D] coulomb.
- (5) When there is an electric current passing through a wire, the particles moving are:
- [A] ions.
 [B] protons.
- [C] atoms.
 [D] electrons.
- (6) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- [A] $\frac{R_Y}{R_X} = \frac{1}{4}$.
 [B] $\frac{R_Y}{R_X} = \frac{1}{1}$.
 [C] $\frac{R_Y}{R_X} = \frac{2}{1}$.
 [D] $\frac{R_Y}{R_X} = \frac{1}{2}$.
- (7) Determine which one of the following statements concerning resistors in parallel is *true*.
- [A] The power dissipated by each resistor is the same.
 [B] The current through each resistor is the same.
 [C] The voltage across each resistor is the same.
 [D] The total voltage across the resistors is the sum of the voltage across each resistor.
- (8) In Figure 2 at the end of the text, the resistance across AB is:
- [A] 4 Ω.
 [B] 1 Ω.
 [C] 2 Ω.
 [D] 0.5 Ω.
- (9) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- [A] resistance.
 [B] current.
 [C] power.
 [D] potential difference.

- (10) Determine which of the following statements does not represent Ohm's law.
- A current = resistance × potential difference.
 B potential difference = current × resistance.
 C current / potential difference = constant.
 D potential difference / current = constant.
- (11) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D \cdot F^2$.
 B D^2/F .
 C $D \cdot F$.
 D $D^2 \cdot F$.
- (12) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 3 at the end of the text.
- A Upward.
 B To the left.
 C To the right.
 D Downward.
- (13) Ohm's law relates potential difference with:
- A current.
 B power.
 C time.
 D energy.
- (14) The resistivity of a wire depends on:
- A material.
 B length.
 C length, material and area of cross-section.
 D area of cross-section.
- (15) The current in a wire:
- A depends on both resistance and potential difference.
 B depends only on the resistance of the wire.
 C depends only on the potential difference applied.
 D does not depend on resistance and potential difference.
- (16) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- A 6Ω .
 B 2Ω .
 C 3Ω .
 D 1Ω .
- (17) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- A I^2R/t .
 B IR^2t .
 C I^2Rt .
 D IRt .
- (18) Determine which one of the following statements concerning resistors in series is *true*.
- A The total current through the resistors is the sum of the current through each resistor.
 B The current through each resistor is the same.
 C The power dissipated by each resistor is the same.
 D The voltage across each resistor is the same.
- (19) The unit of resistivity is:
- A ohm/m².
 B ohm·m.
 C ohm.
 D ohm/m.
- (20) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 200 C.
 B 400 C.
 C 500 C.
 D 600 C.
- (21) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- A 15 W.
 B 20 W.
 C 5 W.
 D 10 W.
- (22) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:
- A all in parallel.
 B all in series.
 C 2Ω and 3Ω in series and the combination in parallel to 4Ω .
 D 2Ω and 3Ω in parallel and the combination in series with 4Ω .
- (23) Determine which of the graphs in Figure 5 at the end of the text represents Ohm's law for a solid conductor.
- A (a).
 B (c).
 C (b).
 D (d).
- (24) A positive charge released from rest:
- A moves towards the regions of higher potential.
 B moves towards the regions of equal potential.

C does not move.

D moves towards the regions of lower potential.

(25) Joule/coulomb is same as:

A watt.

B ampere.

C ohm.

D volt.

(26) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

A 4.8×10^{15} .

B 2.2×10^{20} .

C 36.

D 6.4×10^{18} .

(27) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

A D^2/P .

B $D \cdot P^2$.

C $D^2 \cdot P$.

D $D \cdot P$.

(28) A battery is used to:

A measure electric potential.

B safeguard against short-circuit.

C measure electric current.

D maintain a potential difference.

(29) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

A Power.

B Resistance.

C Current.

D Voltage.

(30) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the resistance of the wire.

A 1 Ω .

B 0.8 Ω .

C 0.4 Ω .

D 1.7 Ω .

(31) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:

A 100 V.

B 1 V.

C 40 V.

D 4 V.

(32) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:

A 810 Ω .

B 30 Ω .

C 270 Ω .

D 10 Ω .

(33) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

A 15 J.

B 30 J.

C 60 J.

D 120 J.

(34) All of the wires in Figure 6 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (d).

B (a).

C (b).

D (c).

(35) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{1}{4}$.

B $\frac{R_B}{R_A} = \frac{1}{1}$.

C $\frac{R_B}{R_A} = \frac{1}{2}$.

D $\frac{R_B}{R_A} = \frac{2}{1}$.

(36) Two resistances of 100 Ω and zero ohm are connected in series. The overall resistance will be:

A 0 Ω .

B 100 Ω .

C 50 Ω .

D 25 Ω .

(37) Two resistances of 100 Ω and zero ohm are connected in parallel. The overall resistance will be:

A 0 Ω .

B 25 Ω .

C 100 Ω .

D 50 Ω .

(38) Complete the following statement: "The electromotive force is:

A the force that accelerates electrons through a wire when a battery is connected to it".

- B the maximum electric potential energy stored within a battery".
- C the maximum potential difference between the terminals of a battery".
- D the force that accelerates protons through a wire when a battery is connected to it".

(39) The unit of electric power is:

- A ampere.
- B joule.
- C volt.

D watt.

(40) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- A $R = \frac{\rho L}{A}$.
- B $R = \frac{\rho A}{L}$.
- C $R = \frac{A}{\rho L}$.
- D $R = \frac{L}{\rho A}$.

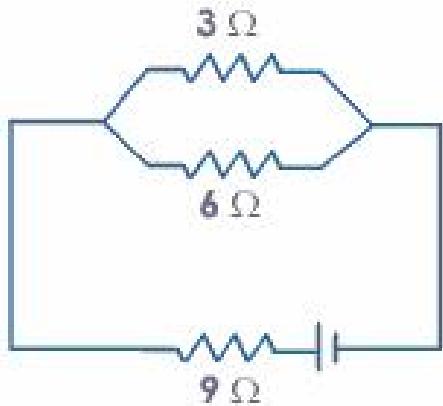


Figura 1

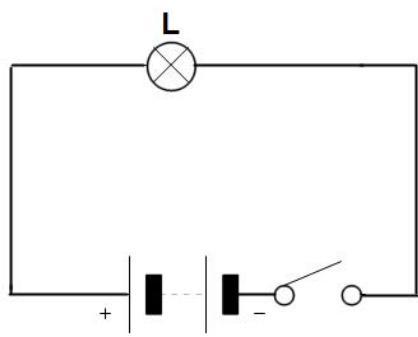


Figura 3

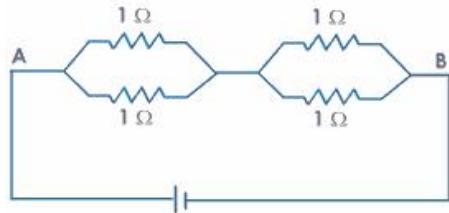


Figura 2

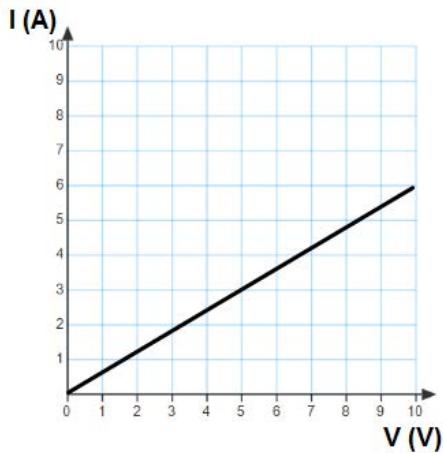


Figura 4

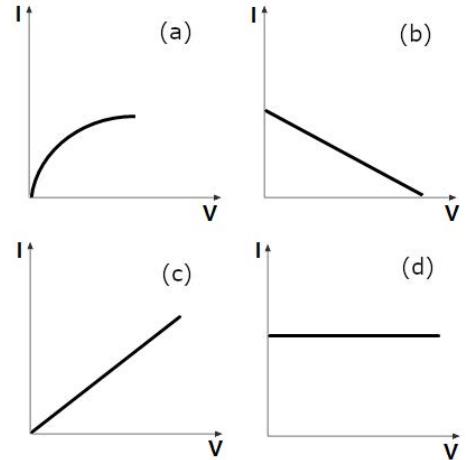


Figura 5

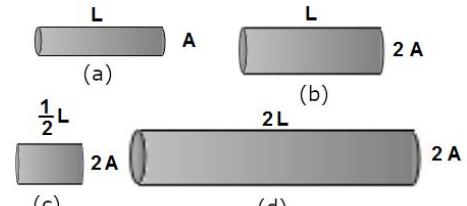


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 23

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- A I^2Rt .
 B IRt .
 C I^2R/t .
 D IR^2t .
- (2) A battery is used to:
- A measure electric current.
 B safeguard against short-circuit.
 C maintain a potential difference.
 D measure electric potential.
- (3) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:
- A 40 V.
 B 4 V.
 C 1 V.
 D 100 V.
- (4) A positive charge released from rest:
- A moves towards the regions of lower potential.
 B moves towards the regions of equal potential.
 C does not move.
 D moves towards the regions of higher potential.
- (5) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 200 C.
 B 600 C.
 C 400 C.
- (6) Complete the following statement: “The electromotive force is:
- A the force that accelerates protons through a wire when a battery is connected to it”.
 B the maximum electric potential energy stored within a battery”.
 C the maximum potential difference between the terminals of a battery”.
 D the force that accelerates electrons through a wire when a battery is connected to it”.
- (7) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A resistance.
 B power.
 C current.
 D potential difference.
- (8) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.
- A 0.8 Ω .
 B 1.7 Ω .
 C 1 Ω .
 D 0.4 Ω .
- (9) When there is an electric current passing through a wire, the particles moving are:
- A ions.
 B protons.
 C electrons.
 D atoms.

- (10) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 2Ω .
 [B] 1Ω .
 [C] 6Ω .
 [D] 3Ω .
- (11) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- [A] $\frac{R_B}{R_A} = \frac{1}{4}$.
 [B] $\frac{R_B}{R_A} = \frac{2}{1}$.
 [C] $\frac{R_B}{R_A} = \frac{1}{1}$.
 [D] $\frac{R_B}{R_A} = \frac{1}{2}$.
- (12) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:
- [A] 100Ω .
 [B] 25Ω .
 [C] 0Ω .
 [D] 50Ω .
- (13) In Figure 2 at the end of the text, the resistance across AB is:
- [A] 0.5Ω .
 [B] 2Ω .
 [C] 4Ω .
 [D] 1Ω .
- (14) Determine which one of the following statements concerning resistors in series is *true*.
- [A] The power dissipated by each resistor is the same.
 [B] The current through each resistor is the same.
 [C] The total current through the resistors is the sum of the current through each resistor.
 [D] The voltage across each resistor is the same.
- (15) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- [A] 60 J.
 [B] 30 J.
 [C] 15 J.
 [D] 120 J.
- (16) The current in a wire:
- [A] does not depend on resistance and potential difference.
 [B] depends only on the potential difference applied.
- [C] depends on both resistance and potential difference.
 [D] depends only on the resistance of the wire.
- (17) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 0.5 W.
 [B] 0.2 W.
 [C] 5 W.
 [D] 2 W.
- (18) The unit of resistivity is:
- [A] ohm/m^2 .
 [B] $\text{ohm}\cdot\text{m}$.
 [C] ohm .
 [D] ohm/m .
- (19) Determine which of the following statements does not represent Ohm's law.
- [A] potential difference = current \times resistance.
 [B] potential difference / current = constant.
 [C] current = resistance \times potential difference.
 [D] current / potential difference = constant.
- (20) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- [A] 2Ω .
 [B] 3Ω .
 [C] 1Ω .
 [D] 6Ω .
- (21) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.
- [A] (b).
 [B] (d).
 [C] (a).
 [D] (c).
- (22) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] $D \cdot P$.
 [B] $D^2 \cdot P$.
 [C] D^2/P .
 [D] $D \cdot P^2$.
- (23) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- [A] 5 W.
 [B] 10 W.
 [C] 20 W.
 [D] 15 W.

- (24) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- A $\frac{R_Y}{R_X} = \frac{1}{4}$.
 B $\frac{R_Y}{R_X} = \frac{2}{1}$.
 C $\frac{R_Y}{R_X} = \frac{1}{1}$.
 D $\frac{R_Y}{R_X} = \frac{1}{2}$.
- (25) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:
- A 2Ω and 3Ω in series and the combination in parallel to 4Ω .
 B all in parallel.
 C 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 D all in series.
- (26) Ohm's law relates potential difference with:
- A power.
 B time.
 C current.
 D energy.
- (27) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:
- A 810Ω .
 B 270Ω .
 C 30Ω .
 D 10Ω .
- (28) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- A $R = \frac{A}{\rho L}$.
 B $R = \frac{L}{\rho A}$.
 C $R = \frac{\rho A}{L}$.
 D $R = \frac{\rho L}{A}$.
- (29) The unit of electric power is:
- A ampere.
 B volt.
 C joule.
 D watt.
- (30) The resistivity of a wire depends on:
- A material.
 B length.
 C area of cross-section.
 D length, material and area of cross-section.
- (31) In Figure 4 at the end of the text,
- A 3Ω , 6Ω and Ω are in parallel.
 B 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
 C 6Ω , 3Ω and 9Ω are in series.
 D 3Ω , 6Ω are in parallel and 9Ω is in series.
- (32) The unit of current is:
- A coulomb.
 B volt.
 C ampere.
 D watt.
- (33) Determine which one of the following statements concerning resistors in parallel is true.
- A The current through each resistor is the same.
 B The power dissipated by each resistor is the same.
 C The total voltage across the resistors is the sum of the voltage across each resistor.
 D The voltage across each resistor is the same.
- (34) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- A Current.
 B Resistance.
 C Power.
 D Voltage.
- (35) Joule/coulomb is same as:
- A volt.
 B watt.
 C ohm.
 D ampere.
- (36) Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:
- A 25Ω .
 B 100Ω .
 C 50Ω .
 D 0Ω .
- (37) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .
- A 2.2×10^{20} .
 B 4.8×10^{15} .
 C 6.4×10^{18} .
 D 36.

- (38) All of the wires in Figure 5 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (d).
 B (c).
 C (b).
 D (a).
- (39) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D \cdot F$.
- B $D \cdot F^2$.
 C D^2/F .
 D $D^2 \cdot F$.
- (40) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 6 at the end of the text.
- A To the left.
 B Upward.
 C To the right.
 D Downward.

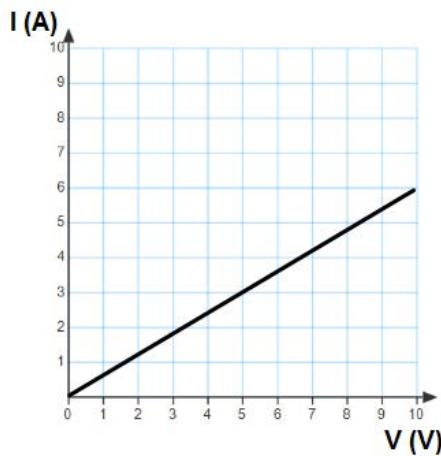


Figura 1

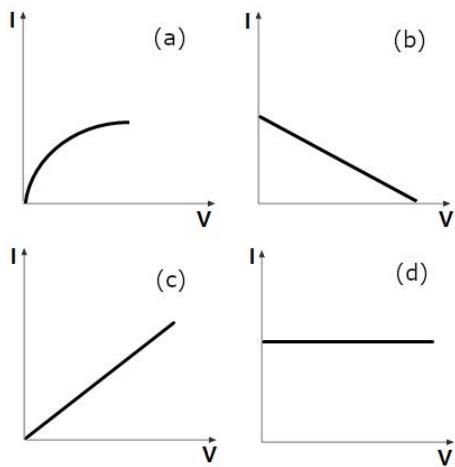


Figura 3

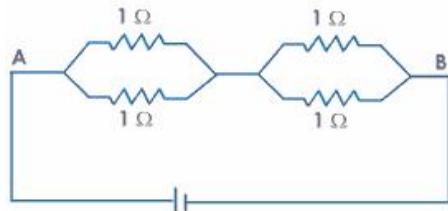


Figura 2



Figura 4

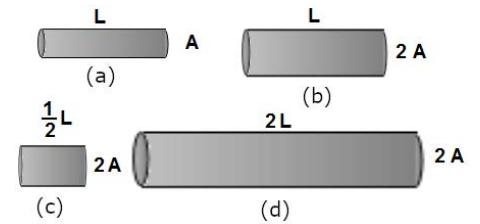


Figura 5

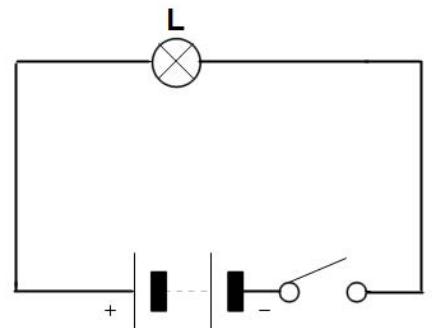


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 24

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- [A] $R = \frac{\rho A}{L}$.
 [B] $R = \frac{A}{\rho L}$.
 [C] $R = \frac{L}{\rho A}$.
 [D] $R = \frac{\rho L}{A}$.
- (2) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A . Determine how the resistance of wire B compares to the resistance of wire A .
- [A] $\frac{R_B}{R_A} = \frac{1}{4}$.
 [B] $\frac{R_B}{R_A} = \frac{1}{2}$.
 [C] $\frac{R_B}{R_A} = \frac{2}{1}$.
 [D] $\frac{R_B}{R_A} = \frac{1}{2}$.
- (3) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- [A] $\frac{R_Y}{R_X} = \frac{1}{1}$.
 [B] $\frac{R_Y}{R_X} = \frac{1}{2}$.
 [C] $\frac{R_Y}{R_X} = \frac{1}{4}$.
 [D] $\frac{R_Y}{R_X} = \frac{2}{1}$.
- (4) Joule/coulomb is same as:
- [A] volt.
- (5) When there is an electric current passing through a wire, the particles moving are:
- [A] atoms.
 [B] electrons.
 [C] ions.
 [D] protons.
- (6) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:
- [A] all in parallel.
 [B] 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 [C] all in series.
 [D] 2Ω and 3Ω in series and the combination in parallel to 4Ω .
- (7) Determine which one of the following statements concerning resistors in series is *true*.
- [A] The current through each resistor is the same.
 [B] The voltage across each resistor is the same.
 [C] The total current through the resistors is the sum of the current through each resistor.
 [D] The power dissipated by each resistor is the same.
- (8) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] D^2/P .
 [B] $D^2 \cdot P$.
 [C] $D \cdot P^2$.
 [D] $D \cdot P$.

(9) The current in a wire:

- A depends only on the resistance of the wire.
- B depends on both resistance and potential difference.
- C does not depend on resistance and potential difference.
- D depends only on the potential difference applied.

(10) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.

- A 10 W.
- B 20 W.
- C 5 W.
- D 15 W.

(11) The unit of resistivity is:

- A ohm.
- B ohm/m².
- C ohm/m.
- D ohm·m.

(12) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A current.
- B potential difference.
- C power.
- D resistance.

(13) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D^2 \cdot F$.
- B $D \cdot F^2$.
- C D^2/F .
- D $D \cdot F$.

(14) Determine which one of the following statements concerning resistors in parallel is *true*.

- A The voltage across each resistor is the same.
- B The power dissipated by each resistor is the same.
- C The current through each resistor is the same.
- D The total voltage across the resistors is the sum of the voltage across each resistor.

(15) A positive charge released from rest:

- A moves towards the regions of lower potential.
- B does not move.
- C moves towards the regions of equal potential.
- D moves towards the regions of higher potential.

(16) In Figure 2 at the end of the text, the resistance across AB is:

- A 2 Ω.
- B 1 Ω.
- C 4 Ω.
- D 0.5 Ω.

(17) Complete the following statement: “The electromotive force is:

- A the force that accelerates protons through a wire when a battery is connected to it”.
- B the force that accelerates electrons through a wire when a battery is connected to it”.
- C the maximum potential difference between the terminals of a battery”.
- D the maximum electric potential energy stored within a battery”.

(18) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

- A 6 Ω.
- B 1 Ω.
- C 2 Ω.
- D 3 Ω.

(19) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- A 120 J.
- B 15 J.
- C 30 J.
- D 60 J.

(20) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Current.
- B Resistance.
- C Power.
- D Voltage.

(21) The resistivity of a wire depends on:

- A length.
- B material.
- C length, material and area of cross-section.
- D area of cross-section.

(22) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 600 C.
- B 500 C.
- C 200 C.
- D 400 C.

(23) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

A 36.

B 2.2×10^{20} .

C 6.4×10^{18} .

D 4.8×10^{15} .

- (24) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.

A (d).

B (b).

C (a).

D (c).

- (25) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 3Ω .

B 2Ω .

C 1Ω .

D 6Ω .

- (26) Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:

A 50Ω .

B 25Ω .

C 100Ω .

D 0Ω .

- (27) All of the wires in Figure 4 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (c).

B (a).

C (d).

D (b).

- (28) A battery is used to:

A maintain a potential difference.

B measure electric current.

C safeguard against short-circuit.

D measure electric potential.

- (29) In Figure 5 at the end of the text,

A 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .

B 3Ω , 6Ω are in parallel and 9Ω is in series.

C 3Ω , 6Ω and 9Ω are in parallel.

D 6Ω , 3Ω and 9Ω are in series.

- (30) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

A 0.5 W .

B 5 W .

C 2 W .

D 0.2 W .

- (31) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:

A 25Ω .

B 0Ω .

C 50Ω .

D 100Ω .

- (32) Ohm's law relates potential difference with:

A energy.

B power.

C time.

D current.

- (33) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.

A 0.4Ω .

B 1Ω .

C 0.8Ω .

D 1.7Ω .

- (34) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

A 100 V .

B 1 V .

C 40 V .

D 4 V .

- (35) When a current I flows through a resistance R for time t the electrical energy spent is given by:

A I^2R/t .

B IR^2t .

C IRt .

D I^2Rt .

- (36) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:

A 30Ω .

B 270Ω .

C 810Ω .

D 10Ω .

- (37) The unit of electric power is:

A joule.

B watt.

C volt.

D ampere.

(38) The unit of current is:

- A volt.
- B watt.
- C coulomb.
- D ampere.

(39) Determine which of the following statements does not represent Ohm's law.

- A potential difference / current = constant.
- B potential difference = current \times resistance.

C current = resistance \times potential difference.

D current / potential difference = constant.

(40) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 6 at the end of the text.

- A Downward.
- B Upward.
- C To the left.
- D To the right.

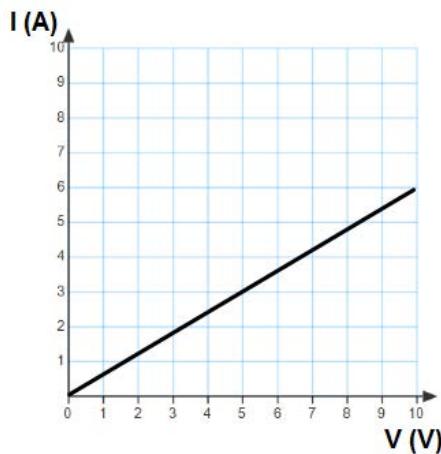


Figura 1

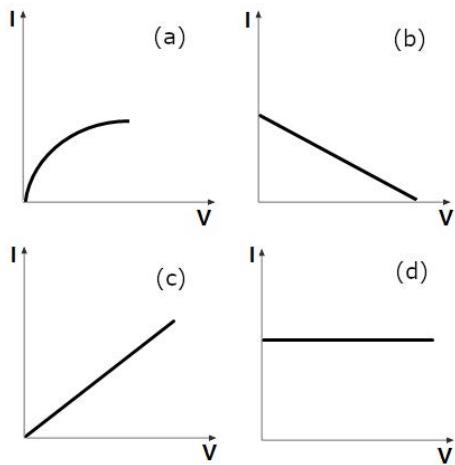


Figura 3

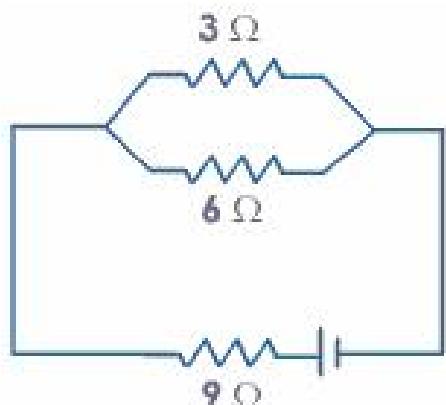


Figura 5

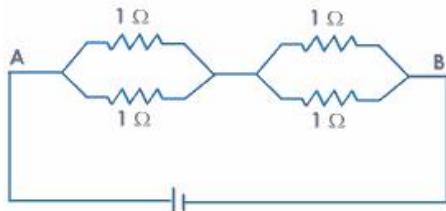


Figura 2

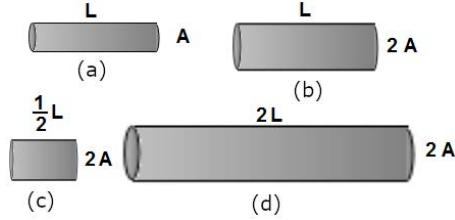


Figura 4

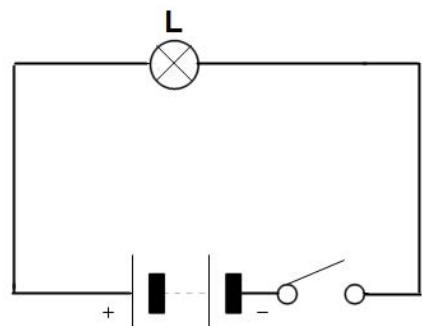


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 25

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
- [A] 36.
 [B] 2.2×10^{20} .
 [C] 6.4×10^{18} .
 [D] 4.8×10^{15} .
- ② Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 6Ω .
 [B] 2Ω .
 [C] 1Ω .
 [D] 3Ω .
- ③ When there is an electric current passing through a wire, the particles moving are:
- [A] protons.
 [B] atoms.
 [C] electrons.
 [D] ions.
- ④ The current in a wire:
- [A] depends on both resistance and potential difference.
 [B] does not depend on resistance and potential difference.
 [C] depends only on the potential difference applied.
 [D] depends only on the resistance of the wire.
- ⑤ In Figure 1 at the end of the text,
- [A] 3Ω , 6Ω are in parallel and 9Ω is in series.
 [B] 6Ω , 3Ω and 9Ω are in series.
 [C] 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
- ⑥ Determine which one of the following statements concerning resistors in parallel is *true*.
- [A] The voltage across each resistor is the same.
 [B] The total voltage across the resistors is the sum of the voltage across each resistor.
 [C] The power dissipated by each resistor is the same.
 [D] The current through each resistor is the same.
- ⑦ If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- [A] $D^2 \cdot P$.
 [B] $D \cdot P$.
 [C] $D \cdot P^2$.
 [D] D^2/P .
- ⑧ The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 0.5 W.
 [B] 2 W.
 [C] 5 W.
 [D] 0.2 W.
- ⑨ A battery is used to:
- [A] safeguard against short-circuit.
 [B] measure electric potential.
 [C] measure electric current.
 [D] maintain a potential difference.
- ⑩ The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- [A] 10 W.

- B 20 W.
 C 5 W.
 D 15 W.

(11) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- A $R = \frac{\rho A}{L}$.
 B $R = \frac{A}{\rho L}$.
 C $R = \frac{\rho L}{A}$.
 D $R = \frac{L}{\rho A}$.

(12) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A IR^2t .
 B I^2Rt .
 C I^2R/t .
 D IRt .

(13) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A resistance.
 B power.
 C potential difference.
 D current.

(14) A positive charge released from rest:

- A moves towards the regions of lower potential.
 B moves towards the regions of higher potential.
 C does not move.
 D moves towards the regions of equal potential.

(15) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

- A 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 B all in parallel.
 C 2Ω and 3Ω in series and the combination in parallel to 4Ω .
 D all in series.

(16) Determine which of the following statements does not represent Ohm's law.

- A current / potential difference = constant.
 B potential difference = current \times resistance.
 C potential difference / current = constant.
 D current = resistance \times potential difference.

(17) Complete the following statement: "The electromotive force is:

- A the maximum potential difference between the terminals of a battery".
 B the force that accelerates electrons through a wire when a battery is connected to it".
 C the maximum electric potential energy stored within a battery".
 D the force that accelerates protons through a wire when a battery is connected to it".

(18) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

- A 100 V.
 B 1 V.
 C 40 V.
 D 4 V.

(19) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D \cdot F^2$.
 B D^2/F .
 C $D^2 \cdot F$.
 D $D \cdot F$.

(20) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:

- A 100Ω .
 B 50Ω .
 C 0Ω .
 D 25Ω .

(21) All of the wires in Figure 3 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- A (c).
 B (a).
 C (b).
 D (d).

(22) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- A $\frac{R_Y}{R_X} = \frac{2}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{2}$.
 C $\frac{R_Y}{R_X} = \frac{1}{4}$.
 D $\frac{R_Y}{R_X} = \frac{1}{2}$.

(23) The electric current as a function of voltage of a wire is presented by the graph in Figure 2. Compute the resistance of the wire.

- A 0.4Ω .
 B 1.7Ω .

- C 1 Ω .
 D 0.8 Ω .

(24) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A 1 Ω .
 B 3 Ω .
 C 6 Ω .
 D 2 Ω .

(25) In Figure 4 at the end of the text, the resistance across AB is:

- A 0.5 Ω .
 B 4 Ω .
 C 2 Ω .
 D 1 Ω .

(26) Determine which one of the following statements concerning resistors in series is true.

- A The current through each resistor is the same.
 B The voltage across each resistor is the same.
 C The total current through the resistors is the sum of the current through each resistor.
 D The power dissipated by each resistor is the same.

(27) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

- A $\frac{R_B}{R_A} = \frac{2}{1}$.
 B $\frac{R_B}{R_A} = \frac{1}{2}$.
 C $\frac{R_B}{R_A} = \frac{1}{4}$.
 D $\frac{R_B}{R_A} = \frac{1}{1}$.

(28) Two resistances of 100 Ω and zero ohm are connected in series. The overall resistance will be:

- A 25 Ω .
 B 50 Ω .
 C 100 Ω .
 D 0 Ω .

(29) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Power.
 B Voltage.
 C Resistance.
 D Current.

(30) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 5 at the end of the text.

- A To the left.
 B Downward.
 C Upward.
 D To the right.

(31) Ohm's law relates potential difference with:

- A energy.
 B time.
 C current.
 D power.

(32) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

- A 15 J.
 B 120 J.
 C 30 J.
 D 60 J.

(33) The unit of electric power is:

- A ampere.
 B watt.
 C volt.
 D joule.

(34) Determine which of the graphs in Figure 6 at the end of the text represents Ohm's law for a solid conductor.

- A (d).
 B (a).
 C (b).
 D (c).

(35) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 200 C.
 B 400 C.
 C 600 C.
 D 500 C.

(36) The resistivity of a wire depends on:

- A material.
 B length, material and area of cross-section.
 C area of cross-section.
 D length.

(37) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:

- A 30 Ω .
 B 270 Ω .
 C 10 Ω .

D 810 Ω .

(38) The unit of resistivity is:

- A ohm/m.
- B ohm/m².
- C ohm.
- D ohm·m.

(39) The unit of current is:

- A ampere.

B coulomb.

C watt.

D volt.

(40) Joule/coulomb is same as:

- A volt.
- B ohm.
- C watt.
- D ampere.

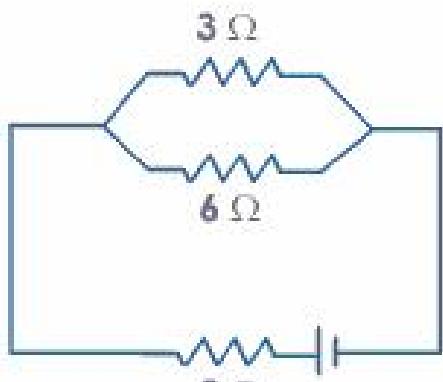


Figura 1

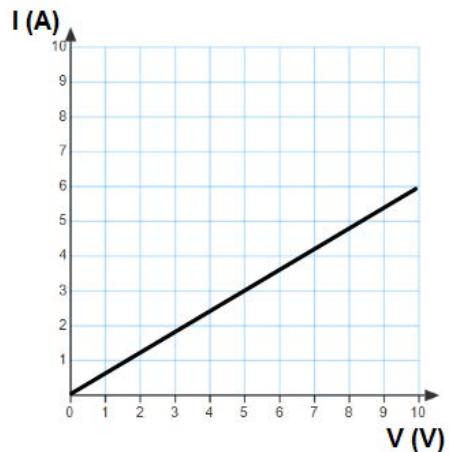


Figura 2

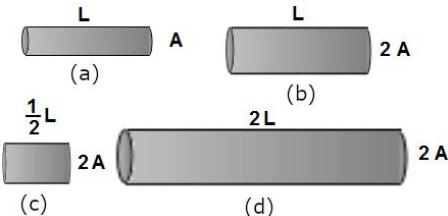


Figura 3

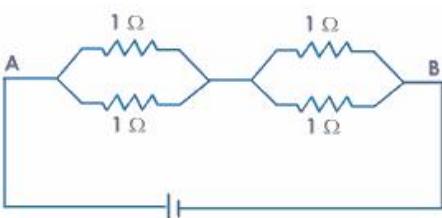


Figura 4

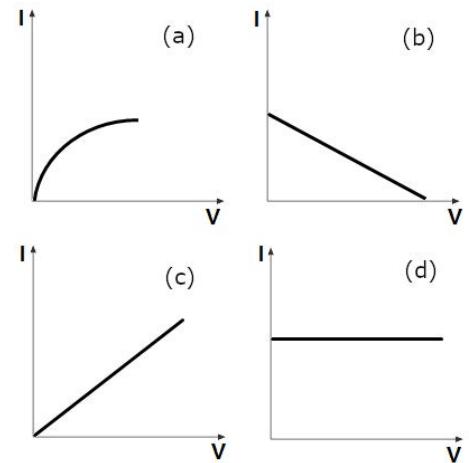


Figura 6

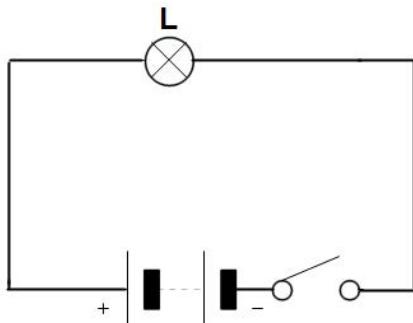


Figura 5

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 26

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- (1) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A current.
 B power.
 C resistance.
 D potential difference.
- (2) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:
- A $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
 B all in series.
 C all in parallel.
 D $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
- (3) Determine which of the graphs in Figure 1 at the end of the text represents Ohm's law for a solid conductor.
- A (c).
 B (b).
 C (a).
 D (d).
- (4) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D^2 \cdot F$.
 B D^2/F .
 C $D \cdot F$.
 D $D \cdot F^2$.
- (5) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A $10\ \Omega$.
 B $270\ \Omega$.
- (6) Determine which one of the following statements concerning resistors in parallel is *true*.
- A The total voltage across the resistors is the sum of the voltage across each resistor.
 B The power dissipated by each resistor is the same.
 C The voltage across each resistor is the same.
 D The current through each resistor is the same.
- (7) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{1}{1}$.
 B $\frac{R_B}{R_A} = \frac{1}{2}$.
 C $\frac{R_B}{R_A} = \frac{1}{4}$.
 D $\frac{R_B}{R_A} = \frac{2}{1}$.
- (8) The unit of electric power is:
- A volt.
 B joule.
 C ampere.
 D watt.
- (9) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- A $10\ \Omega$.
 B $270\ \Omega$.

C $30\ \Omega$.

D $810\ \Omega$.

(10) A positive charge released from rest:

- A moves towards the regions of lower potential.
- B does not move.
- C moves towards the regions of higher potential.
- D moves towards the regions of equal potential.

(11) The unit of resistivity is:

- A ohm/m.
- B ohm·m.
- C ohm/m².
- D ohm.

(12) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.

- A To the left.
- B Upward.
- C To the right.
- D Downward.

(13) Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A $3\ \Omega$.
- B $2\ \Omega$.
- C $1\ \Omega$.
- D $6\ \Omega$.

(14) All of the wires in Figure 3 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- A (d).
- B (c).
- C (a).
- D (b).

(15) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A D^2/P .
- B $D \cdot P$.
- C $D^2 \cdot P$.
- D $D \cdot P^2$.

(16) In Figure 4 at the end of the text, the resistance across AB is:

- A $4\ \Omega$.
- B $2\ \Omega$.
- C $0.5\ \Omega$.

D $1\ \Omega$.

(17) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Resistance.
- B Power.
- C Current.
- D Voltage.

(18) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.

- A $1\ \Omega$.
- B $2\ \Omega$.
- C $3\ \Omega$.
- D $6\ \Omega$.

(19) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:

- A $25\ \Omega$.
- B $0\ \Omega$.
- C $100\ \Omega$.
- D $50\ \Omega$.

(20) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A IRt .
- B IR^2t .
- C I^2Rt .
- D I^2R/t .

(21) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

- A $25\ \Omega$.
- B $0\ \Omega$.
- C $100\ \Omega$.
- D $50\ \Omega$.

(22) The resistance of an electric bulb drawing $1.2\ A$ current at $6.0\ V$ is:

- A $0.5\ W$.
- B $0.2\ W$.
- C $5\ W$.
- D $2\ W$.

(23) The unit of current is:

- A watt.
- B coulomb.
- C volt.
- D ampere.

(24) Determine which one of the following statements concerning resistors in series is *true*.

- A The power dissipated by each resistor is the same.

- (B) The current through each resistor is the same.
 (C) The voltage across each resistor is the same.
 (D) The total current through the resistors is the sum of the current through each resistor.
- (25) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
 (A) 400 C.
 (B) 600 C.
 (C) 200 C.
 (D) 500 C.
- (26) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
 (A) $R = \frac{\rho A}{L}$.
 (B) $R = \frac{\rho L}{A}$.
 (C) $R = \frac{A}{\rho L}$.
 (D) $R = \frac{L}{\rho A}$.
- (27) Ohm's law relates potential difference with:
 (A) current.
 (B) energy.
 (C) power.
 (D) time.
- (28) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:
 (A) 100 V.
 (B) 4 V.
 (C) 1 V.
 (D) 40 V.
- (29) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the resistance of the wire.
 (A) 0.8Ω .
 (B) 1Ω .
 (C) 1.7Ω .
 (D) 0.4Ω .
- (30) A battery is used to:
 (A) measure electric potential.
 (B) safeguard against short-circuit.
 (C) measure electric current.
 (D) maintain a potential difference.
- (31) In Figure 6 at the end of the text,
- (A) 6Ω , 3Ω and 9Ω are in series.
 (B) 3Ω , 6Ω are in parallel and 9Ω is in series.
 (C) 3Ω , 6Ω and 9Ω are in parallel.
 (D) 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
- (32) Joule/coulomb is same as:
 (A) ohm.
 (B) watt.
 (C) ampere.
 (D) volt.
- (33) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.
 (A) 2.2×10^{20} .
 (B) 36.
 (C) 6.4×10^{18} .
 (D) 4.8×10^{15} .
- (34) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
 (A) $\frac{R_Y}{R_X} = \frac{1}{1}$.
 (B) $\frac{R_Y}{R_X} = \frac{1}{2}$.
 (C) $\frac{R_Y}{R_X} = \frac{2}{1}$.
 (D) $\frac{R_Y}{R_X} = \frac{1}{4}$.
- (35) Determine which of the following statements does not represent Ohm's law.
 (A) current / potential difference = constant.
 (B) potential difference = current \times resistance.
 (C) potential difference / current = constant.
 (D) current = resistance \times potential difference.
- (36) When there is an electric current passing through a wire, the particles moving are:
 (A) ions.
 (B) protons.
 (C) electrons.
 (D) atoms.
- (37) The resistivity of a wire depends on:
 (A) length, material and area of cross-section.
 (B) material.
 (C) length.
 (D) area of cross-section.
- (38) Complete the following statement: "The electromotive force is:

- A the maximum electric potential energy stored within a battery”.
- B the maximum potential difference between the terminals of a battery”.
- C the force that accelerates protons through a wire when a battery is connected to it”.
- D the force that accelerates electrons through a wire when a battery is connected to it”.
- (39) The current in a wire:
- A depends on both resistance and potential difference.
- B does not depend on resistance and potential difference.
- C depends only on the resistance of the wire.
- D depends only on the potential difference applied.
- (40) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- A 20 W.
- B 10 W.
- C 15 W.
- D 5 W.

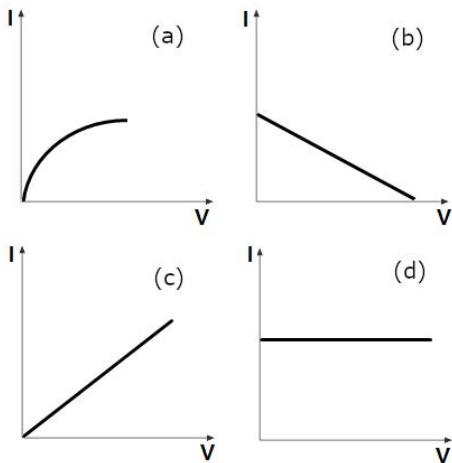


Figura 1

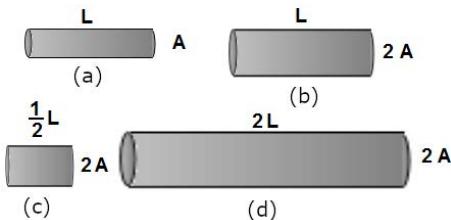


Figura 3

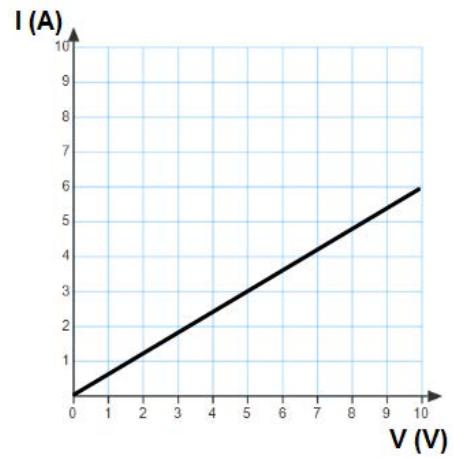


Figura 5

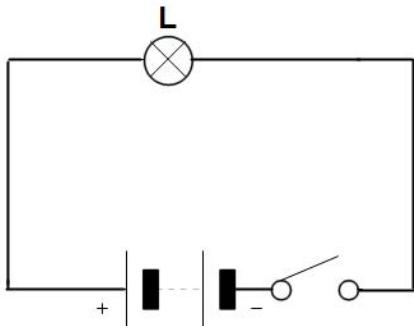


Figura 2

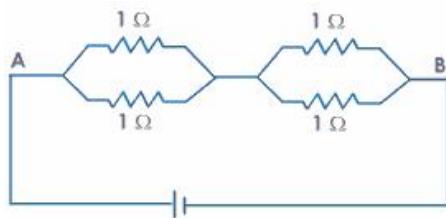


Figura 4

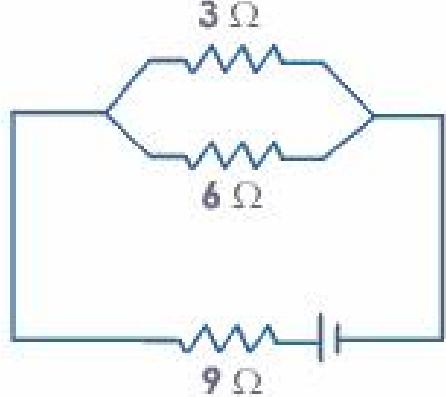


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 27

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- 1 Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
- A $0\ \Omega$.
 B $50\ \Omega$.
 C $100\ \Omega$.
 D $25\ \Omega$.
- 2 The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- A Power.
 B Current.
 C Voltage.
 D Resistance.
- 3 If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D \cdot F$.
 B $D \cdot F^2$.
 C $D^2 \cdot F$.
 D D^2/F .
- 4 Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{1}{2}$.
 B $\frac{R_B}{R_A} = \frac{1}{4}$.
 C $\frac{R_B}{R_A} = \frac{2}{1}$.
 D $\frac{R_B}{R_A} = \frac{1}{1}$.
- 5 A positive charge released from rest:
- A moves towards the regions of higher potential.
 B does not move.
 C moves towards the regions of equal potential.
 D moves towards the regions of lower potential.
- 6 The current in a wire:
- A does not depend on resistance and potential difference.
 B depends only on the potential difference applied.
 C depends on both resistance and potential difference.
 D depends only on the resistance of the wire.
- 7 Determine which one of the following statements concerning resistors in series is *true*.
- A The total current through the resistors is the sum of the current through each resistor.
 B The power dissipated by each resistor is the same.
 C The current through each resistor is the same.
 D The voltage across each resistor is the same.
- 8 Two resistors $R_1 = 3\ \Omega$ and $R_2 = 6\ \Omega$ are connected in parallel. Compute the net resistance in the circuit.
- A $6\ \Omega$.
 B $2\ \Omega$.
 C $3\ \Omega$.
 D $1\ \Omega$.
- 9 All of the wires in Figure 1 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (b).
 B (d).
 C (c).
 D (a).

- (10) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- A $25\ \Omega$.
 B $50\ \Omega$.
 C $0\ \Omega$.
 D $100\ \Omega$.
- (11) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- A $R = \frac{\rho A}{L}$.
 B $R = \frac{\rho L}{A}$.
 C $R = \frac{L}{\rho A}$.
 D $R = \frac{A}{\rho L}$.
- (12) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.
- A Downward.
 B Upward.
 C To the right.
 D To the left.
- (13) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A power.
 B potential difference.
 C current.
 D resistance.
- (14) Complete the following statement: "The electromotive force is:
- A the maximum electric potential energy stored within a battery.
 B the force that accelerates protons through a wire when a battery is connected to it".
 C the maximum potential difference between the terminals of a battery".
 D the force that accelerates electrons through a wire when a battery is connected to it".
- (15) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 200 C .
 B 600 C .
 C 500 C .
 D 400 C .
- (16) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.
- A $1\ \Omega$.
 B $3\ \Omega$.
 C $6\ \Omega$.
 D $2\ \Omega$.
- (17) A battery is used to:
- A maintain a potential difference.
 B measure electric potential.
 C measure electric current.
 D safeguard against short-circuit.
- (18) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 2 W .
 B 0.2 W .
 C 5 W .
 D 0.5 W .
- (19) The resistivity of a wire depends on:
- A area of cross-section.
 B length, material and area of cross-section.
 C length.
 D material.
- (20) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:
- A $\frac{R_Y}{R_X} = \frac{1}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{4}$.
 C $\frac{R_Y}{R_X} = \frac{2}{1}$.
 D $\frac{R_Y}{R_X} = \frac{1}{2}$.
- (21) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- A $D \cdot P$.
 B $D^2 \cdot P$.
 C $D \cdot P^2$.
 D D^2/P .
- (22) The unit of resistivity is:
- A ohm/m.
 B ohm.
 C ohm/m².
 D ohm·m.
- (23) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A IRt .
 B IR^2t .
 C I^2Rt .
 D I^2R/t .

(24) The unit of electric power is:

- A volt.
 B ampere.
 C watt.
 D joule.

(25) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:

- A $10\ \Omega$.
 B $810\ \Omega$.
 C $270\ \Omega$.
 D $30\ \Omega$.

(26) The unit of current is:

- A volt.
 B coulomb.
 C watt.
 D ampere.

(27) In Figure 3 at the end of the text,

- A $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 B $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
 C $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 D $3\ \Omega$, $6\ \Omega$ and $9\ \Omega$ are in parallel.

(28) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:

- A $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.
 B all in parallel.
 C all in series.
 D $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.

(29) Heat produced in a current carrying wire in 5s is 60 J . The same current is passed through another wire of half the resistance. The heat produced in 5s will be:

- A 15 J .
 B 120 J .
 C 30 J .
 D 60 J .

(30) When there is an electric current passing through a wire, the particles moving are:

- A atoms.
 B ions.
 C protons.
 D electrons.

(31) Joule/coulomb is same as:

- A ampere.
 B volt.
 C watt.
 D ohm.

(32) In Figure 4 at the end of the text, the resistance across AB is:

- A $4\ \Omega$.
 B $0.5\ \Omega$.
 C $1\ \Omega$.
 D $2\ \Omega$.

(33) Determine which of the following statements does not represent Ohm's law.

- A potential difference = current \times resistance.
 B potential difference / current = constant.
 C current = resistance \times potential difference.
 D current / potential difference = constant.

(34) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the power dissipated in the resistor when the applied voltage is 5 V .

- A 10 W .
 B 20 W .
 C 5 W .
 D 15 W .

(35) Determine which of the graphs in Figure 6 at the end of the text represents Ohm's law for a solid conductor.

- A (a).
 B (d).
 C (c).
 D (b).

(36) The potential difference required to pass a current 0.2 A in a wire of resistance $20\ \Omega$ is:

- A 100 V .
 B 4 V .
 C 40 V .
 D 1 V .

(37) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .

- A 2.2×10^{20} .
 B 4.8×10^{15} .
 C 36.
 D 6.4×10^{18} .

- (38) The electric current as a function of voltage of a wire is presented by the graph in Figure 5. Compute the resistance of the wire.

- A 1.7Ω .
- B 0.8Ω .
- C 0.4Ω .
- D 1Ω .

- (39) Ohm's law relates potential difference with:

- A time.
- B current.

C power.

D energy.

- (40) Determine which one of the following statements concerning resistors in parallel is *true*.

- A The total voltage across the resistors is the sum of the voltage across each resistor.
- B The power dissipated by each resistor is the same.
- C The current through each resistor is the same.
- D The voltage across each resistor is the same.

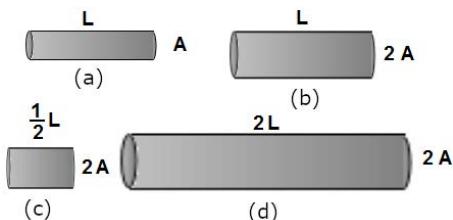


Figura 1

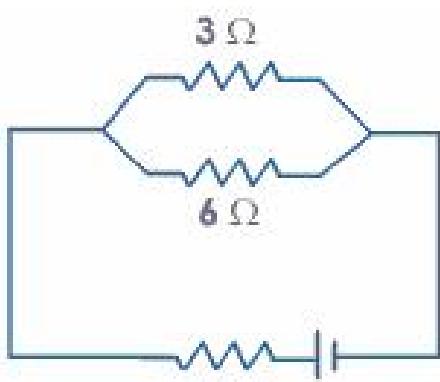


Figura 3

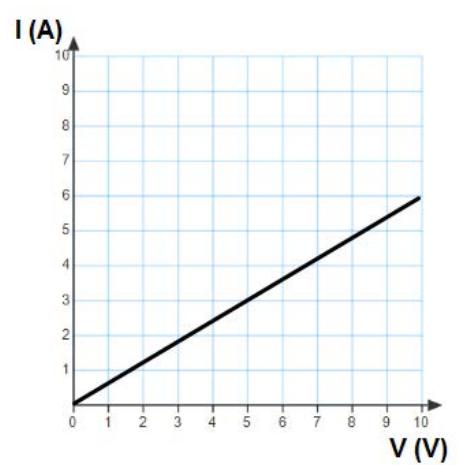


Figura 5

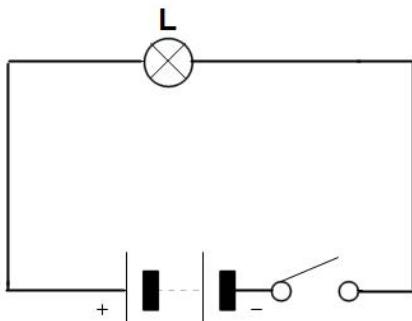


Figura 2

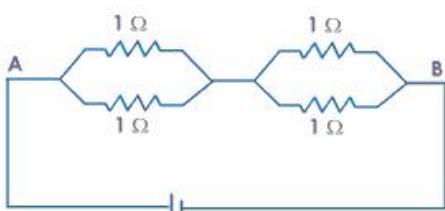


Figura 4

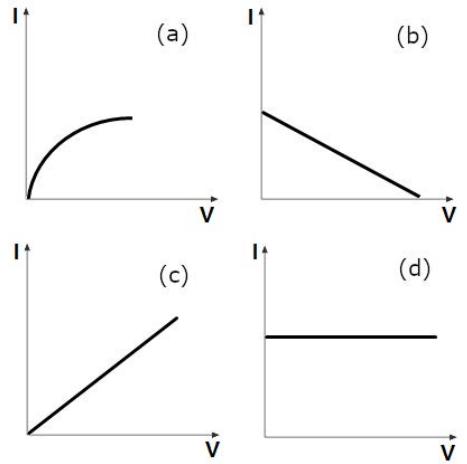


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 28

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- [A] 10 W.
 [B] 20 W.
 [C] 15 W.
 [D] 5 W.
- ② A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- [A] $R = \frac{\rho L}{A}$.
 [B] $R = \frac{L}{\rho A}$.
 [C] $R = \frac{A}{\rho L}$.
 [D] $R = \frac{\rho A}{L}$.
- ③ Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:
- [A] 0Ω .
 [B] 25Ω .
 [C] 100Ω .
 [D] 50Ω .
- ④ Determine which one of the following statements concerning resistors in series is *true*.
- [A] The total current through the resistors is the sum of the current through each resistor.
 [B] The voltage across each resistor is the same.
 [C] The current through each resistor is the same.
 [D] The power dissipated by each resistor is the same.
- ⑤ Joule/coulomb is same as:
- [A] volt.
 [B] watt.
 [C] ampere.
 [D] ohm.
- ⑥ Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 2 at the end of the text.
- [A] Downward.
 [B] To the right.
 [C] To the left.
 [D] Upward.
- ⑦ Determine which of the following statements does not represent Ohm's law.
- [A] current = resistance \times potential difference.
 [B] current / potential difference = constant.
 [C] potential difference = current \times resistance.
 [D] potential difference / current = constant.
- ⑧ A battery is used to:
- [A] safeguard against short-circuit.
 [B] measure electric current.
 [C] measure electric potential.
 [D] maintain a potential difference.
- ⑨ When there is an electric current passing through a wire, the particles moving are:
- [A] ions.
 [B] protons.
 [C] atoms.
 [D] electrons.

- (10) Determine which of the graphs in Figure 3 at the end of the text represents Ohm's law for a solid conductor.

- [A] (c).
- [B] (d).
- [C] (a).
- [D] (b).

- (11) The resistivity of a wire depends on:

- [A] material.
- [B] length.
- [C] area of cross-section.
- [D] length, material and area of cross-section.

- (12) Three resistors $2\ \Omega$, $3\ \Omega$ and $4\ \Omega$ are connected so that the equivalent resistance is $9\ \Omega$. The resistors are connected:

- [A] $2\ \Omega$ and $3\ \Omega$ in series and the combination in parallel to $4\ \Omega$.
- [B] all in series.
- [C] all in parallel.
- [D] $2\ \Omega$ and $3\ \Omega$ in parallel and the combination in series with $4\ \Omega$.

- (13) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- [A] $\frac{R_Y}{R_X} = \frac{1}{4}$.
- [B] $\frac{R_Y}{R_X} = \frac{1}{1}$.
- [C] $\frac{R_Y}{R_X} = \frac{2}{1}$.
- [D] $\frac{R_Y}{R_X} = \frac{1}{2}$.

- (14) Two resistors $R_1 = 6\ \Omega$ and $R_2 = 12\ \Omega$ are connected in parallel to each other and in series to $R_2 = 2\ \Omega$. Compute the net resistance in the circuit.

- [A] $3\ \Omega$.
- [B] $1\ \Omega$.
- [C] $6\ \Omega$.
- [D] $2\ \Omega$.

- (15) A positive charge released from rest:

- [A] does not move.
- [B] moves towards the regions of equal potential.
- [C] moves towards the regions of higher potential.
- [D] moves towards the regions of lower potential.

- (16) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:

- [A] $100\ \Omega$.
- [B] $50\ \Omega$.

[C] $25\ \Omega$.

[D] $0\ \Omega$.

- (17) The unit of resistivity is:

- [A] ohm/m^2 .
- [B] $\text{ohm}\cdot\text{m}$.
- [C] ohm/m .
- [D] ohm .

- (18) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.

- [A] $1.7\ \Omega$.
- [B] $1\ \Omega$.
- [C] $0.8\ \Omega$.
- [D] $0.4\ \Omega$.

- (19) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:

- [A] $810\ \Omega$.
- [B] $30\ \Omega$.
- [C] $270\ \Omega$.
- [D] $10\ \Omega$.

- (20) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

- [A] $\frac{R_B}{R_A} = \frac{1}{4}$.
- [B] $\frac{R_B}{R_A} = \frac{2}{1}$.
- [C] $\frac{R_B}{R_A} = \frac{1}{2}$.
- [D] $\frac{R_B}{R_A} = \frac{1}{1}$.

- (21) The current in a wire:

- [A] depends only on the resistance of the wire.
- [B] depends only on the potential difference applied.
- [C] does not depend on resistance and potential difference.
- [D] depends on both resistance and potential difference.

- (22) Determine which one of the following statements concerning resistors in parallel is *true*.

- [A] The total voltage across the resistors is the sum of the voltage across each resistor.
- [B] The power dissipated by each resistor is the same.
- [C] The voltage across each resistor is the same.
- [D] The current through each resistor is the same.

- (23) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- [A] 600 C .

- B 200 C.
- C 500 C.
- D 400 C.

(24) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A 2Ω .
- B 1Ω .
- C 3Ω .
- D 6Ω .

(25) The unit of electric power is:

- A volt.
- B ampere.
- C watt.
- D joule.

(26) In Figure 4 at the end of the text, the resistance across AB is:

- A 0.5Ω .
- B 1Ω .
- C 2Ω .
- D 4Ω .

(27) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A $D \cdot P^2$.
- B D^2/P .
- C $D \cdot P$.
- D $D^2 \cdot P$.

(28) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

- A 100 V.
- B 1 V.
- C 40 V.
- D 4 V.

(29) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A IRt .
- B IR^2t .
- C I^2R/t .
- D I^2Rt .

(30) Ohm's law relates potential difference with:

- A time.
- B power.
- C current.
- D energy.

(31) In Figure 5 at the end of the text,

- A 3Ω , 6Ω are in parallel and 9Ω is in series.
- B 3Ω , 6Ω and Ω are in parallel.
- C 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
- D 6Ω , 3Ω and 9Ω are in series.

(32) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

- A power.
- B current.
- C potential difference.
- D resistance.

(33) Heat produced in a current carrying wire in 5s is 60 J . The same current is passed through another wire of half the resistance. The heat produced in 5s will be:

- A 60 J .
- B 15 J .
- C 30 J .
- D 120 J .

(34) All of the wires in Figure 6 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- A (a).
- B (d).
- C (c).
- D (b).

(35) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

- A 0.2 W .
- B 5 W .
- C 2 W .
- D 0.5 W .

(36) The unit of current is:

- A watt.
- B coulomb.
- C ampere.
- D volt.

(37) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .

- A 36.
- B 2.2×10^{20} .
- C 4.8×10^{15} .
- D 6.4×10^{18} .

(38) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Voltage.
 B Power.
 C Resistance.
 D Current.

(39) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

- A $D \cdot F^2$.
 B $D \cdot F$.
 C D^2/F .

- D $D^2 \cdot F$.

(40) Complete the following statement: "The electromotive force is:

- A the force that accelerates protons through a wire when a battery is connected to it".
 B the force that accelerates electrons through a wire when a battery is connected to it".
 C the maximum electric potential energy stored within a battery".
 D the maximum potential difference between the terminals of a battery".

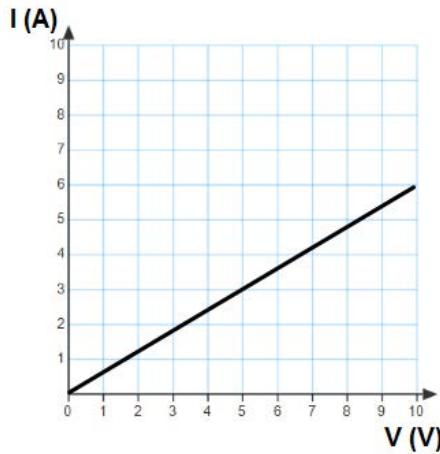


Figura 1

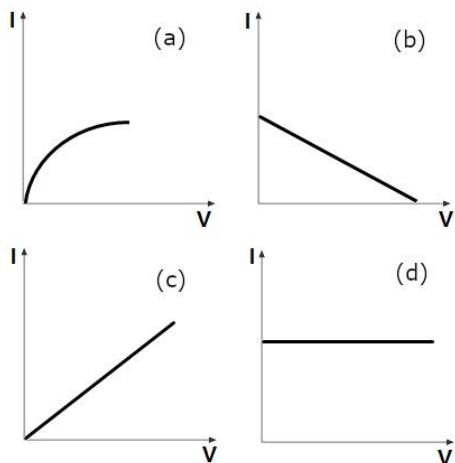


Figura 3

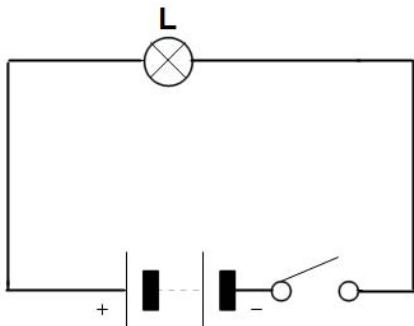


Figura 2

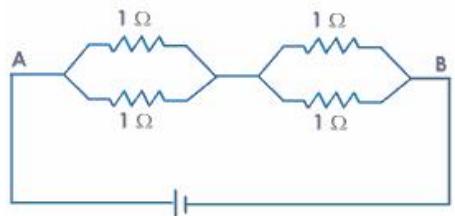


Figura 4

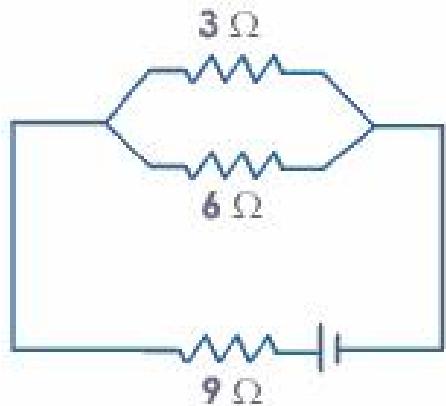


Figura 5

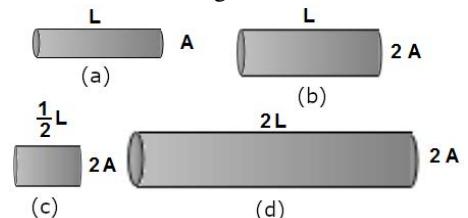


Figura 6

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 29

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:
- A 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 - B all in series.
 - C all in parallel.
 - D 2Ω and 3Ω in series and the combination in parallel to 4Ω .
- ② Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:
- A 25Ω .
 - B 0Ω .
 - C 50Ω .
 - D 100Ω .
- ③ Heat produced in a current carrying wire in 5s is 60 J . The same current is passed through another wire of half the resistance. The heat produced in 5s will be:
- A 15 J .
 - B 120 J .
 - C 30 J .
 - D 60 J .
- ④ A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- A $R = \frac{\rho L}{A}$.
 - B $R = \frac{A}{\rho L}$.
 - C $R = \frac{\rho A}{L}$.
 - D $R = \frac{L}{\rho A}$.
- ⑤ Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- A 1Ω .
 - B 6Ω .
 - C 2Ω .
 - D 3Ω .
- ⑥ Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s .
- A 4.8×10^{15} .
 - B 2.2×10^{20} .
 - C 36.
 - D 6.4×10^{18} .
- ⑦ In Figure 1 at the end of the text,
- A 3Ω , 6Ω and Ω are in parallel.
 - B 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
 - C 3Ω , 6Ω are in parallel and 9Ω is in series.
 - D 6Ω , 3Ω and 9Ω are in series.
- ⑧ Determine which of the graphs in Figure 2 at the end of the text represents Ohm's law for a solid conductor.
- A (d).
 - B (a).
 - C (b).
 - D (c).
- ⑨ Ohm's law relates potential difference with:
- A power.
 - B energy.
 - C time.
 - D current.

- (10) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- A $D^2 \cdot P$.
 B $D \cdot P$.
 C D^2/P .
 D $D \cdot P^2$.
- (11) A battery is used to:
- A safeguard against short-circuit.
 B maintain a potential difference.
 C measure electric potential.
 D measure electric current.
- (12) The unit of current is:
- A volt.
 B watt.
 C ampere.
 D coulomb.
- (13) Joule/coulomb is same as:
- A watt.
 B ampere.
 C volt.
 D ohm.
- (14) When there is an electric current passing through a wire, the particles moving are:
- A electrons.
 B atoms.
 C protons.
 D ions.
- (15) All of the wires in Figure 3 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (c).
 B (a).
 C (b).
 D (d).
- (16) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 4 at the end of the text.
- A To the right.
 B Downward.
 C To the left.
 D Upward.
- (17) The resistivity of a wire depends on:
- A material.
 B length.
 C length, material and area of cross-section.
 D area of cross-section.
- (18) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 5 W.
 B 2 W.
 C 0.2 W.
 D 0.5 W.
- (19) In Figure 5 at the end of the text, the resistance across AB is:
- A 0.5Ω .
 B 1Ω .
 C 4Ω .
 D 2Ω .
- (20) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 600 C.
 B 400 C.
 C 500 C.
 D 200 C.
- (21) The electric current as a function of voltage of a wire is presented by the graph in Figure 6. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- A 20 W.
 B 15 W.
 C 10 W.
 D 5 W.
- (22) The unit of electric power is:
- A volt.
 B ampere.
 C joule.
 D watt.
- (23) The current in a wire:
- A depends on both resistance and potential difference.
 B does not depend on resistance and potential difference.
 C depends only on the resistance of the wire.
 D depends only on the potential difference applied.
- (24) The electric current as a function of voltage of a wire is presented by the graph in Figure 6. Compute the resistance of the wire.
- A 1Ω .
 B 0.8Ω .
 C 1.7Ω .

D 0.4Ω .

- (25) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{1}{4}$.

B $\frac{R_Y}{R_X} = \frac{1}{1}$.

C $\frac{R_Y}{R_X} = \frac{2}{1}$.

D $\frac{R_Y}{R_X} = \frac{1}{2}$.

- (26) The unit of resistivity is:

A ohm/m.

B ohm·m.

C ohm/m².

D ohm.

- (27) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

A Resistance.

B Voltage.

C Power.

D Current.

- (28) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

A 100 V.

B 1 V.

C 4 V.

D 40 V.

- (29) When a current I flows through a resistance R for time t the electrical energy spent is given by:

A IRt .

B IR^2t .

C I^2R/t .

D I^2Rt .

- (30) Determine which of the following statements does not represent Ohm's law.

A current / potential difference = constant.

B potential difference = current \times resistance.

C current = resistance \times potential difference.

D potential difference / current = constant.

- (31) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 1Ω .

B 2Ω .

C 6Ω .

D 3Ω .

- (32) A positive charge released from rest:

A moves towards the regions of higher potential.

B does not move.

C moves towards the regions of lower potential.

D moves towards the regions of equal potential.

- (33) Determine which one of the following statements concerning resistors in parallel is *true*.

A The total voltage across the resistors is the sum of the voltage across each resistor.

B The power dissipated by each resistor is the same.

C The current through each resistor is the same.

D The voltage across each resistor is the same.

- (34) Complete the following statement: "The electromotive force is:

A the force that accelerates electrons through a wire when a battery is connected to it".

B the force that accelerates protons through a wire when a battery is connected to it".

C the maximum potential difference between the terminals of a battery".

D the maximum electric potential energy stored within a battery".

- (35) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

A resistance.

B potential difference.

C current.

D power.

- (36) Determine which one of the following statements concerning resistors in series is *true*.

A The current through each resistor is the same.

B The power dissipated by each resistor is the same.

C The voltage across each resistor is the same.

D The total current through the resistors is the sum of the current through each resistor.

- (37) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:

A $D^2 \cdot F$.

B $D \cdot F$.

C D^2/F .

D $D \cdot F^2$.

- (38) Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:

A 25Ω .

B 50Ω .

C 0 Ω .

D 100 Ω .

- (39) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:

A 270 Ω .

B 10 Ω .

C 810 Ω .

D 30 Ω .







- (40) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{1}{2}$.

B $\frac{R_B}{R_A} = \frac{2}{1}$.

C $\frac{R_B}{R_A} = \frac{1}{4}$.

D $\frac{R_B}{R_A} = \frac{1}{1}$.

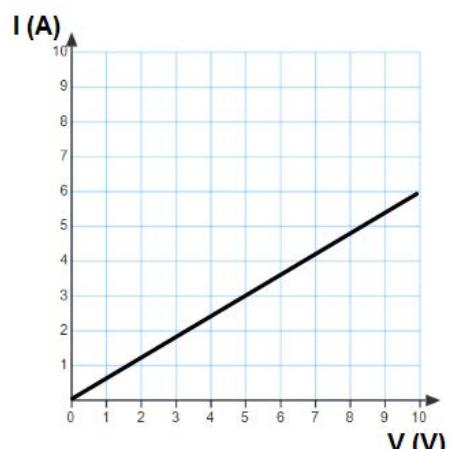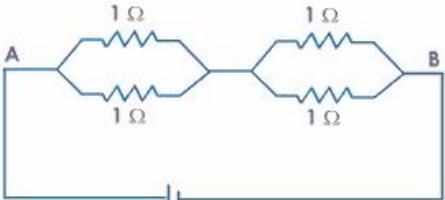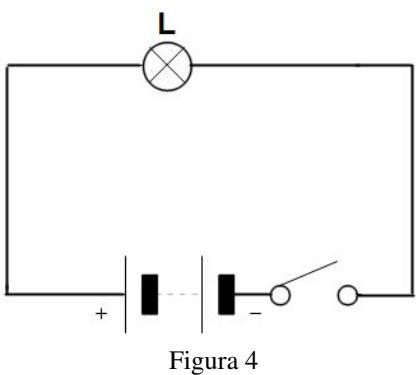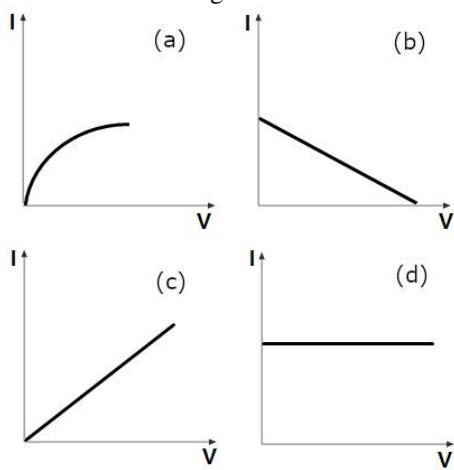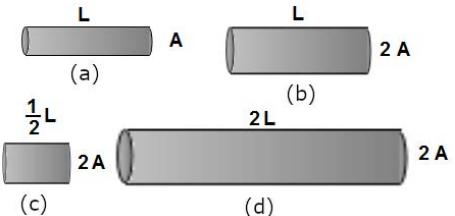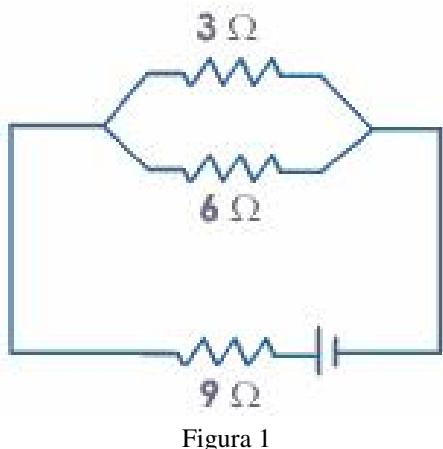

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 30

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																				
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	

- (1) Ohm's law relates potential difference with:
- A current.
 B energy.
 C power.
 D time.
- (2) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{2}{1}$.
 B $\frac{R_B}{R_A} = \frac{1}{2}$.
 C $\frac{R_B}{R_A} = \frac{1}{4}$.
 D $\frac{R_B}{R_A} = \frac{1}{2}$.
- (3) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D \cdot F$.
 B $D \cdot F^2$.
 C $D^2 \cdot F$.
 D D^2/F .
- (4) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:
- A 40 V.
 B 4 V.
 C 100 V.
 D 1 V.
- (5) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- A 2 Ω .
 B 3 Ω .
 C 6 Ω .
 D 1 Ω .
- (6) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- A 0.5 W.
 B 5 W.
 C 2 W.
 D 0.2 W.
- (7) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A 15 J.
 B 30 J.
 C 60 J.
 D 120 J.
- (8) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:
- A $D^2 \cdot P$.
 B $D \cdot P^2$.
 C $D \cdot P$.
 D D^2/P .
- (9) Determine which of the following statements does not represent Ohm's law.
- A current = resistance \times potential difference.
 B current / potential difference = constant.
 C potential difference = current \times resistance.

- (D) potential difference / current = constant.
- (10) The resistivity of a wire depends on:
- (A) length.
 - (B) length, material and area of cross-section.
 - (C) area of cross-section.
 - (D) material.
- (11) When there is an electric current passing through a wire, the particles moving are:
- (A) atoms.
 - (B) protons.
 - (C) ions.
 - (D) electrons.
- (12) Three equal resistances when combined in series are equivalent to $90\ \Omega$. Their equivalent resistance when combined in parallel will be:
- (A) $30\ \Omega$.
 - (B) $810\ \Omega$.
 - (C) $270\ \Omega$.
 - (D) $10\ \Omega$.
- (13) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- (A) $50\ \Omega$.
 - (B) $25\ \Omega$.
 - (C) $0\ \Omega$.
 - (D) $100\ \Omega$.
- (14) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V .
- (A) 10 W .
 - (B) 20 W .
 - (C) 15 W .
 - (D) 5 W .
- (15) A positive charge released from rest:
- (A) does not move.
 - (B) moves towards the regions of equal potential.
 - (C) moves towards the regions of lower potential.
 - (D) moves towards the regions of higher potential.
- (16) The unit of current is:
- (A) ampere.
 - (B) watt.
 - (C) coulomb.
 - (D) volt.
- (17) Determine which one of the following statements concerning resistors in series is *true*.
- (A) The voltage across each resistor is the same.
 - (B) The power dissipated by each resistor is the same.
 - (C) The current through each resistor is the same.
 - (D) The total current through the resistors is the sum of the current through each resistor.
- (18) In Figure 2 at the end of the text,
- (A) $6\ \Omega$, $3\ \Omega$ and $9\ \Omega$ are in series.
 - (B) $9\ \Omega$ and $6\ \Omega$ are in parallel and the combination is in series with $3\ \Omega$.
 - (C) $3\ \Omega$, $6\ \Omega$ are in parallel and $9\ \Omega$ is in series.
 - (D) $3\ \Omega$, $6\ \Omega$ and $9\ \Omega$ are in parallel.
- (19) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 3 at the end of the text.
- (A) Downward.
 - (B) Upward.
 - (C) To the right.
 - (D) To the left.
- (20) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
- (A) $0\ \Omega$.
 - (B) $50\ \Omega$.
 - (C) $100\ \Omega$.
 - (D) $25\ \Omega$.
- (21) A battery is used to:
- (A) safeguard against short-circuit.
 - (B) measure electric potential.
 - (C) maintain a potential difference.
 - (D) measure electric current.
- (22) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- (A) potential difference.
 - (B) current.
 - (C) power.
 - (D) resistance.
- (23) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- (A) IRt .
 - (B) IR^2t .
 - (C) I^2Rt .
 - (D) I^2R/t .
- (24) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- A $\frac{R_Y}{R_X} = \frac{1}{4}$.
- B $\frac{R_Y}{R_X} = \frac{1}{1}$.
- C $\frac{R_Y}{R_X} = \frac{1}{2}$.
- D $\frac{R_Y}{R_X} = \frac{2}{1}$.

(25) The current in a wire:

- A does not depend on resistance and potential difference.
- B depends only on the potential difference applied.
- C depends on both resistance and potential difference.
- D depends only on the resistance of the wire.

(26) Determine which of the graphs in Figure 4 at the end of the text represents Ohm's law for a solid conductor.

- A (c).
- B (d).
- C (b).
- D (a).

(27) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.

- A 400 C.
- B 600 C.
- C 200 C.
- D 500 C.

(28) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

- A 2.2×10^{20} .
- B 4.8×10^{15} .
- C 6.4×10^{18} .
- D 36.

(29) Joule/coulomb is same as:

- A volt.
- B watt.
- C ampere.
- D ohm.

(30) All of the wires in Figure 5 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

- A (d).
- B (c).
- C (b).
- D (a).

(31) The unit of electric power is:

- A joule.
- B watt.
- C ampere.
- D volt.

(32) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:

- A Resistance.
- B Voltage.
- C Power.
- D Current.

(33) The unit of resistivity is:

- A ohm/m.
- B ohm/m².
- C ohm.
- D ohm·m.

(34) Complete the following statement: "The electromotive force is:

- A the force that accelerates protons through a wire when a battery is connected to it".
- B the maximum electric potential energy stored within a battery".
- C the force that accelerates electrons through a wire when a battery is connected to it".
- D the maximum potential difference between the terminals of a battery".

(35) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

- A 2Ω and 3Ω in parallel and the combination in series with 4Ω .
- B all in series.
- C 2Ω and 3Ω in series and the combination in parallel to 4Ω .
- D all in parallel.

(36) Determine which one of the following statements concerning resistors in parallel is true.

- A The total voltage across the resistors is the sum of the voltage across each resistor.
- B The power dissipated by each resistor is the same.
- C The voltage across each resistor is the same.
- D The current through each resistor is the same.

(37) Two resistors $R_1 = 3\Omega$ and $R_2 = 6\Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A 1Ω .
- B 6Ω .
- C 3Ω .
- D 2Ω .

- (38) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.

- A 0.4 Ω .
 B 1 Ω .
 C 0.8 Ω .
 D 1.7 Ω .

- (39) In Figure 6 at the end of the text, the resistance across AB is:

- A 0.5 Ω .
 B 2 Ω .

C 1 Ω .

D 4 Ω .

- (40) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

- A $R = \frac{\rho A}{L}$.
 B $R = \frac{A}{\rho L}$.
 C $R = \frac{L}{\rho A}$.
 D $R = \frac{\rho L}{A}$.

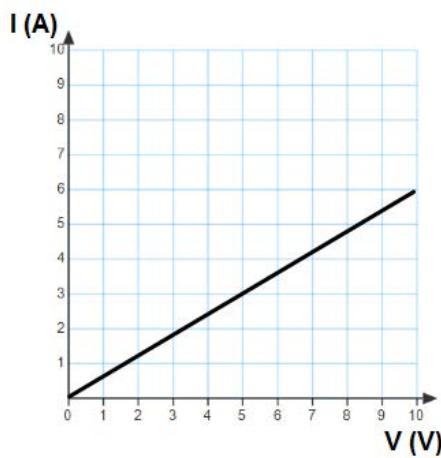


Figura 1

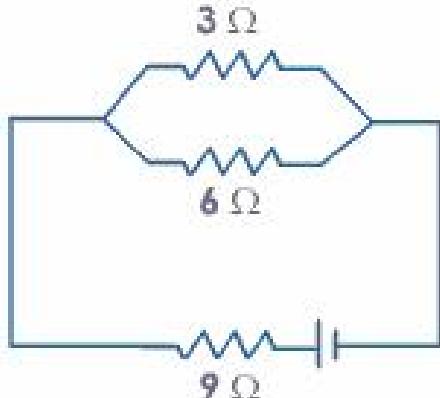


Figura 2

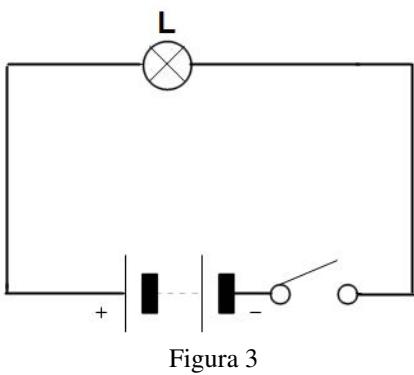


Figura 3

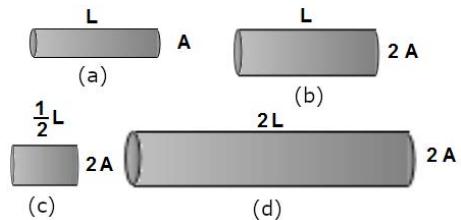


Figura 5

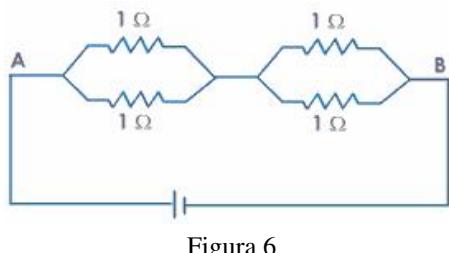


Figura 6

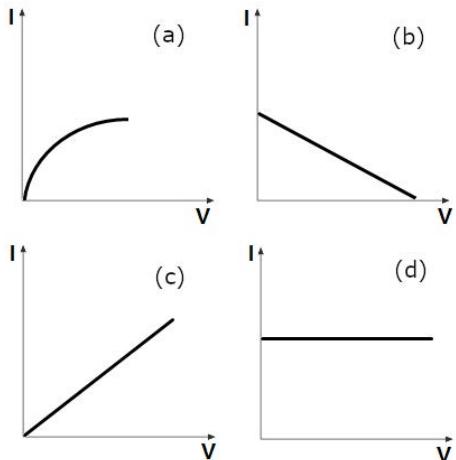


Figura 4

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 31

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																				
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	

- 1) Complete the following statement: “The electromotive force is:
- A the force that accelerates protons through a wire when a battery is connected to it”.
 - B the maximum electric potential energy stored within a battery”.
 - C the force that accelerates electrons through a wire when a battery is connected to it”.
 - D the maximum potential difference between the terminals of a battery”.
- 2) Two resistances of $100\ \Omega$ and zero ohm are connected in parallel. The overall resistance will be:
- A $50\ \Omega$.
 - B $100\ \Omega$.
 - C $25\ \Omega$.
 - D $0\ \Omega$.
- 3) Two resistances of $100\ \Omega$ and zero ohm are connected in series. The overall resistance will be:
- A $25\ \Omega$.
 - B $100\ \Omega$.
 - C $50\ \Omega$.
 - D $0\ \Omega$.
- 4) The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- A Power.
 - B Resistance.
 - C Voltage.
 - D Current.
- 5) Determine which one of the following statements concerning resistors in parallel is *true*.
- 6) The total voltage across the resistors is the sum of the voltage across each resistor.
- 7) The current through each resistor is the same.
- 8) The voltage across each resistor is the same.
- 9) The power dissipated by each resistor is the same.
- 10) If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- A $D \cdot F^2$.
 - B D^2/F .
 - C $D^2 \cdot F$.
 - D $D \cdot F$.
- 11) A $10\ A$ current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A $500\ C$.
 - B $400\ C$.
 - C $600\ C$.
 - D $200\ C$.
- 12) When a current I flows through a resistance R for time t the electrical energy spent is given by:
- A IRt .
 - B I^2R/t .
 - C I^2Rt .
 - D IR^2t .
- 13) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the resistance of the wire.
- A $0.8\ \Omega$.
 - B $1.7\ \Omega$.
 - C $1\ \Omega$.

A 0.4Ω .

- (10) Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.

A 1Ω .
 B 6Ω .
 C 3Ω .
 D 2Ω .

- (11) In Figure 2 at the end of the text,

A 6Ω , 3Ω and 9Ω are in series.
 B 3Ω , 6Ω are in parallel and 9Ω is in series.
 C 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .
 D 3Ω , 6Ω and 9Ω are in parallel.

- (12) Three equal resistances when combined in series are equivalent to 90Ω . Their equivalent resistance when combined in parallel will be:

A 30Ω .
 B 10Ω .
 C 810Ω .
 D 270Ω .

- (13) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.

A $\frac{R_B}{R_A} = \frac{1}{4}$.
 B $\frac{R_B}{R_A} = \frac{1}{2}$.
 C $\frac{R_B}{R_A} = \frac{2}{1}$.
 D $\frac{R_B}{R_A} = \frac{1}{1}$.

- (14) The unit of current is:

A watt.
 B volt.
 C ampere.
 D coulomb.

- (15) The electric current as a function of voltage of a wire is presented by the graph in Figure 1. Compute the power dissipated in the resistor when the applied voltage is 5 V.

A 5 W.
 B 10 W.
 C 15 W.
 D 20 W.

- (16) The current in a wire:

A depends on both resistance and potential difference.

B depends only on the resistance of the wire.

C depends only on the potential difference applied.

D does not depend on resistance and potential difference.

- (17) In Figure 3 at the end of the text, the resistance across AB is:

A 2Ω .
 B 0.5Ω .
 C 4Ω .
 D 1Ω .

- (18) Three resistors 2Ω , 3Ω and 4Ω are connected so that the equivalent resistance is 9Ω . The resistors are connected:

A 2Ω and 3Ω in parallel and the combination in series with 4Ω .
 B 2Ω and 3Ω in series and the combination in parallel to 4Ω .
 C all in series.
 D all in parallel.

- (19) A positive charge released from rest:

A does not move.
 B moves towards the regions of equal potential.
 C moves towards the regions of lower potential.
 D moves towards the regions of higher potential.

- (20) Determine which of the following statements does not represent Ohm's law.

A current / potential difference = constant.
 B potential difference / current = constant.
 C current = resistance \times potential difference.
 D potential difference = current \times resistance.

- (21) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

A 2Ω .
 B 1Ω .
 C 3Ω .
 D 6Ω .

- (22) All of the wires in Figure 4 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.

A (b).
 B (c).
 C (d).
 D (a).

- (23) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

A D^2/P .
 B $D \cdot P^2$.
 C $D \cdot P$.

D $D^2 \cdot P$.

- (24) Joule/coulomb is same as:

A ohm.
 B watt.
 C ampere.
 D volt.

- (25) Determine which of the graphs in Figure 5 at the end of the text represents Ohm's law for a solid conductor.

A (c).
 B (a).
 C (d).
 D (b).

- (26) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

A $\frac{R_Y}{R_X} = \frac{2}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{4}$.
 C $\frac{R_Y}{R_X} = \frac{1}{2}$.
 D $\frac{R_Y}{R_X} = \frac{1}{1}$.

- (27) Heat produced in a current carrying wire in 5s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:

A 120 J.
 B 60 J.
 C 30 J.
 D 15 J.

- (28) Determine which one of the following statements concerning resistors in series is true.

A The current through each resistor is the same.
 B The total current through the resistors is the sum of the current through each resistor.
 C The voltage across each resistor is the same.
 D The power dissipated by each resistor is the same.

- (29) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:

A potential difference.
 B current.
 C power.
 D resistance.

- (30) The potential difference required to pass a current 0.2 A in a wire of resistance 20Ω is:

A 40 V.

B 1 V.

C 4 V.
 D 100 V.

- (31) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

A 36.
 B 4.8×10^{15} .
 C 6.4×10^{18} .
 D 2.2×10^{20} .

- (32) The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:

A 0.2 W.
 B 0.5 W.
 C 5 W.
 D 2 W.

- (33) When there is an electric current passing through a wire, the particles moving are:

A electrons.
 B protons.
 C ions.
 D atoms.

- (34) The unit of electric power is:

A watt.
 B volt.
 C joule.
 D ampere.

- (35) Ohm's law relates potential difference with:

A power.
 B energy.
 C current.
 D time.

- (36) A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.

A $R = \frac{\rho A}{L}$.
 B $R = \frac{\rho L}{A}$.
 C $R = \frac{A}{\rho L}$.
 D $R = \frac{L}{\rho A}$.

- (37) A battery is used to:

A measure electric potential.
 B measure electric current.
 C maintain a potential difference.
 D safeguard against short-circuit.

- (38) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 6 at the end of the text.
- A Downward.
 B Upward.
 C To the right.
 D To the left.
- (39) The resistivity of a wire depends on:
- A length.

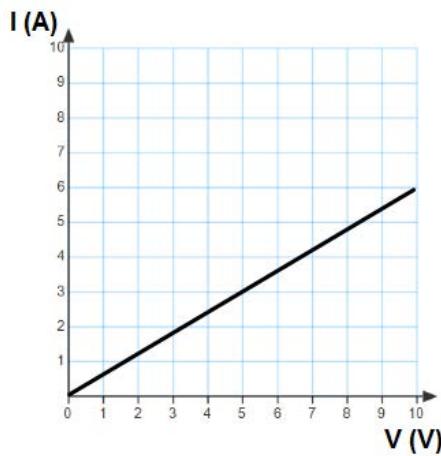


Figura 1

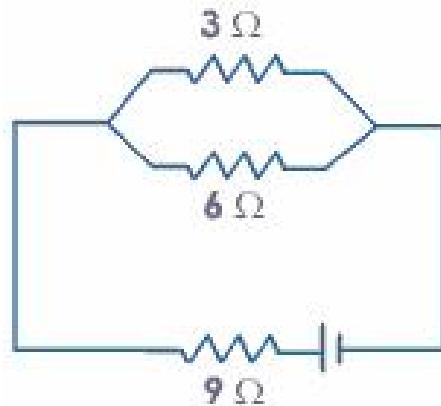


Figura 2

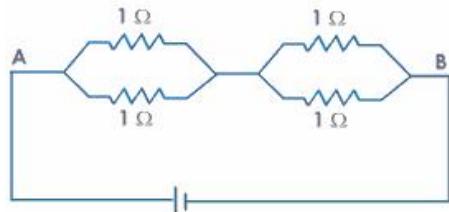


Figura 3

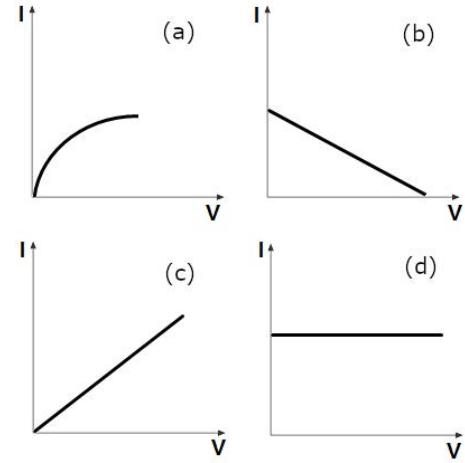


Figura 5

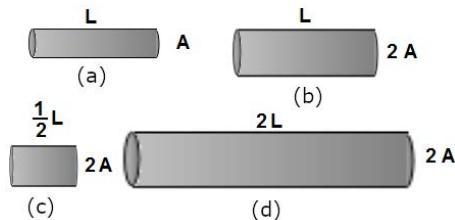


Figura 4

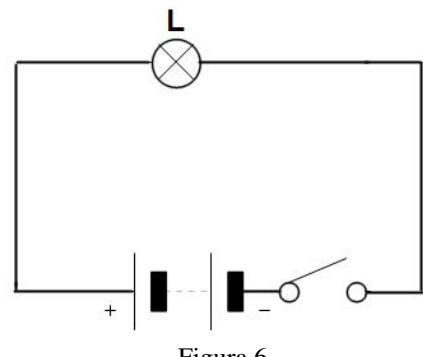


Figura 6

- B length, material and area of cross-section.
 C material.
 D area of cross-section.

- (40) The unit of resistivity is:

- A ohm/m².
 B ohm.
 C ohm·m.
 D ohm/m.

LICEO STATALE “CIRO CIRELLI” DI BORGO SAN CIRO 5° anno – Verifica di Fisica n. 2 – CLIL Electric Currents

Versione 32

Data

Classe

Alunno

Il punteggio per ogni risposta corretta è di 4 punti, per ogni risposta omessa 1 punto, per ogni risposta sbagliata 0 punti. La durata della verifica è di cinquanta minuti. **In ogni caso saranno valutate esclusivamente le risposte riportate nella tabella.**

Risposte																			
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20
21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40

- ① If D is the intensity of current circulating in a resistor with resistance F , the power dissipated by the resistor is described by the formula:
- [A] D^2/F .
 [B] $D \cdot F^2$.
 [C] $D \cdot F$.
 [D] $D^2 \cdot F$.
- ② A wire of length L and cross-sectional area A has a resistivity ρ . Determine which of the following formulas can be used to calculate the resistance of the wire.
- [A] $R = \frac{L}{\rho A}$.
 [B] $R = \frac{\rho L}{A}$.
 [C] $R = \frac{A}{\rho L}$.
 [D] $R = \frac{\rho A}{L}$.
- ③ The current in a wire:
- [A] depends only on the resistance of the wire.
 [B] does not depend on resistance and potential difference.
 [C] depends on both resistance and potential difference.
 [D] depends only on the potential difference applied.
- ④ A battery is used to:
- [A] measure electric current.
 [B] measure electric potential.
 [C] safeguard against short-circuit.
 [D] maintain a potential difference.
- ⑤ The unit of resistivity is:
- [A] ohm/m.
- ⑥ The amount of charge flowing through a cross-sectional area of a wire per unit of time is called:
- [A] Power.
 [B] Current.
 [C] Resistance.
 [D] Voltage.
- ⑦ The unit of electric power is:
- [A] watt.
 [B] ampere.
 [C] volt.
 [D] joule.
- ⑧ The unit of current is:
- [A] ampere.
 [B] coulomb.
 [C] watt.
 [D] volt.
- ⑨ The resistance of an electric bulb drawing 1.2 A current at 6.0 V is:
- [A] 0.2 W.
 [B] 5 W.
 [C] 0.5 W.
 [D] 2 W.
- ⑩ Two resistors $R_1 = 6 \Omega$ and $R_2 = 12 \Omega$ are connected in parallel to each other and in series to $R_2 = 2 \Omega$. Compute the net resistance in the circuit.
- [A] 3Ω .

- B 2 Ω .
- C 1 Ω .
- D 6 Ω .

(11) Compute the number of electrons flowing through a battery that delivers a current of 3.0 A for 12 s.

- A 6.4×10^{18} .
- B 2.2×10^{20} .
- C 36.
- D 4.8×10^{15} .

(12) Two resistances of 100Ω and zero ohm are connected in series. The overall resistance will be:

- A 0 Ω .
- B 25Ω .
- C 50Ω .
- D 100Ω .

(13) Determine the direction of the conventional current through the light bulb in the circuit presented in Figure 1 at the end of the text.

- A Downward.
- B Upward.
- C To the left.
- D To the right.

(14) Determine which one of the following statements concerning resistors in series is *true*.

- A The power dissipated by each resistor is the same.
- B The voltage across each resistor is the same.
- C The current through each resistor is the same.
- D The total current through the resistors is the sum of the current through each resistor.

(15) When there is an electric current passing through a wire, the particles moving are:

- A ions.
- B electrons.
- C atoms.
- D protons.

(16) The resistivity of a wire depends on:

- A length, material and area of cross-section.
- B material.
- C length.
- D area of cross-section.

(17) In Figure 2 at the end of the text,

- A 6Ω , 3Ω and 9Ω are in series.
- B 3Ω , 6Ω and Ω are in parallel.

- C 9Ω and 6Ω are in parallel and the combination is in series with 3Ω .

- D 3Ω , 6Ω are in parallel and 9Ω is in series.

(18) Two resistances of 100Ω and zero ohm are connected in parallel. The overall resistance will be:

- A 0 Ω .
- B 50Ω .
- C 100Ω .
- D 25Ω .

(19) Two resistors $R_1 = 3 \Omega$ and $R_2 = 6 \Omega$ are connected in parallel. Compute the net resistance in the circuit.

- A 2 Ω .
- B 1 Ω .
- C 3 Ω .
- D 6 Ω .

(20) Determine which of the following statements does not represent Ohm's law.

- A current = resistance \times potential difference.
- B potential difference = current \times resistance.
- C current / potential difference = constant.
- D potential difference / current = constant.

(21) When a current I flows through a resistance R for time t the electrical energy spent is given by:

- A IR^2t .
- B I^2R/t .
- C IRt .
- D I^2Rt .

(22) Determine which one of the following statements concerning resistors in parallel is *true*.

- A The voltage across each resistor is the same.
- B The total voltage across the resistors is the sum of the voltage across each resistor.
- C The current through each resistor is the same.
- D The power dissipated by each resistor is the same.

(23) In Figure 3 at the end of the text, the resistance across AB is:

- A 1 Ω .
- B 0.5 Ω .
- C 4 Ω .
- D 2 Ω .

(24) Ohm's law relates potential difference with:

- A current.
- B time.
- C power.
- D energy.

- (25) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the resistance of the wire.
- A 0.4 Ω .
 B 1.7 Ω .
 C 0.8 Ω .
 D 1 Ω .
- (26) The work done in moving a unit positive charge across two points in an electric circuit is a measure of:
- A current.
 B potential difference.
 C power.
 D resistance.
- (27) A positive charge released from rest:
- A does not move.
 B moves towards the regions of lower potential.
 C moves towards the regions of higher potential.
 D moves towards the regions of equal potential.
- (28) Three equal resistances when combined in series are equivalent to 90 Ω . Their equivalent resistance when combined in parallel will be:
- A 810 Ω .
 B 270 Ω .
 C 30 Ω .
 D 10 Ω .
- (29) Joule/coulomb is same as:
- A ohm.
 B ampere.
 C volt.
 D watt.
- (30) Three resistors 2 Ω , 3 Ω and 4 Ω are connected so that the equivalent resistance is 9 Ω . The resistors are connected:
- A all in series.
 B 2 Ω and 3 Ω in parallel and the combination in series with 4 Ω .
 C all in parallel.
 D 2 Ω and 3 Ω in series and the combination in parallel to 4 Ω .
- (31) A 10 A current is maintained in a simple circuit. Compute the net charge that passes through any point in the circuit during a 1 minute interval.
- A 600 C.
 B 400 C.
 C 500 C.
 D 200 C.
- (32) Determine which of the graphs in Figure 5 at the end of the text represents Ohm's law for a solid conductor.
- A (a).
 B (c).
 C (d).
 D (b).
- (33) The electric current as a function of voltage of a wire is presented by the graph in Figure 4. Compute the power dissipated in the resistor when the applied voltage is 5 V.
- A 20 W.
 B 5 W.
 C 10 W.
 D 15 W.
- (34) All of the wires in Figure 6 at the end of the text are made of the same material but are different sizes. Identify the wire with the lowest resistance.
- A (d).
 B (c).
 C (a).
 D (b).
- (35) Heat produced in a current carrying wire in 5 s is 60 J. The same current is passed through another wire of half the resistance. The heat produced in 5 s will be:
- A 120 J.
 B 15 J.
 C 60 J.
 D 30 J.
- (36) Two aluminum wires have the same length and different cross-sectional area. Wire B has twice the radius of that of wire A. Determine how the resistance of wire B compares to the resistance of wire A.
- A $\frac{R_B}{R_A} = \frac{2}{1}$.
 B $\frac{R_B}{R_A} = \frac{1}{1}$.
 C $\frac{R_B}{R_A} = \frac{1}{4}$.
 D $\frac{R_B}{R_A} = \frac{1}{2}$.
- (37) Complete the following statement: "The electromotive force is:
- A the force that accelerates protons through a wire when a battery is connected to it".
 B the maximum potential difference between the terminals of a battery".
 C the force that accelerates electrons through a wire when a battery is connected to it".
 D the maximum electric potential energy stored within a battery".
- (38) The potential difference required to pass a current 0.2 A in a wire of resistance 20 Ω is:

- A 4 V.
 B 40 V.
 C 100 V.
 D 1 V.

(39) Two copper wires have the same cross-sectional area but have different lengths. Wire X has a length L and wire Y has a length $2L$. The ratio between the resistance of wire Y and wire X is:

- A $\frac{R_Y}{R_X} = \frac{2}{1}$.
 B $\frac{R_Y}{R_X} = \frac{1}{1}$.

- C $\frac{R_Y}{R_X} = \frac{1}{2}$.
 D $\frac{R_Y}{R_X} = \frac{1}{4}$.

(40) If D is the intensity of current circulating in a conductor and P is the voltage across the conductor, the power dissipated is described by the formula:

- A $D^2 \cdot P$.
 B $D \cdot P$.
 C $D \cdot P^2$.
 D D^2 / P .

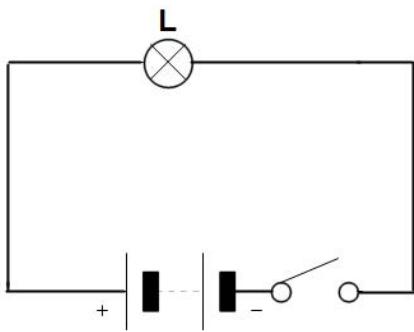


Figura 1

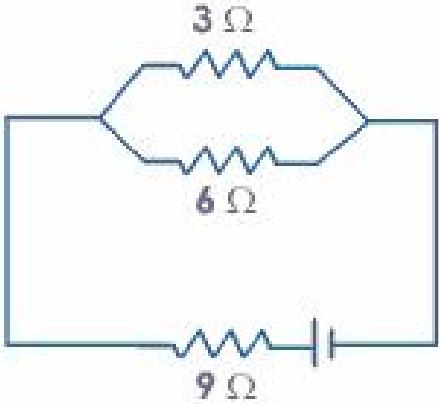


Figura 2

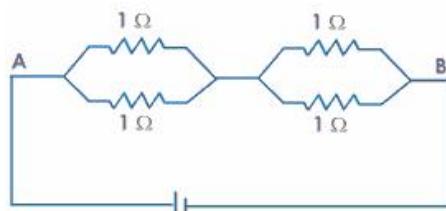


Figura 3

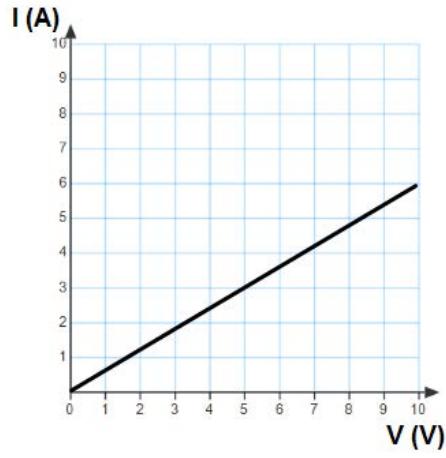


Figura 4

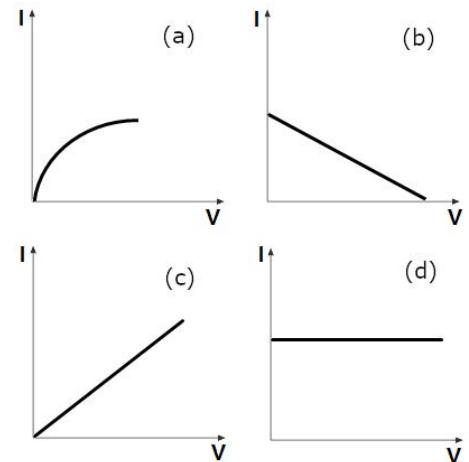


Figura 5

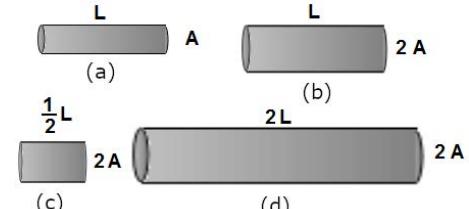


Figura 6